

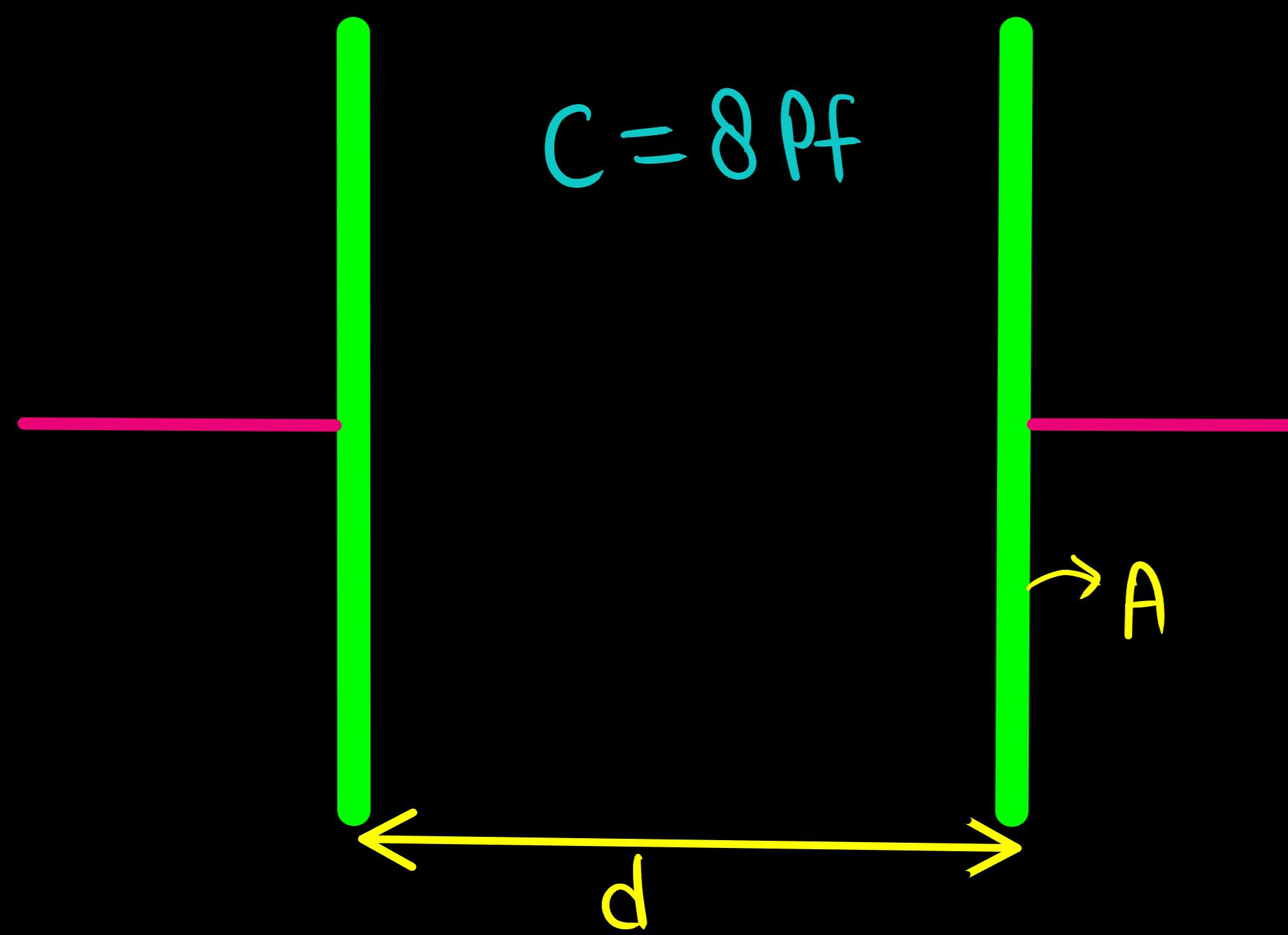


- 2.5** A parallel plate capacitor with air between the plates has a capacitance of 8 pF ($1\text{pF} = 10^{-12}\text{ F}$). What will be the capacitance if the distance between the plates is reduced by half, and the space between them is filled with a substance of dielectric constant 6?


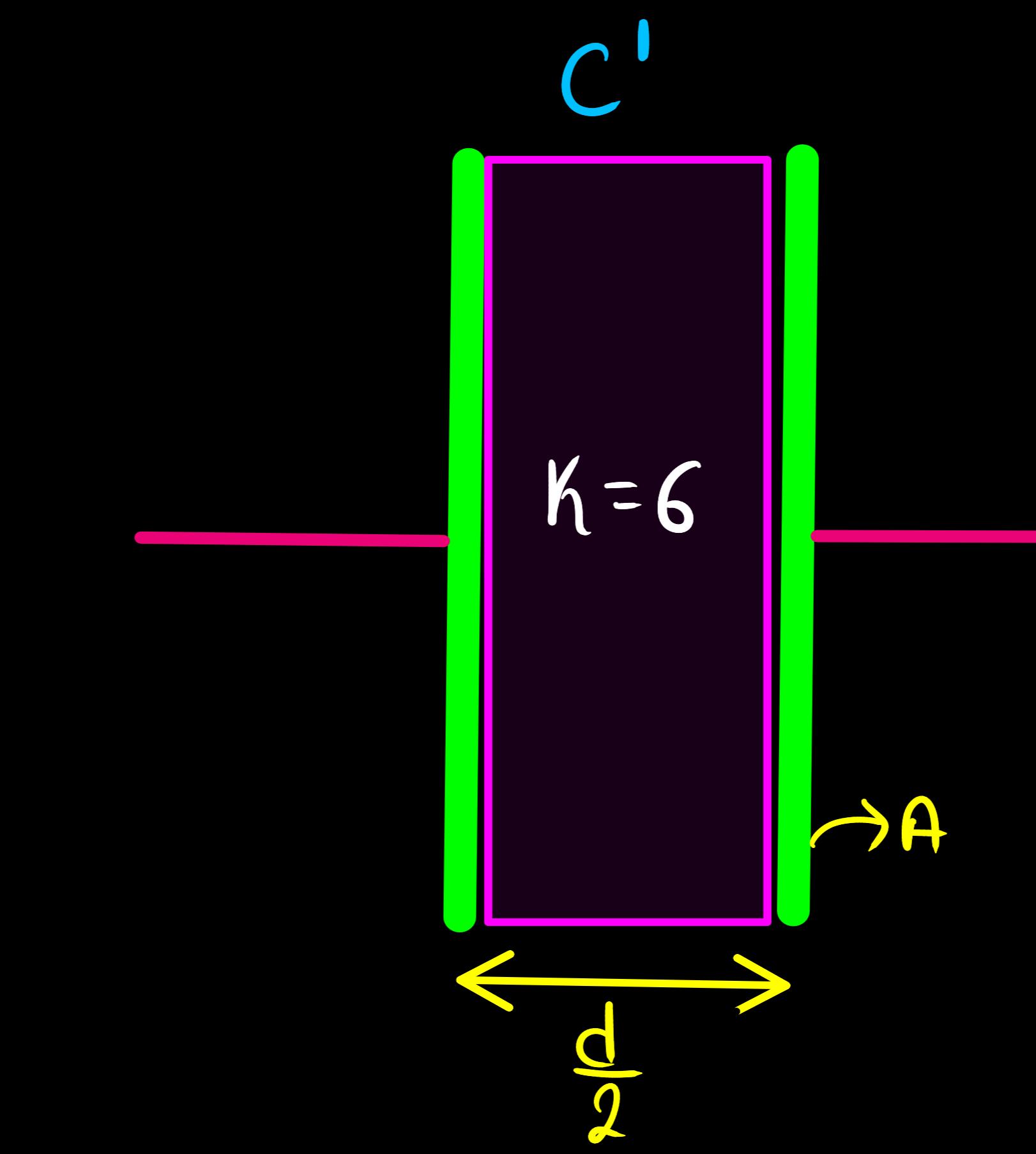
2.5 A parallel plate capacitor with air between the plates has a capacitance of 8 pF ($1\text{pF} = 10^{-12} \text{ F}$). What will be the capacitance if the distance between the plates is reduced by half, and the space between them is filled with a substance of dielectric constant 6?



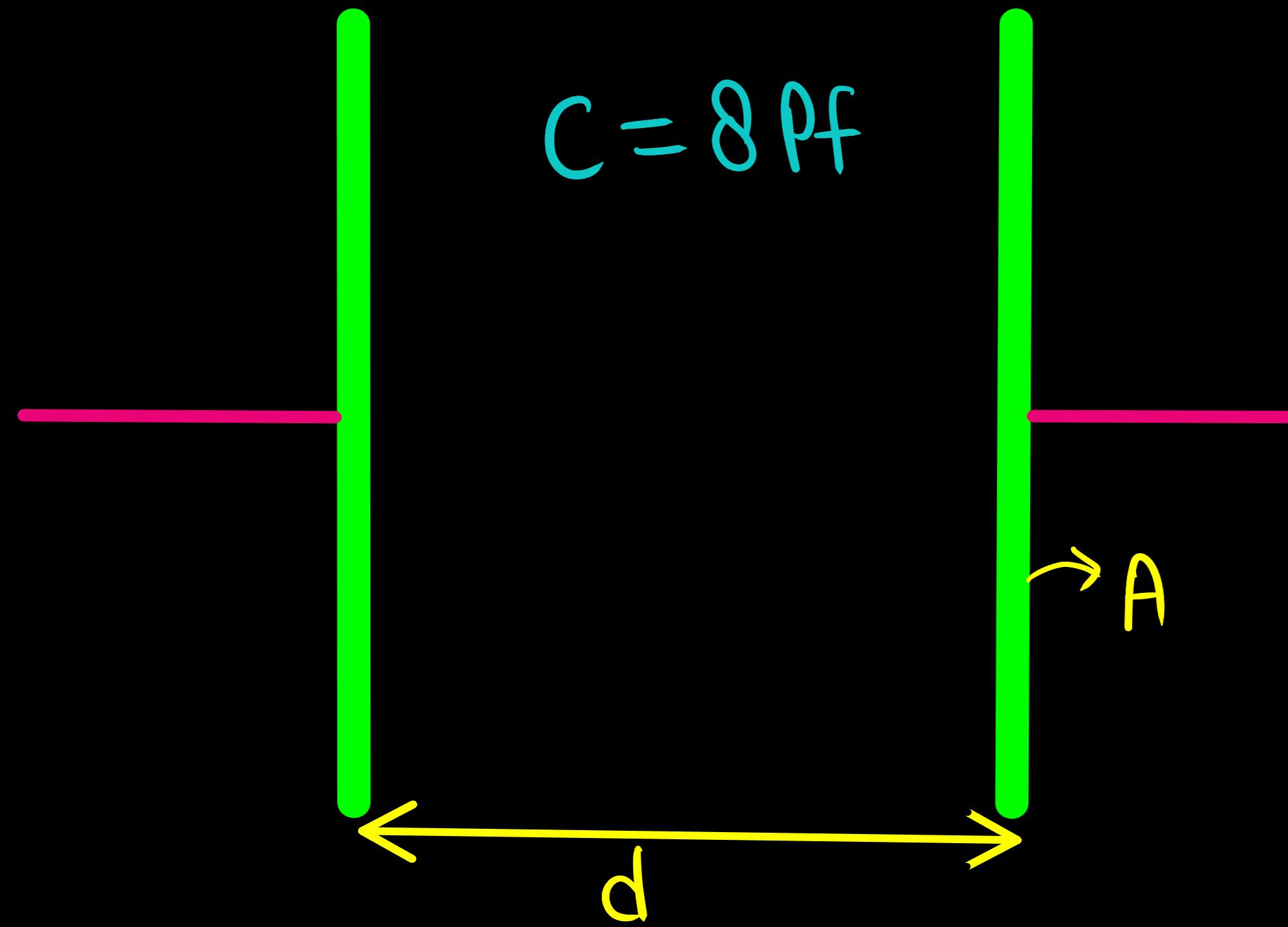2.5 A parallel plate capacitor with air between the plates has a capacitance of 8 pF ($1\text{pF} = 10^{-12} \text{ F}$). What will be the capacitance if the distance between the plates is reduced by half, and the space between them is filled with a substance of dielectric constant 6?





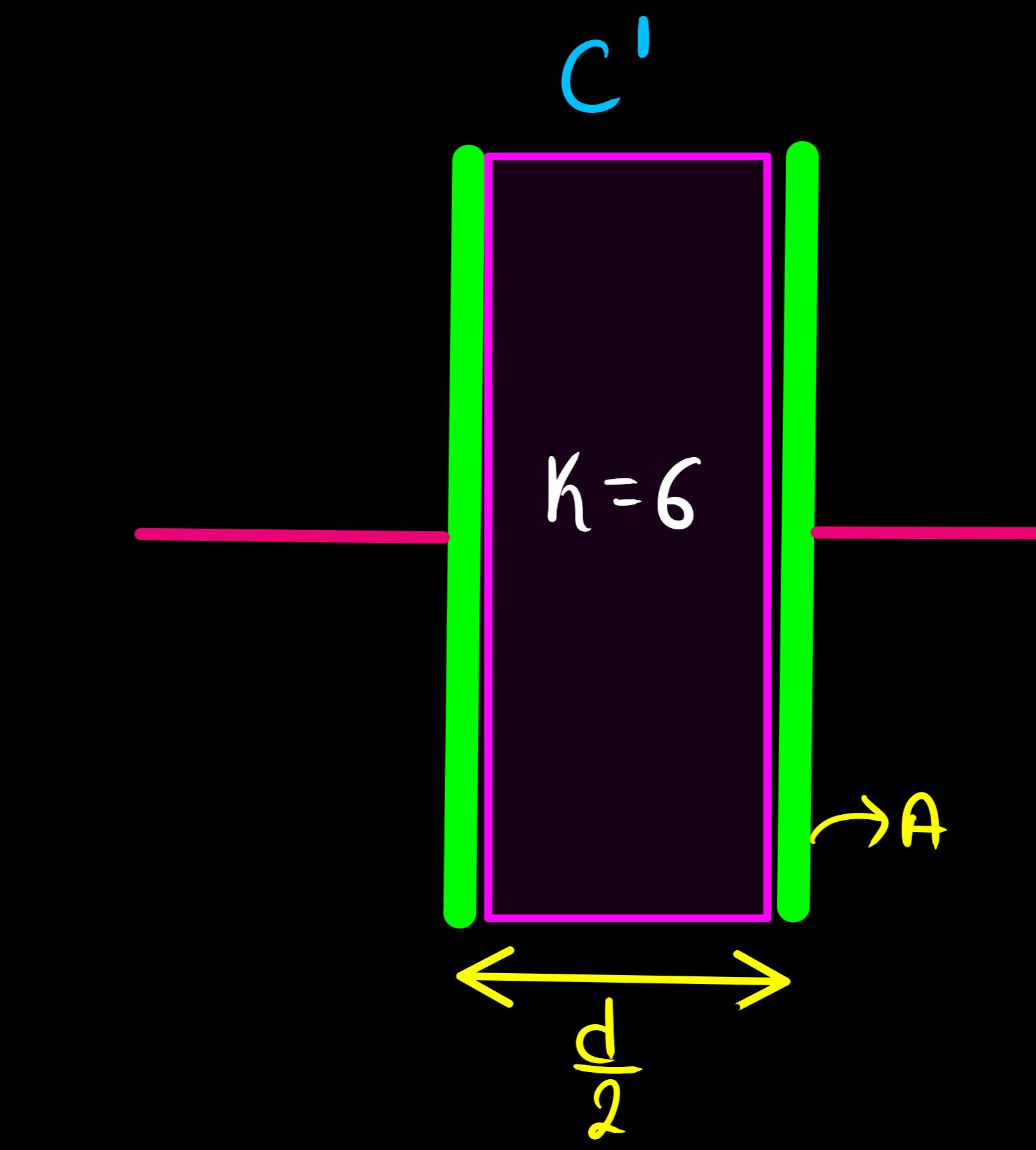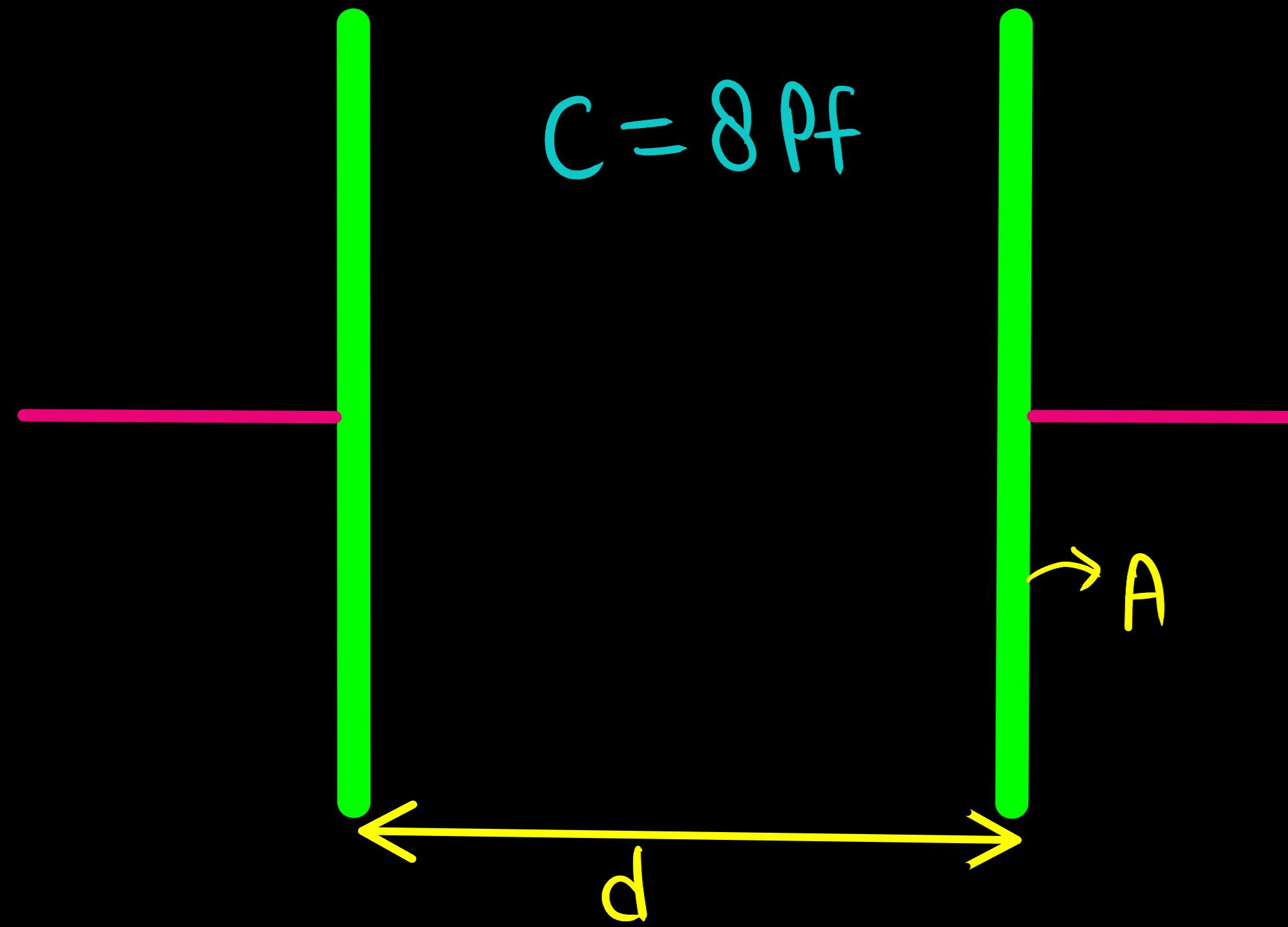2.5 A parallel plate capacitor with air between the plates has a capacitance of 8 pF ($1\text{pF} = 10^{-12} \text{ F}$). What will be the capacitance if the distance between the plates is reduced by half, and the space between them is filled with a substance of dielectric constant 6?



$$C = \frac{\epsilon_0 A}{d} = 8 \text{ pF}$$

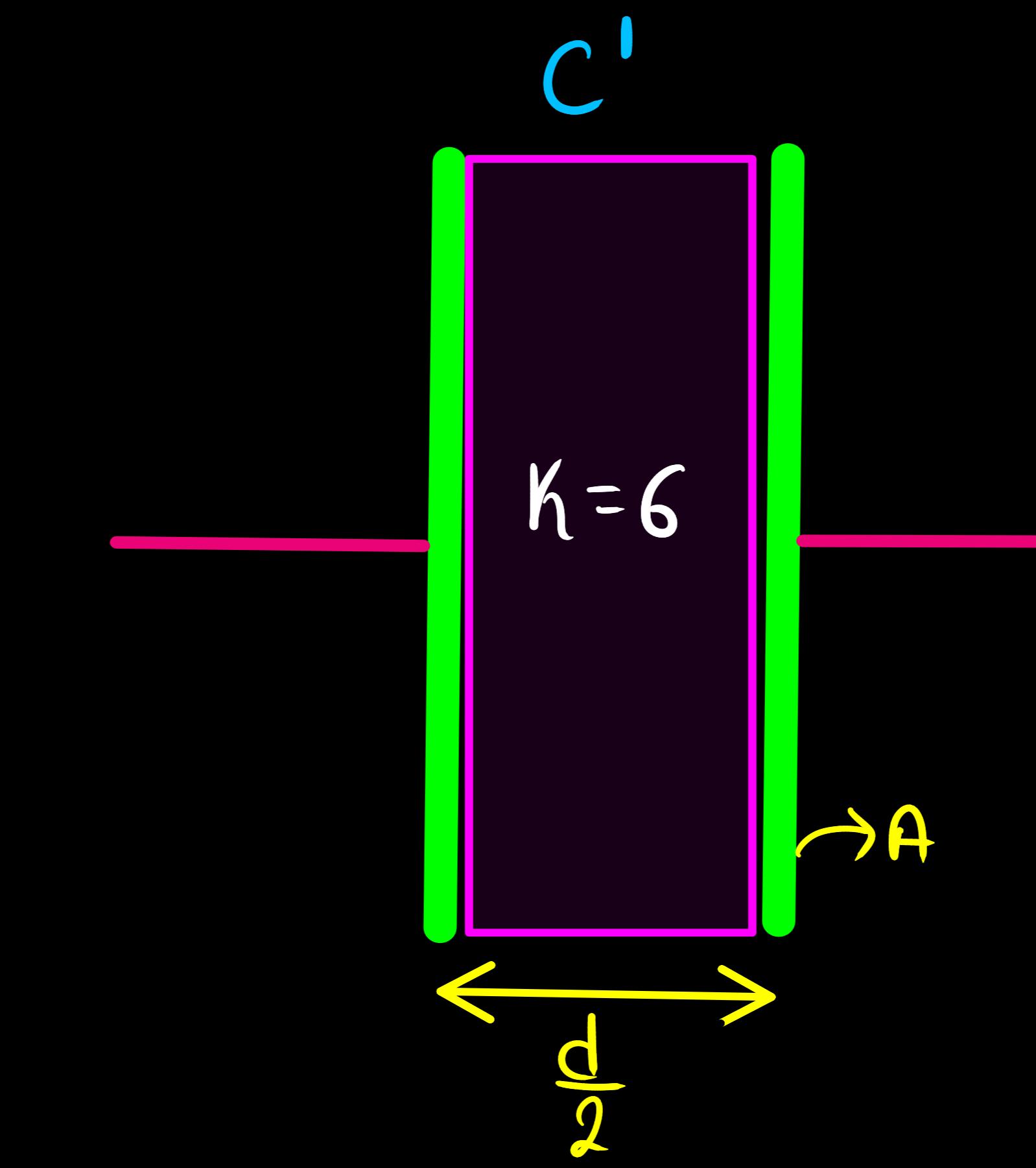
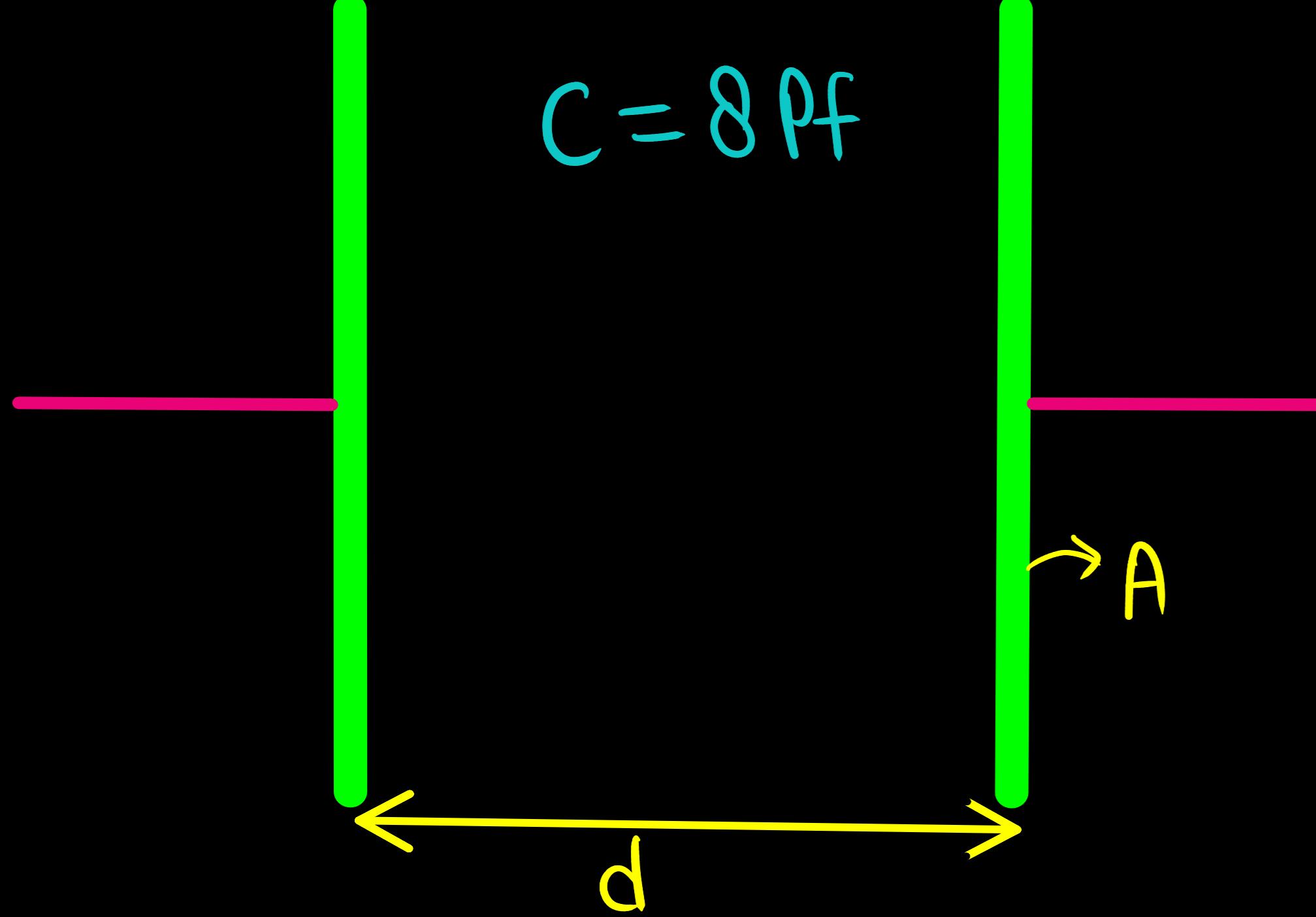
2.5 A parallel plate capacitor with air between the plates has a capacitance of 8 pF ($1\text{pF} = 10^{-12}\text{ F}$). What will be the capacitance if the distance between the plates is reduced by half, and the space between them is filled with a substance of dielectric constant 6?



$$C = \frac{\epsilon_0 A}{d} = 8 \text{ pF}$$

$$C' = \frac{K \epsilon_0 A}{\frac{d}{2}}$$

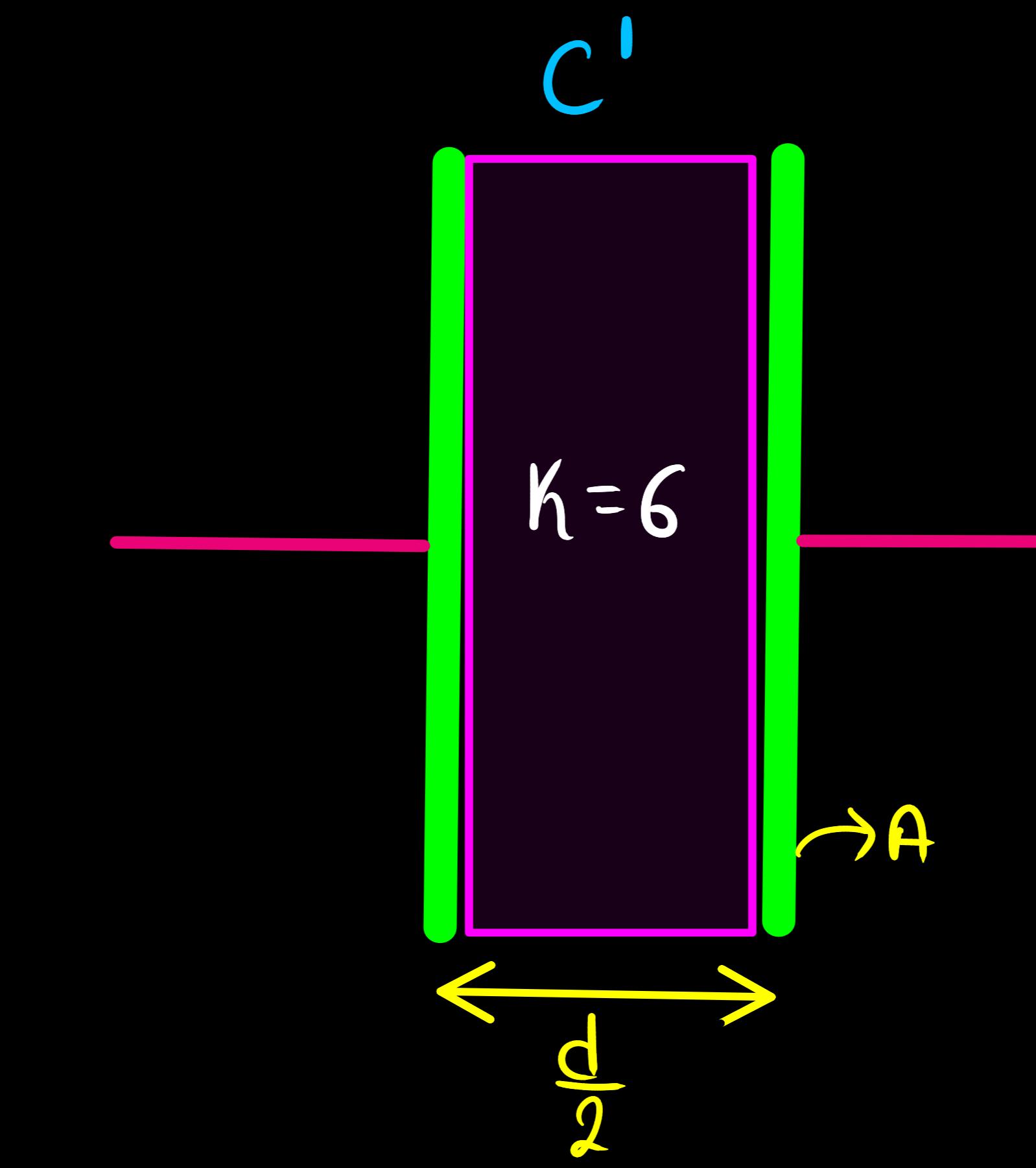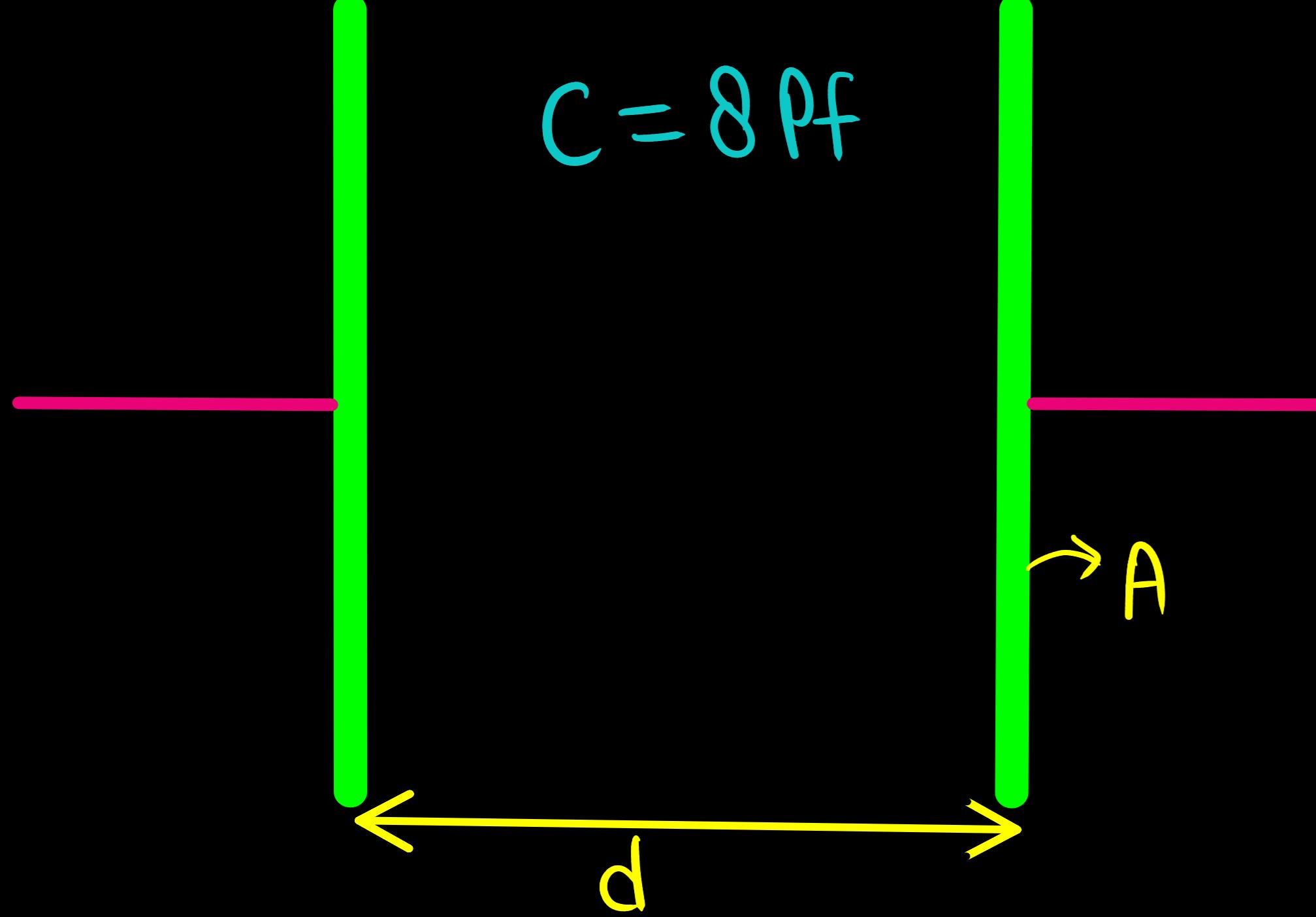2.5 A parallel plate capacitor with air between the plates has a capacitance of 8 pF ($1\text{pF} = 10^{-12}\text{ F}$). What will be the capacitance if the distance between the plates is reduced by half, and the space between them is filled with a substance of dielectric constant 6?





$$C = \frac{\epsilon_0 A}{d} = 8 \text{ pF}$$

$$C' = \frac{K \epsilon_0 A}{\frac{d}{2}}$$

$$C' = 2K \frac{\epsilon_0 A}{d}$$

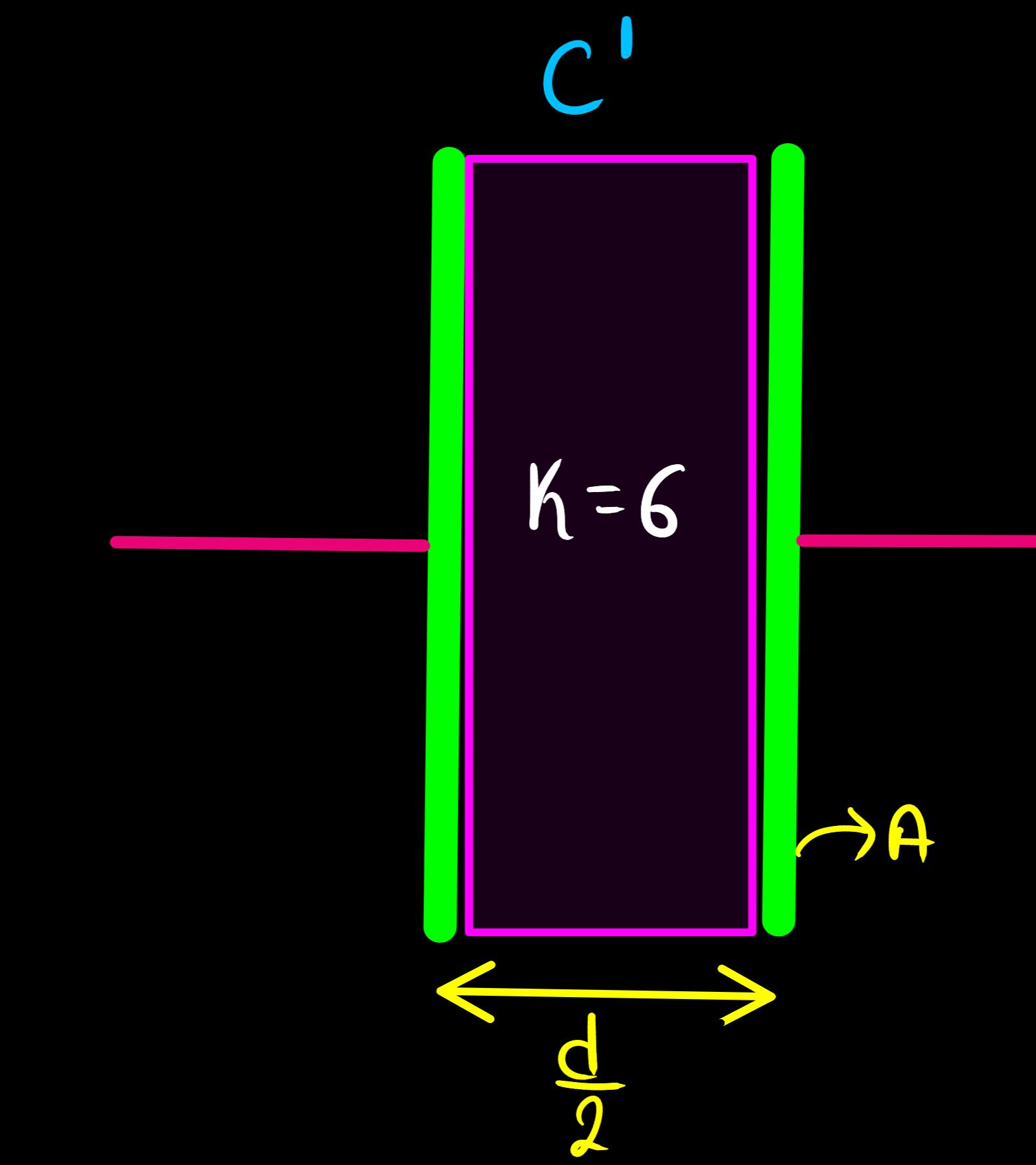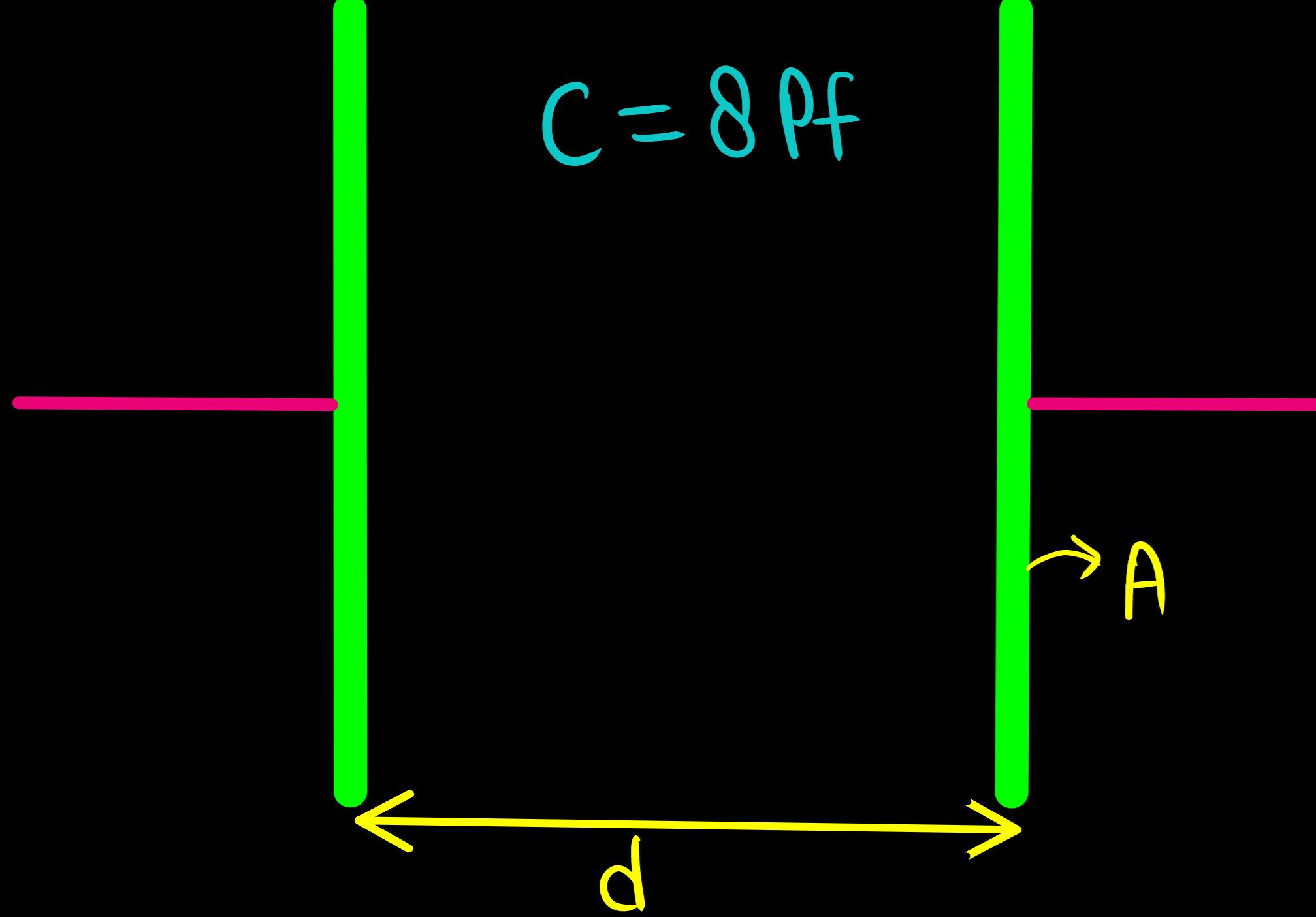2.5 A parallel plate capacitor with air between the plates has a capacitance of 8 pF ($1\text{pF} = 10^{-12} \text{ F}$). What will be the capacitance if the distance between the plates is reduced by half, and the space between them is filled with a substance of dielectric constant 6?



$$C = \frac{\epsilon_0 A}{d} = 8 \text{ pF}$$


$$C' = \frac{K \epsilon_0 A}{\frac{d}{2}}$$

$$C' = 2K \frac{\epsilon_0 A}{d}$$

$$C' = 2 \times 6 \times 8 \text{ pF} = 96 \text{ pF}$$


- 2.8** In a parallel plate capacitor with air between the plates, each plate has an area of $6 \times 10^{-3} \text{ m}^2$ and the distance between the plates is 3 mm. Calculate the capacitance of the capacitor. If this capacitor is connected to a 100 V supply, what is the charge on each plate of the capacitor?

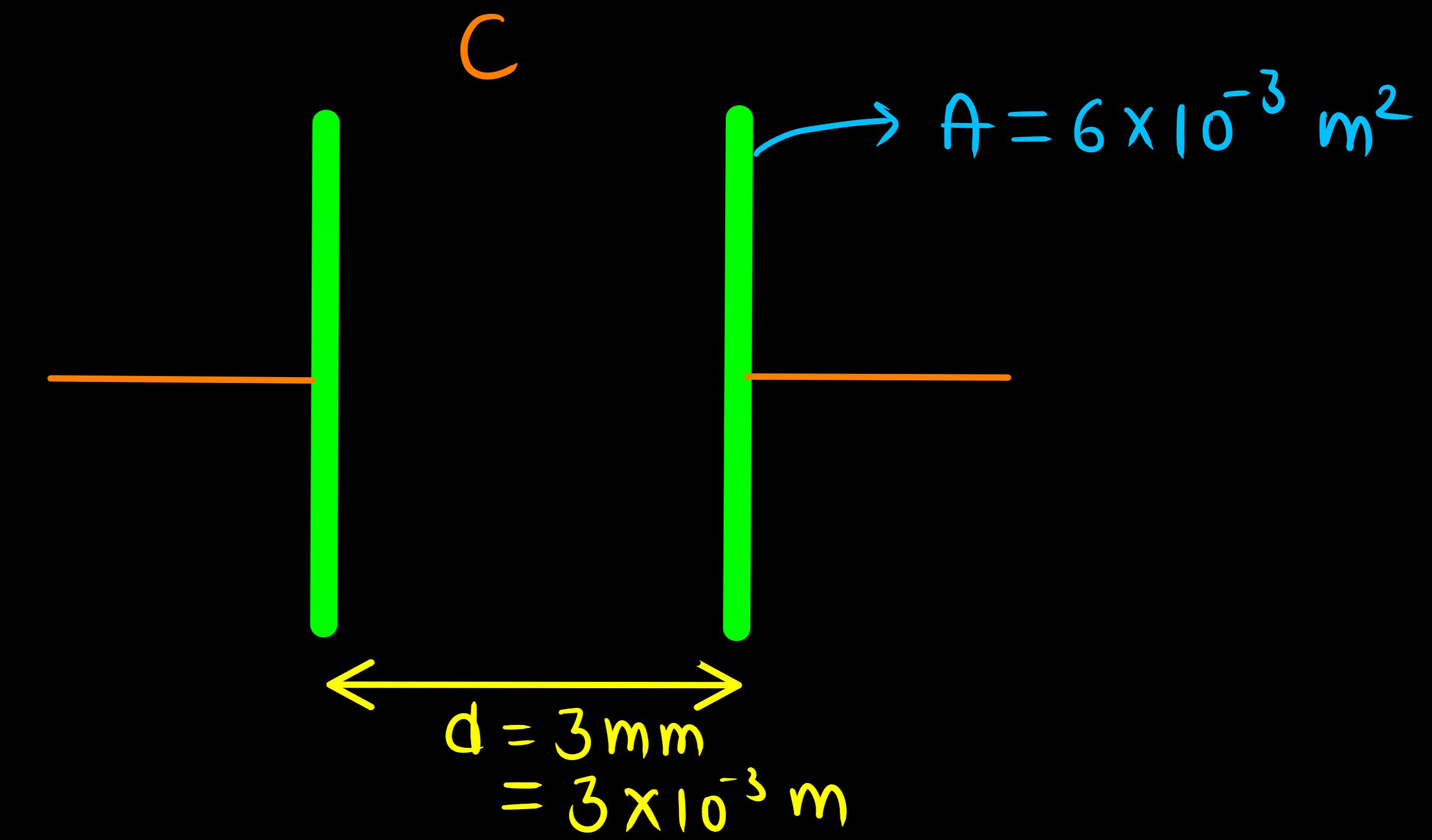- 2.8** In a parallel plate capacitor with air between the plates, each plate has an area of $6 \times 10^{-3} \text{ m}^2$ and the distance between the plates is 3 mm. Calculate the capacitance of the capacitor. If this capacitor is connected to a 100 V supply, what is the charge on each plate of the capacitor?



- 2.8** In a parallel plate capacitor with air between the plates, each plate has an area of $6 \times 10^{-3} \text{ m}^2$ and the distance between the plates is 3 mm. Calculate the capacitance of the capacitor. If this capacitor is connected to a 100 V supply, what is the charge on each plate of the capacitor?


i) $C = \frac{\epsilon_0 A}{d}$

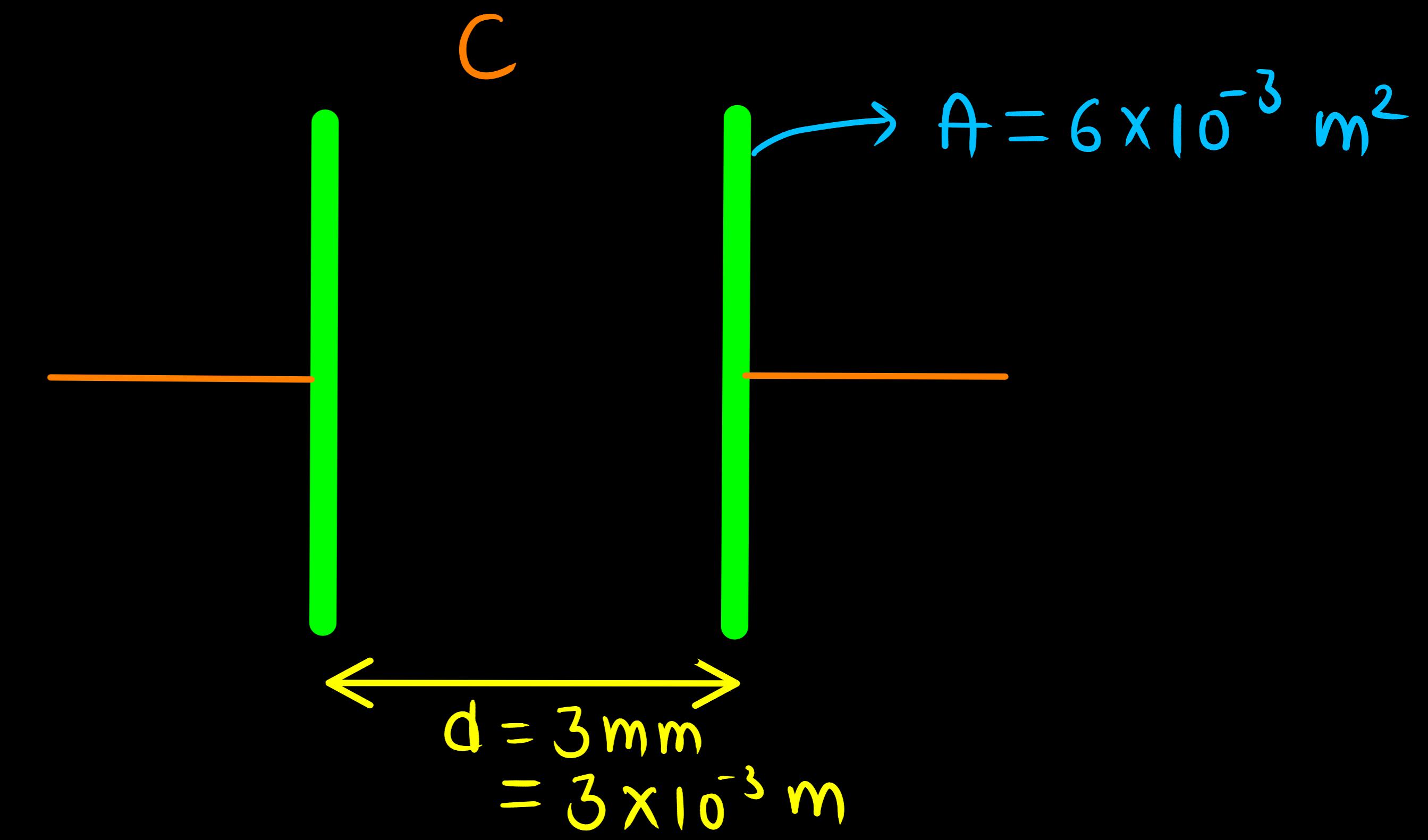

2.8 In a parallel plate capacitor with air between the plates, each plate has an area of $6 \times 10^{-3} \text{ m}^2$ and the distance between the plates is 3 mm. Calculate the capacitance of the capacitor. If this capacitor is connected to a 100 V supply, what is the charge on each plate of the capacitor?

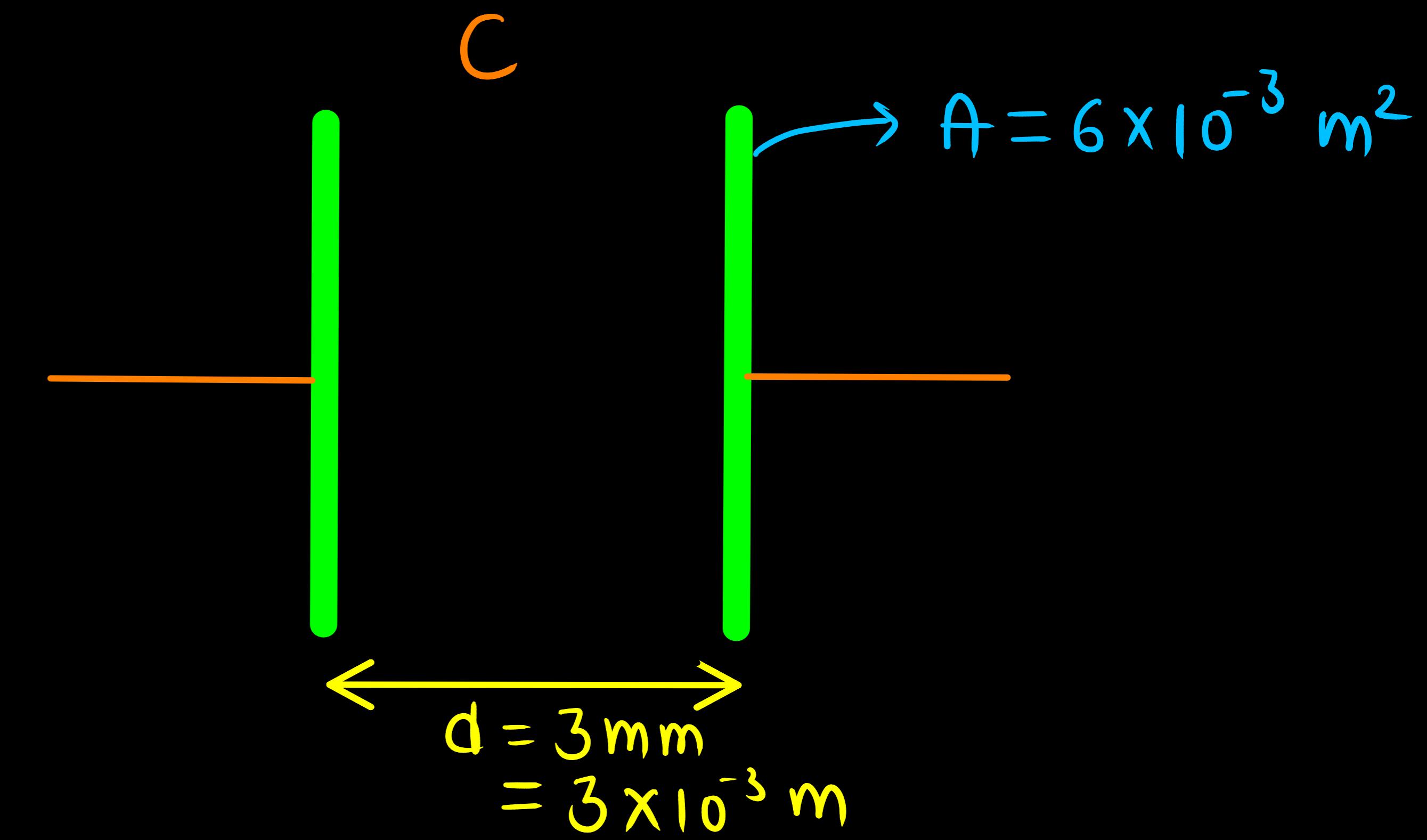i) $C = \frac{\epsilon_0 A}{d}$

$$C = \frac{8.854 \times 10^{-12} \times 6 \times 10^{-3}}{3 \times 10^{-3}}$$




2.8 In a parallel plate capacitor with air between the plates, each plate has an area of $6 \times 10^{-3} \text{ m}^2$ and the distance between the plates is 3 mm. Calculate the capacitance of the capacitor. If this capacitor is connected to a 100 V supply, what is the charge on each plate of the capacitor?

$$\text{i) } C = \frac{\epsilon_0 A}{d}$$

$$C = \frac{8.854 \times 10^{-12} \times 6 \times 10^{-3}}{3 \times 10^{-3}}$$

$$C = 17.708 \times 10^{-12} \text{ F}$$

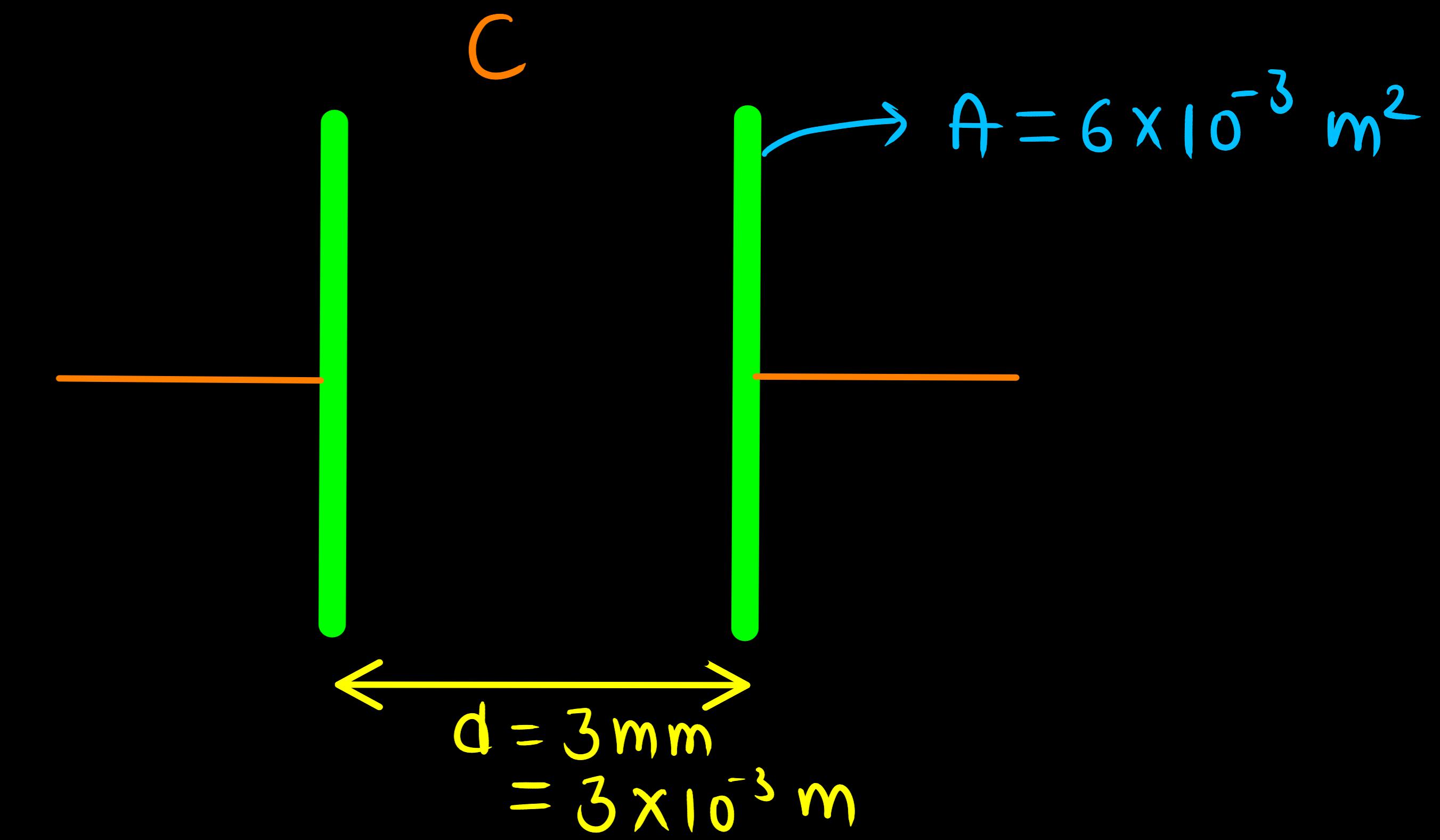


2.8 In a parallel plate capacitor with air between the plates, each plate has an area of $6 \times 10^{-3} \text{ m}^2$ and the distance between the plates is 3 mm. Calculate the capacitance of the capacitor. If this capacitor is connected to a 100 V supply, what is the charge on each plate of the capacitor?

$$\text{i) } C = \frac{\epsilon_0 A}{d}$$

$$C = \frac{8.854 \times 10^{-12} \times 6 \times 10^{-3}}{3 \times 10^{-3}}$$

$$C = 17.708 \times 10^{-12} \text{ F}$$

$$\text{ii) } Q = CV$$

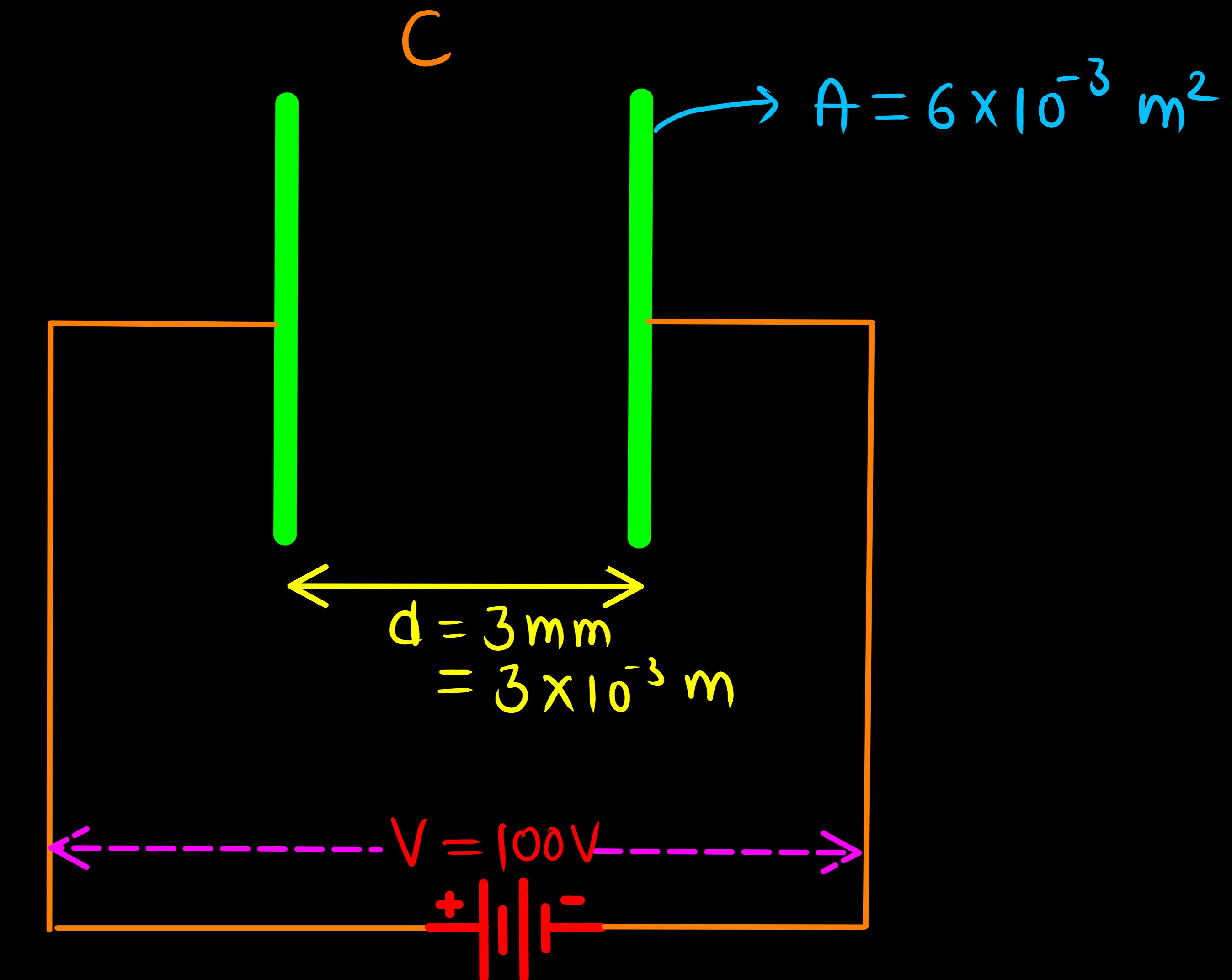

2.8 In a parallel plate capacitor with air between the plates, each plate has an area of $6 \times 10^{-3} \text{ m}^2$ and the distance between the plates is 3 mm. Calculate the capacitance of the capacitor. If this capacitor is connected to a 100 V supply, what is the charge on each plate of the capacitor?

$$\text{i) } C = \frac{\epsilon_0 A}{d}$$


$$C = \frac{8.854 \times 10^{-12} \times 6 \times 10^{-3}}{3 \times 10^{-3}}$$

$$C = 17.708 \times 10^{-12} \text{ F}$$

$$\text{ii) } Q = CV$$

$$Q = 17.708 \times 10^{-12} \times 100 \text{ C}$$

$$Q = 17.708 \times 10^{-10} \text{ C}$$

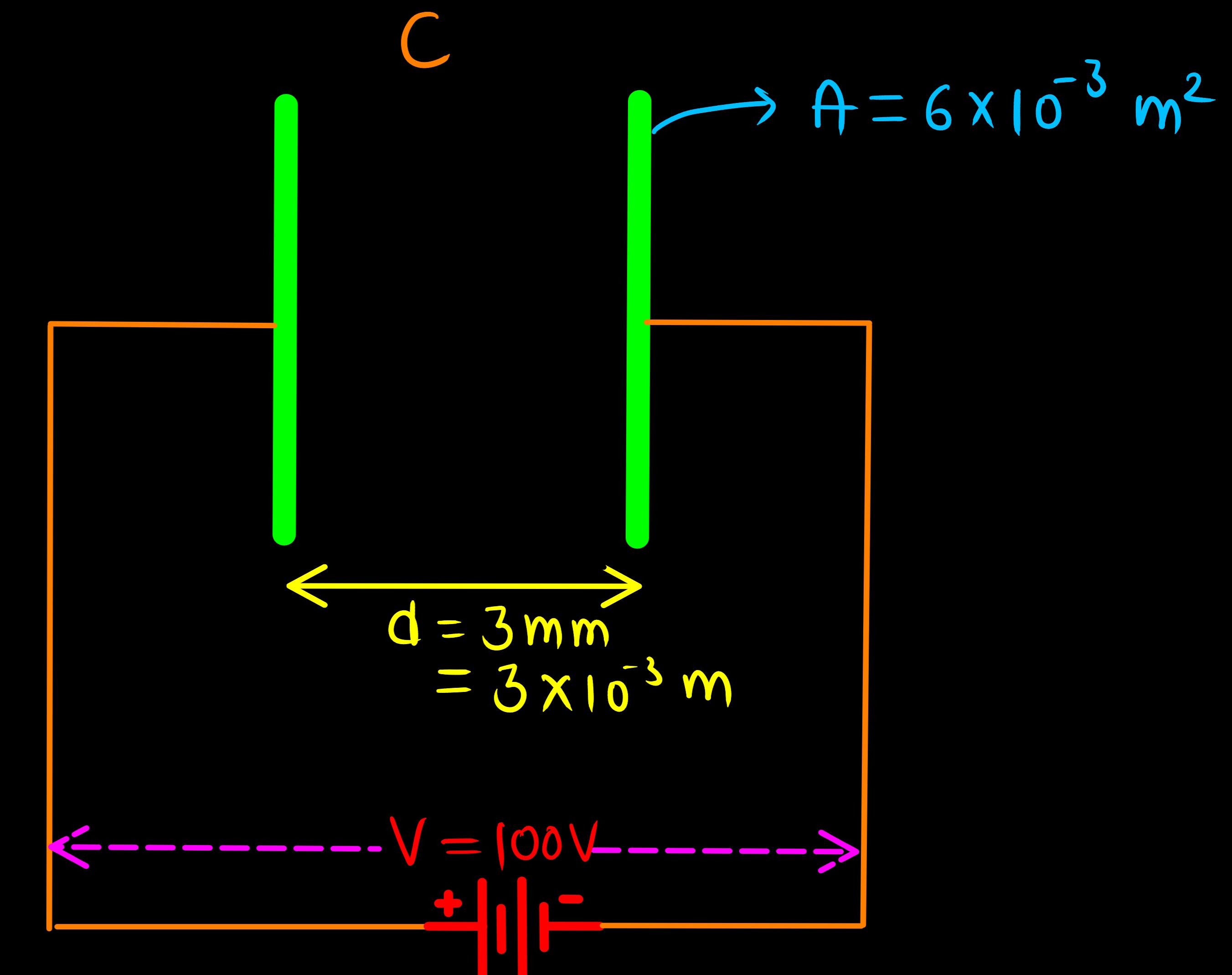


2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,

- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.

2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,

- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.


a)

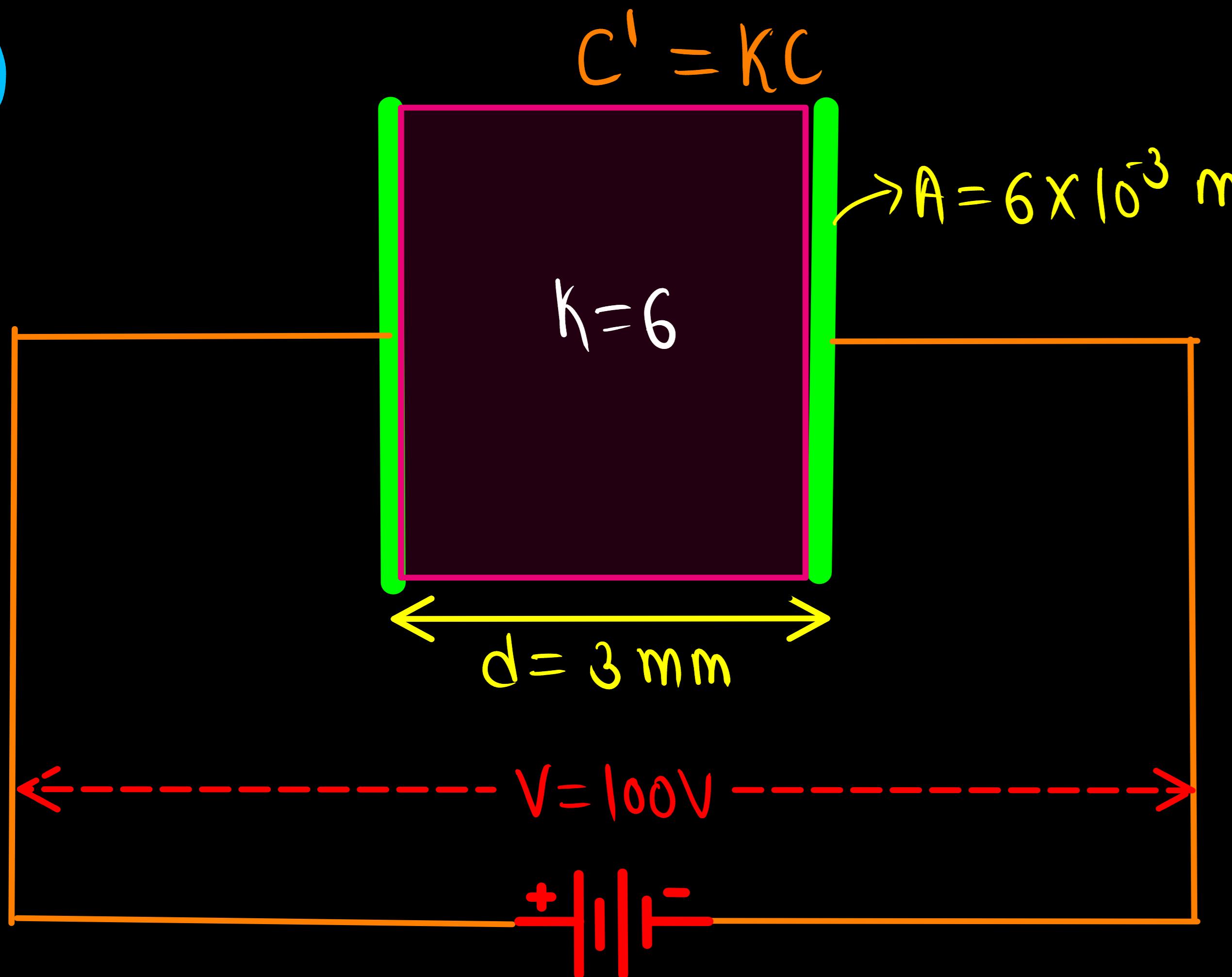

2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,

- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.

a)

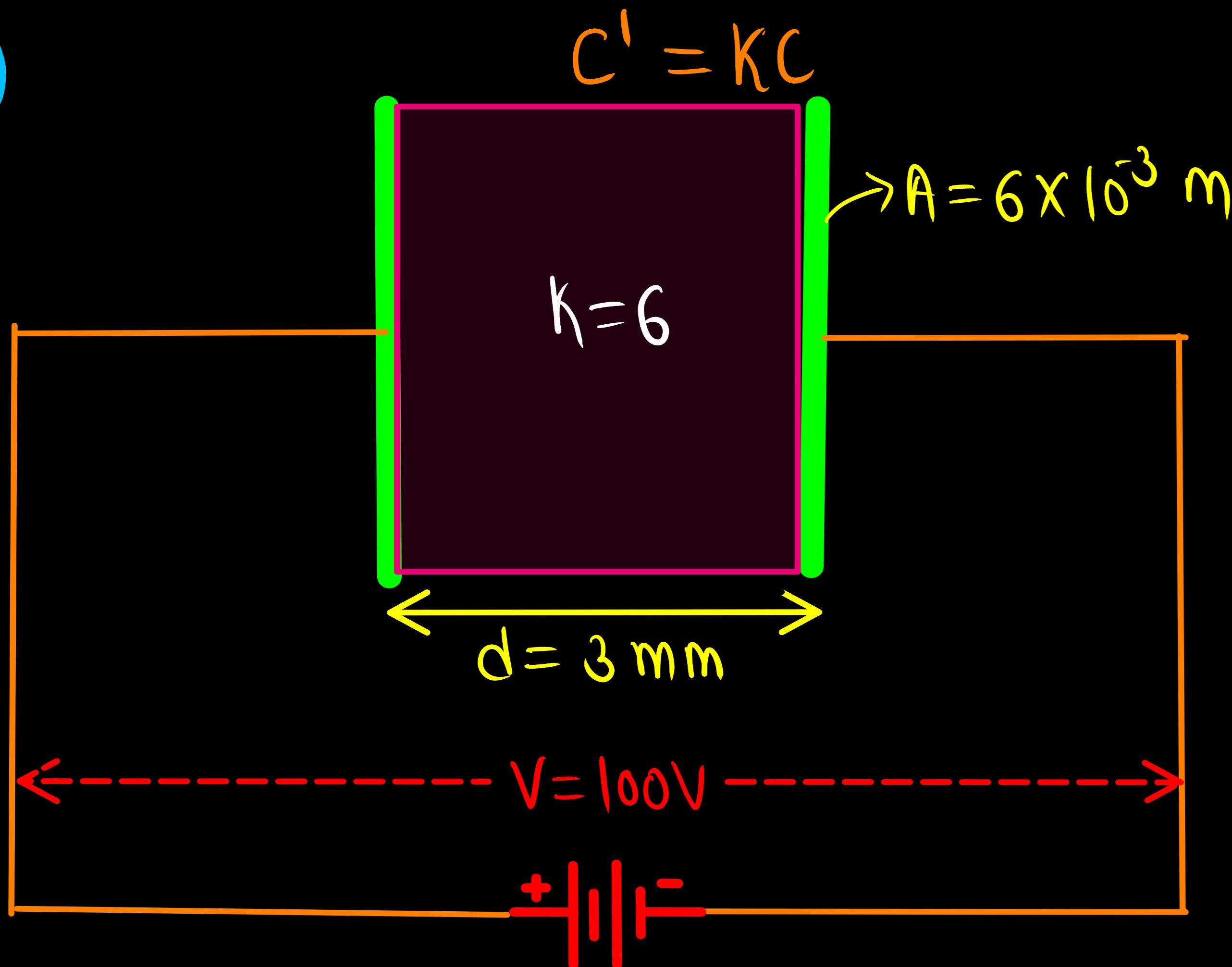


* when Voltage supply remained connected & dielectric is inserted.
 $V' = V$ remains constant

2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,

- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.

a)

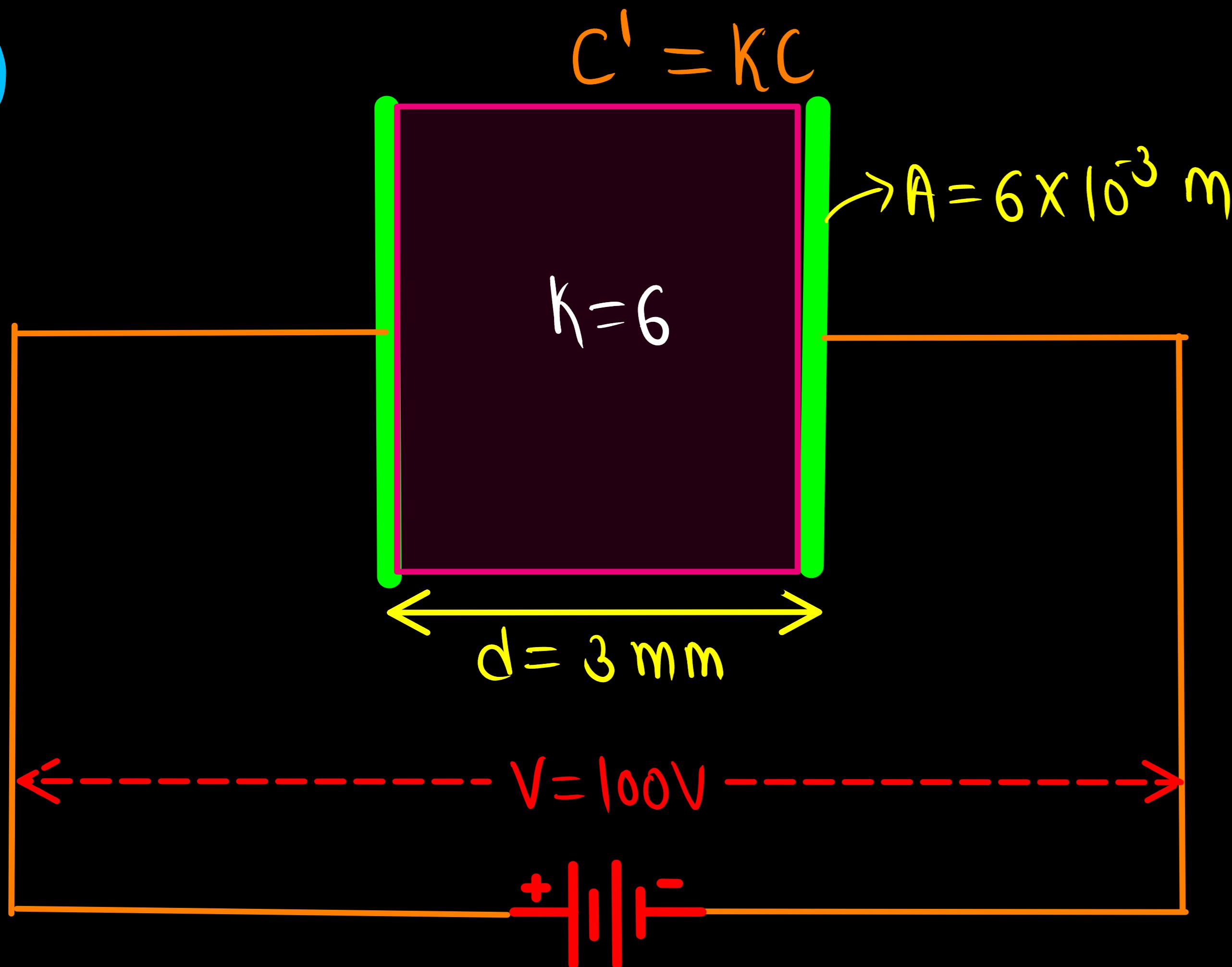


$$C' = kC$$

$$A = 6 \times 10^{-3} \text{ m}^2$$

$$k = 6$$

$$d = 3 \text{ mm}$$

$$V = 100V$$

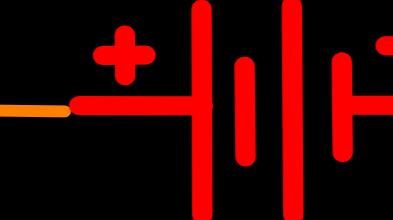

* When Voltage supply remained connected & dielectric is inserted.


$$V' = V \text{ remains constant}$$

$$C' = kC \text{ Capacitance increases}$$

2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,

- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.

a)

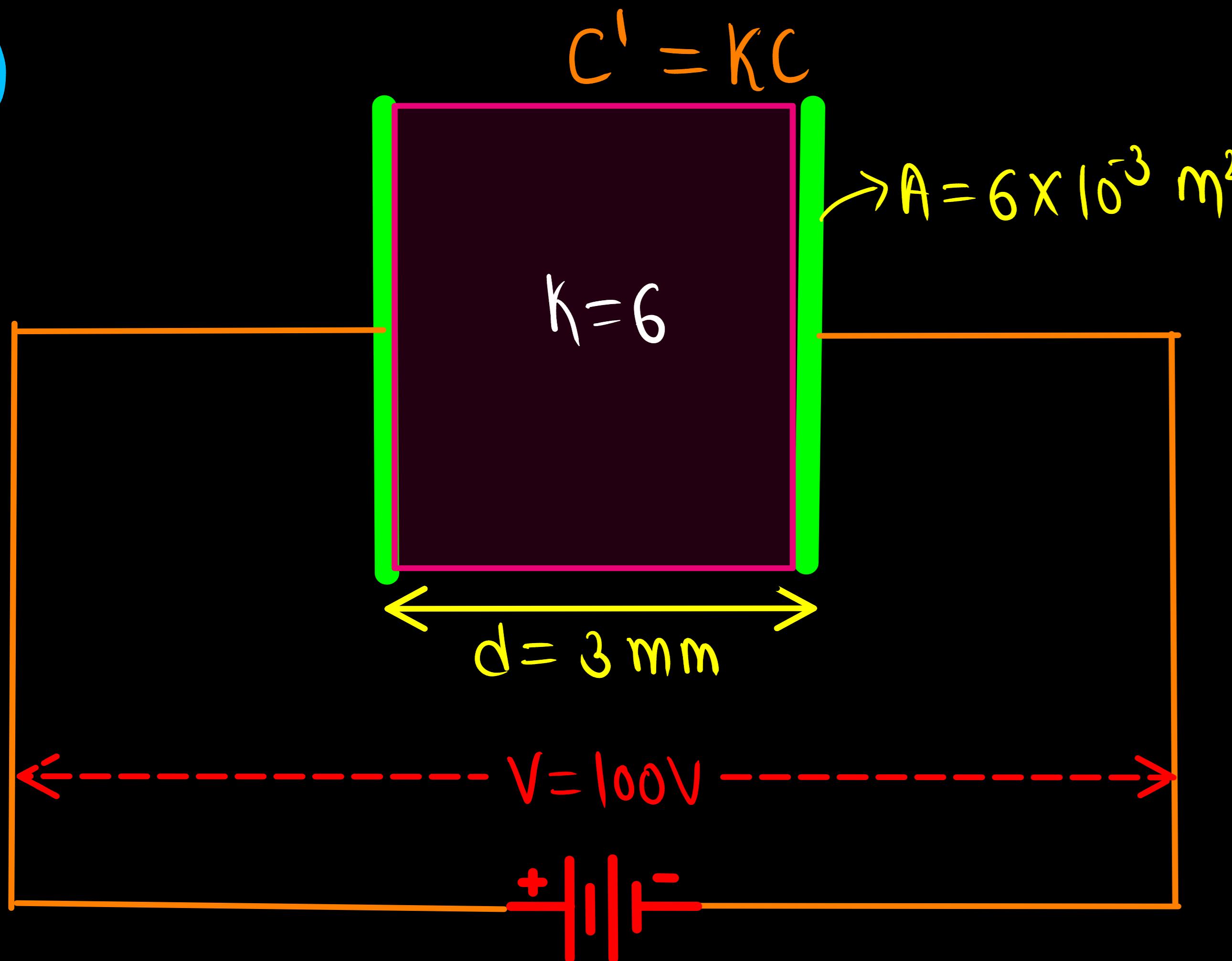

* When Voltage supply remained connected & dielectric is inserted.

$V' = V$ remains constant


$C' = kC$ Capacitance increases

$Q' = C'V$

2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,

- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.

a)

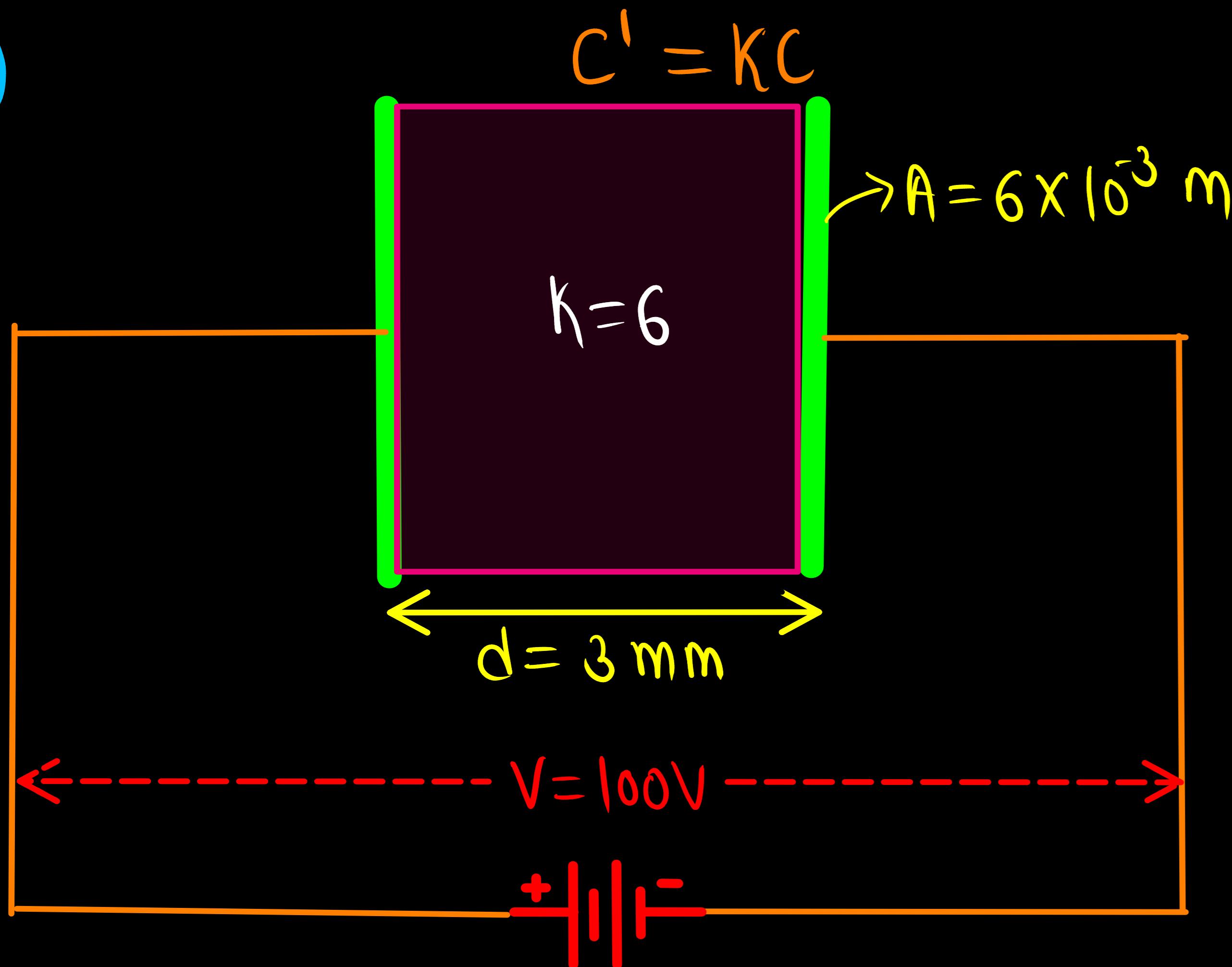

* When Voltage supply remained connected & dielectric is inserted.

$$V' = V \text{ remains constant}$$

$C' = kC$ Capacitance increases


$$Q' = C'V$$

$$Q' = kCV$$

2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,

- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.

a)

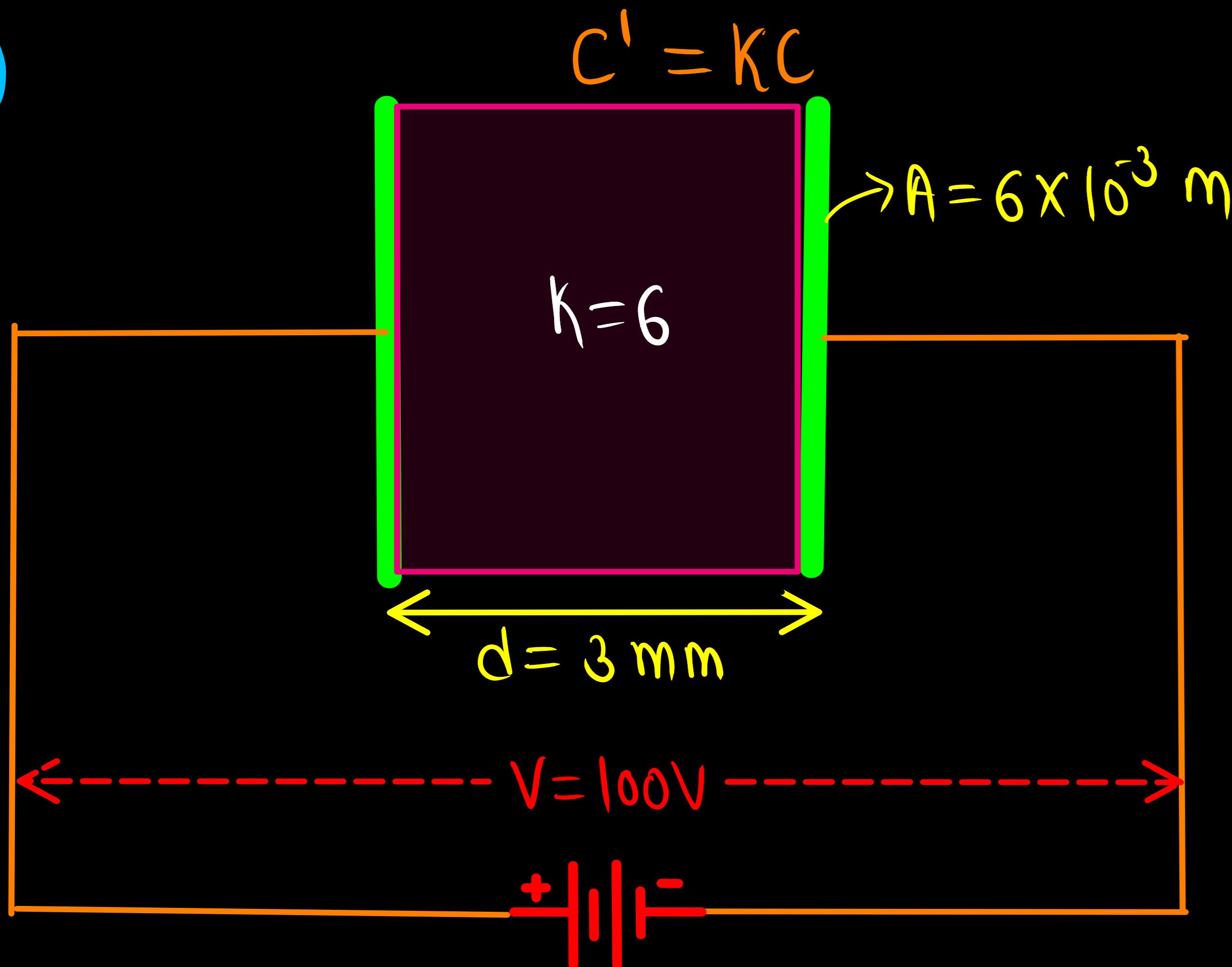

$$C' = kC$$

$$A = 6 \times 10^{-3} \text{ m}^2$$

$$k = 6$$

$$d = 3 \text{ mm}$$

$$V = 100V$$

$$+ || -$$

* When Voltage supply remained connected & dielectric is inserted.

$$V' = V \text{ remains constant}$$

$$C' = kC \quad \text{Capacitance increases}$$

$$Q' = C'V$$


$$Q' = kCV$$

$$Q' = kQ \rightarrow \text{Capacitance increases}$$

2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,

- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.

a)

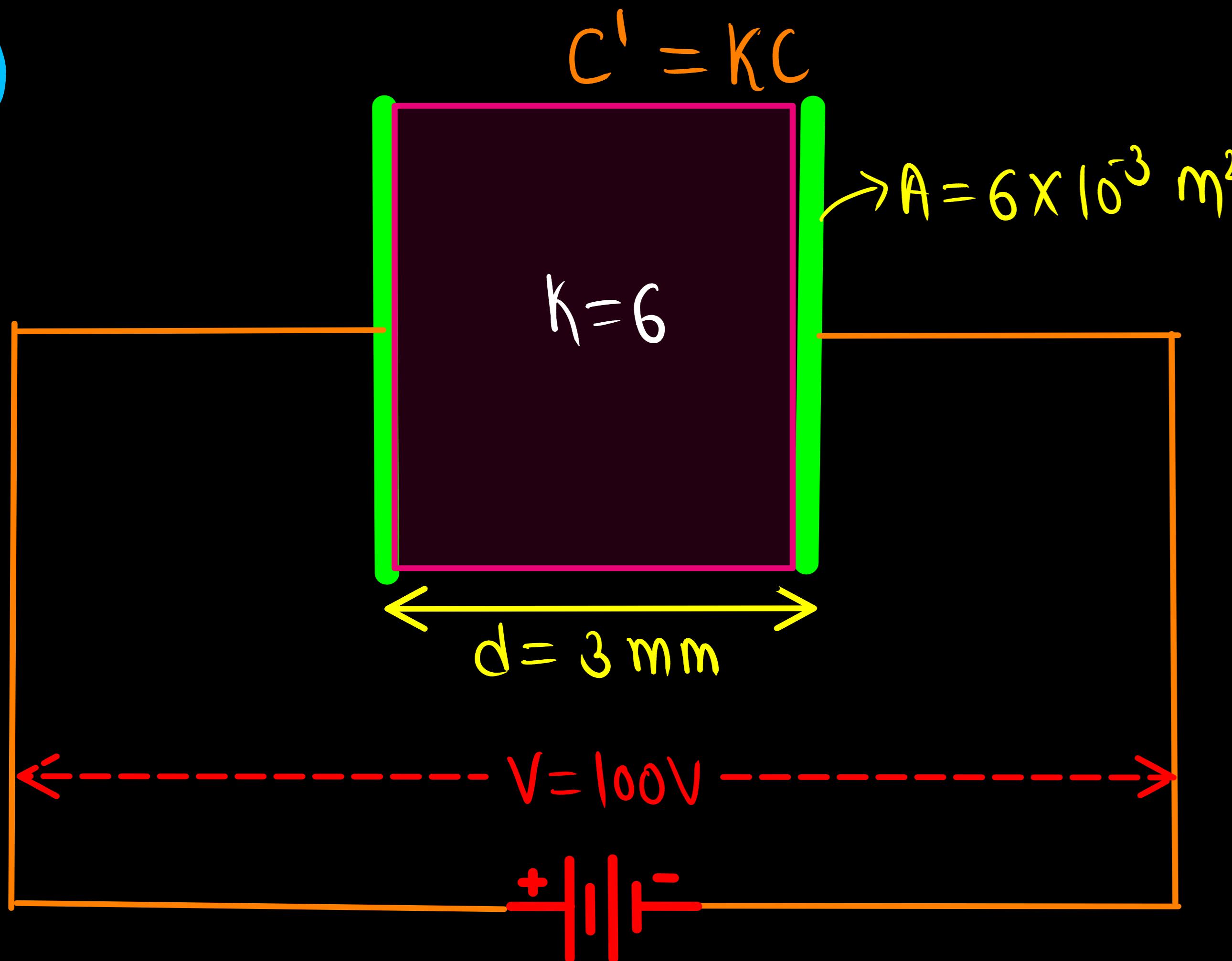


* When Voltage supply remained connected & dielectric is inserted.
 $V' = V$ remains constant
 $C' = kC$ Capacitance increases
 $Q' = C'V$
 $Q' = kQ$ \rightarrow Capacitance increases
from previous question $Q = 17.708 \times 10^{-10} \text{ C}$

2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,

- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.

a)

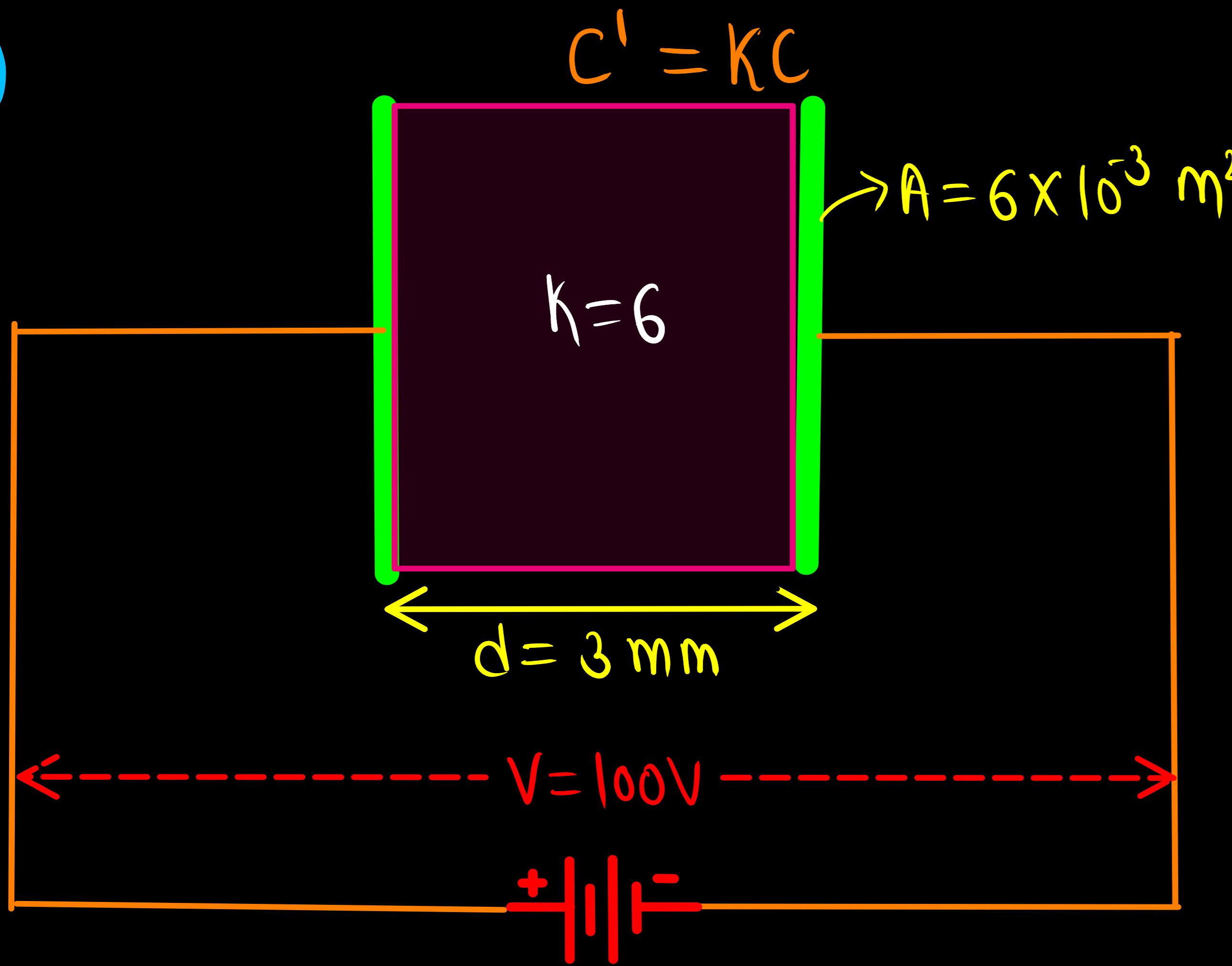


* When Voltage supply remained connected & dielectric is inserted.
 $V' = V$ remains constant
 $C' = kC$ Capacitance increases
 $Q' = C'V$
 $Q' = kCV$
 $Q' = kQ \rightarrow$ Capacitance increases
from previous question $Q = 17.708 \times 10^{-10} \text{ C}$
 $Q' = 6 \times 17.708 \times 10^{-10} \text{ C}$

2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,

- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.

a)

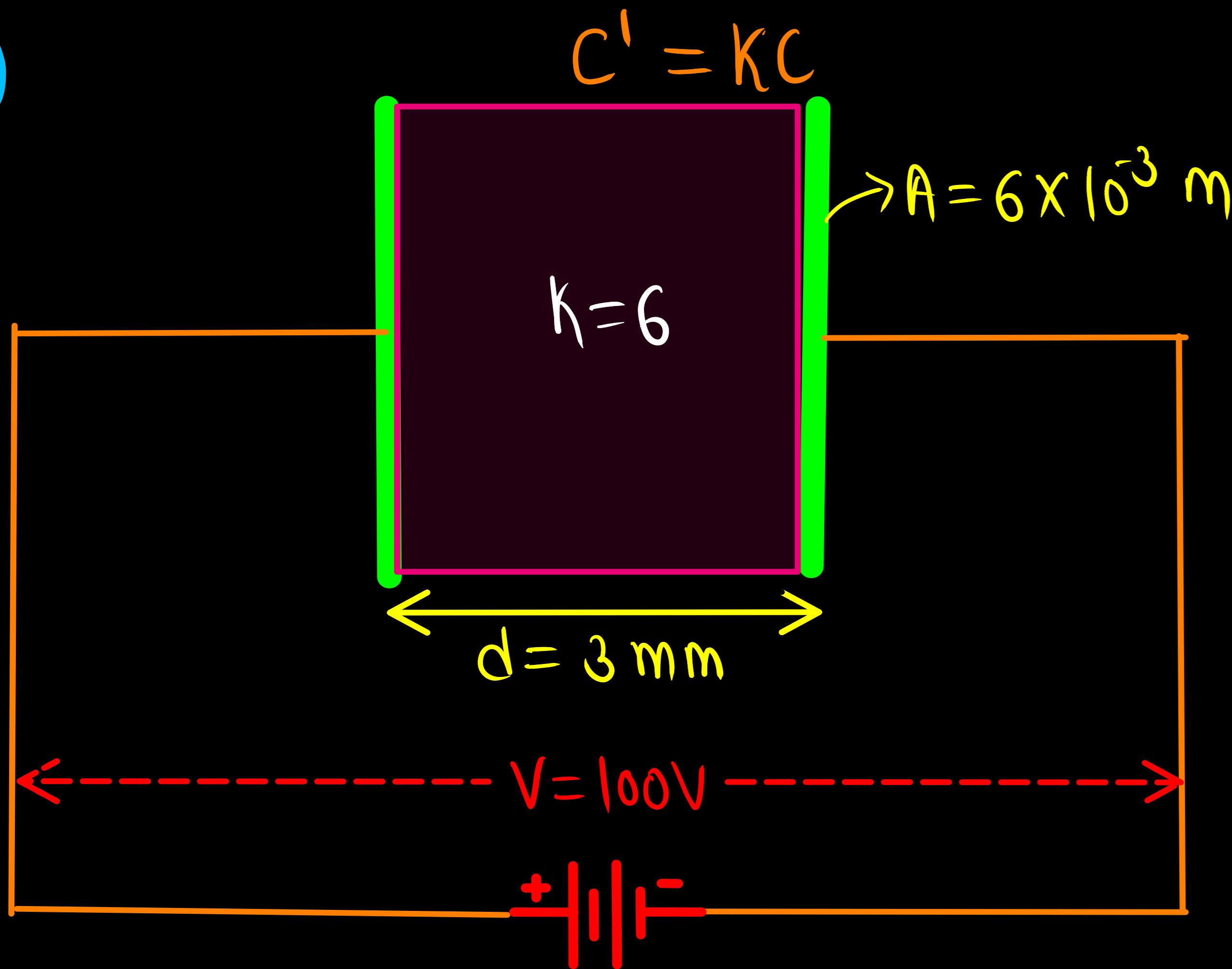


* When Voltage supply remained connected & dielectric is inserted.
 $V' = V$ remains constant
 $C' = kC$ Capacitance increases
 $Q' = C'V$
 $Q' = kCV$
 $Q' = kQ$ → Capacitance increases
from previous question $Q = 17.708 \times 10^{-10} \text{ C}$
 $Q' = 6 \times 17.708 \times 10^{-10} \text{ C}$
 $Q' = 106.248 \times 10^{-10} \text{ C}$

2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,


- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.

b)

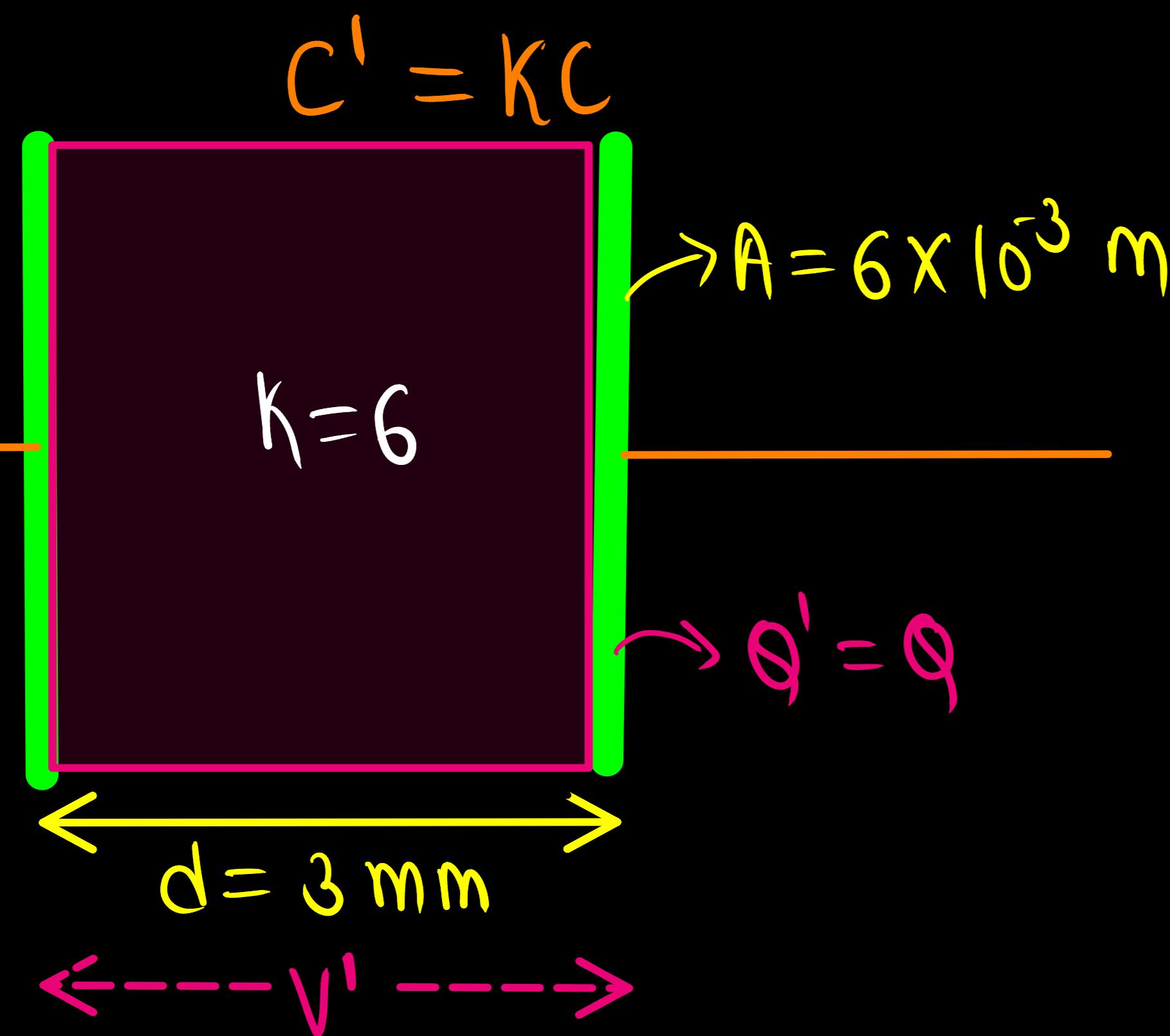

2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,

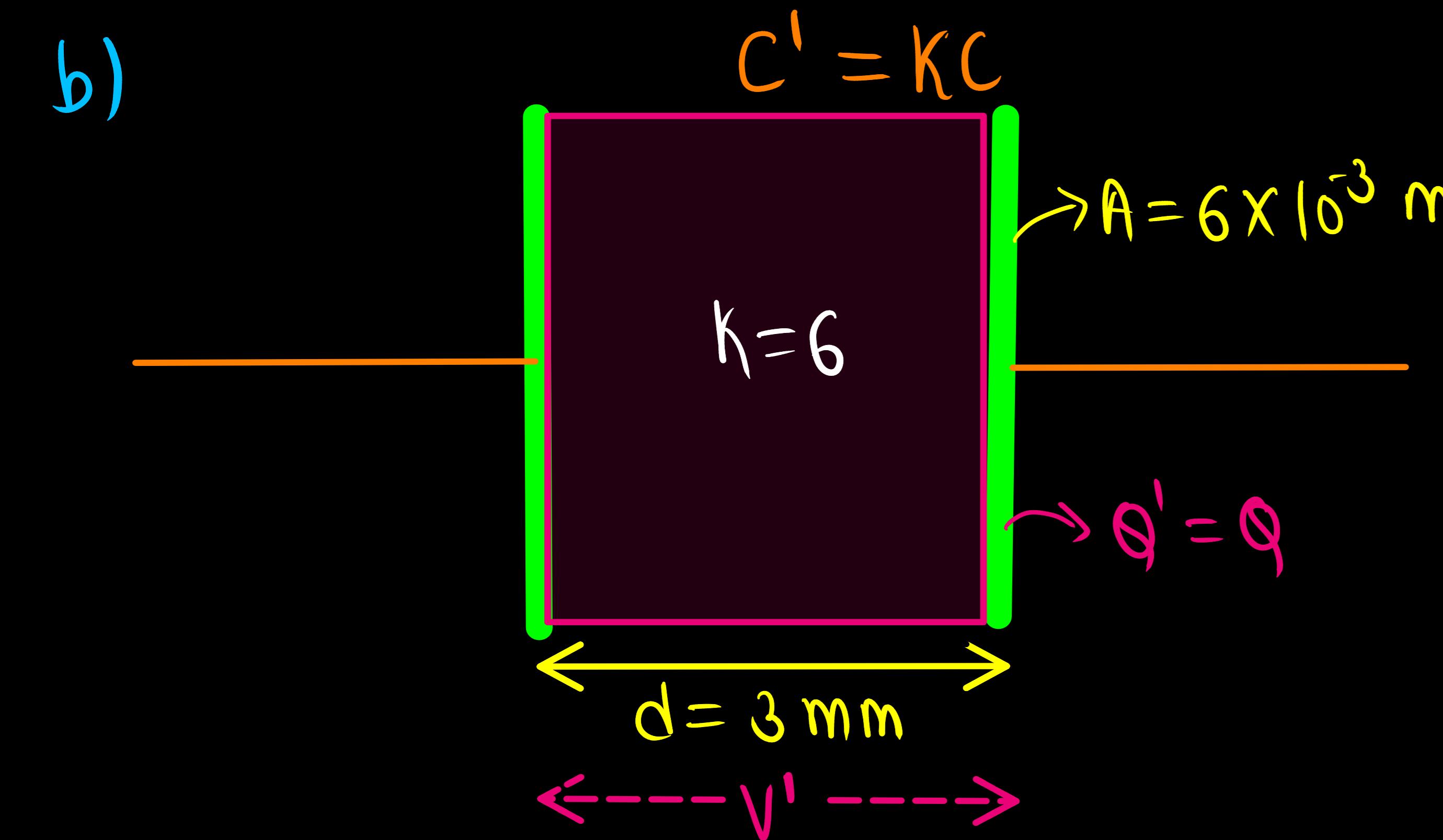
- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.



* When dielectric is inserted after the supply was disconnected.
 $Q' = Q$ → Charge on Capacitor plate remains constant

2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,

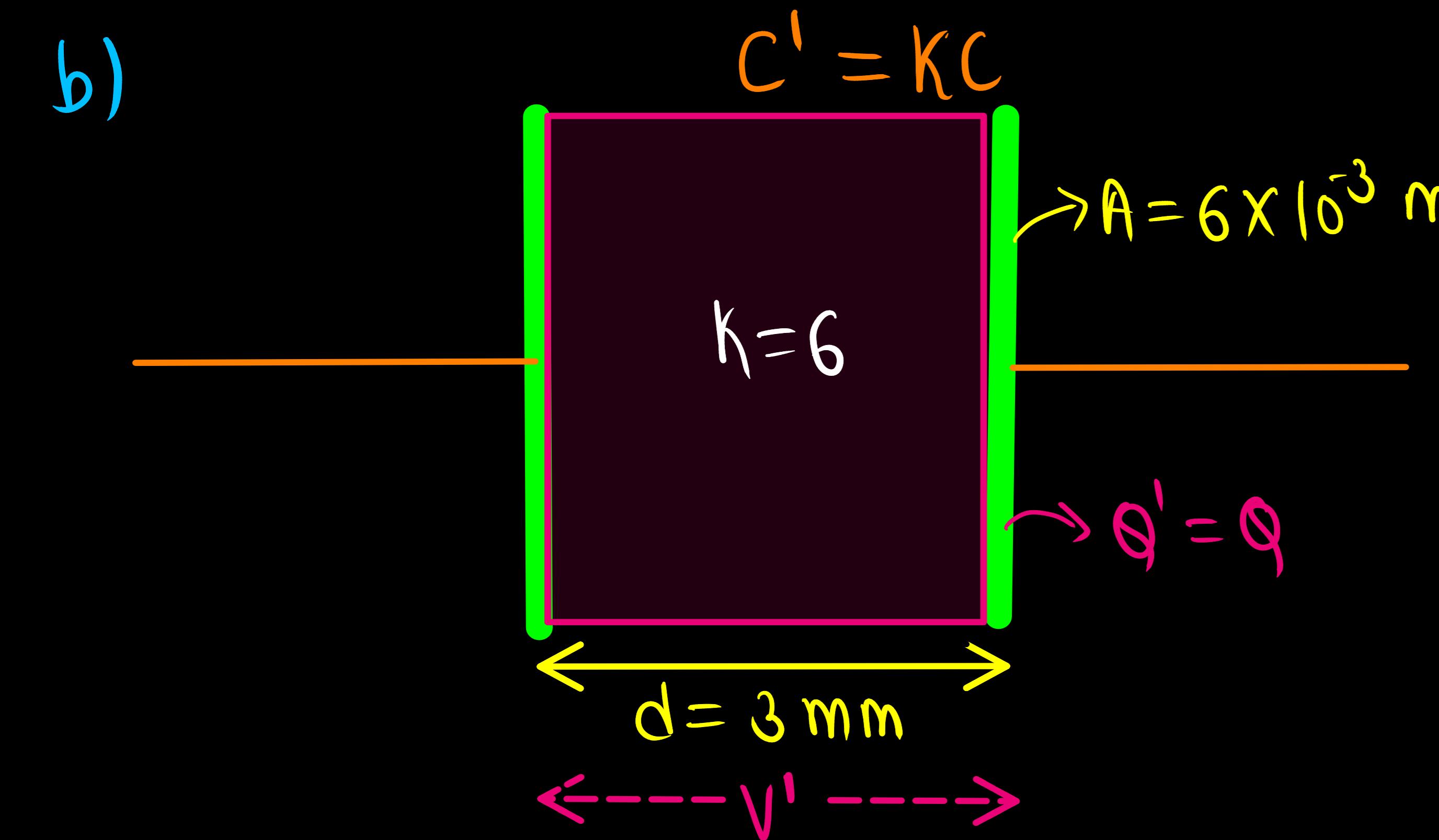- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.




* When dielectric is inserted after the supply was disconnected.

$$Q' = Q \rightarrow \text{Charge on Capacitor plate remains constant}$$
$$C' = KC \rightarrow \text{Capacitance increases}$$

2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,

- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.

b)

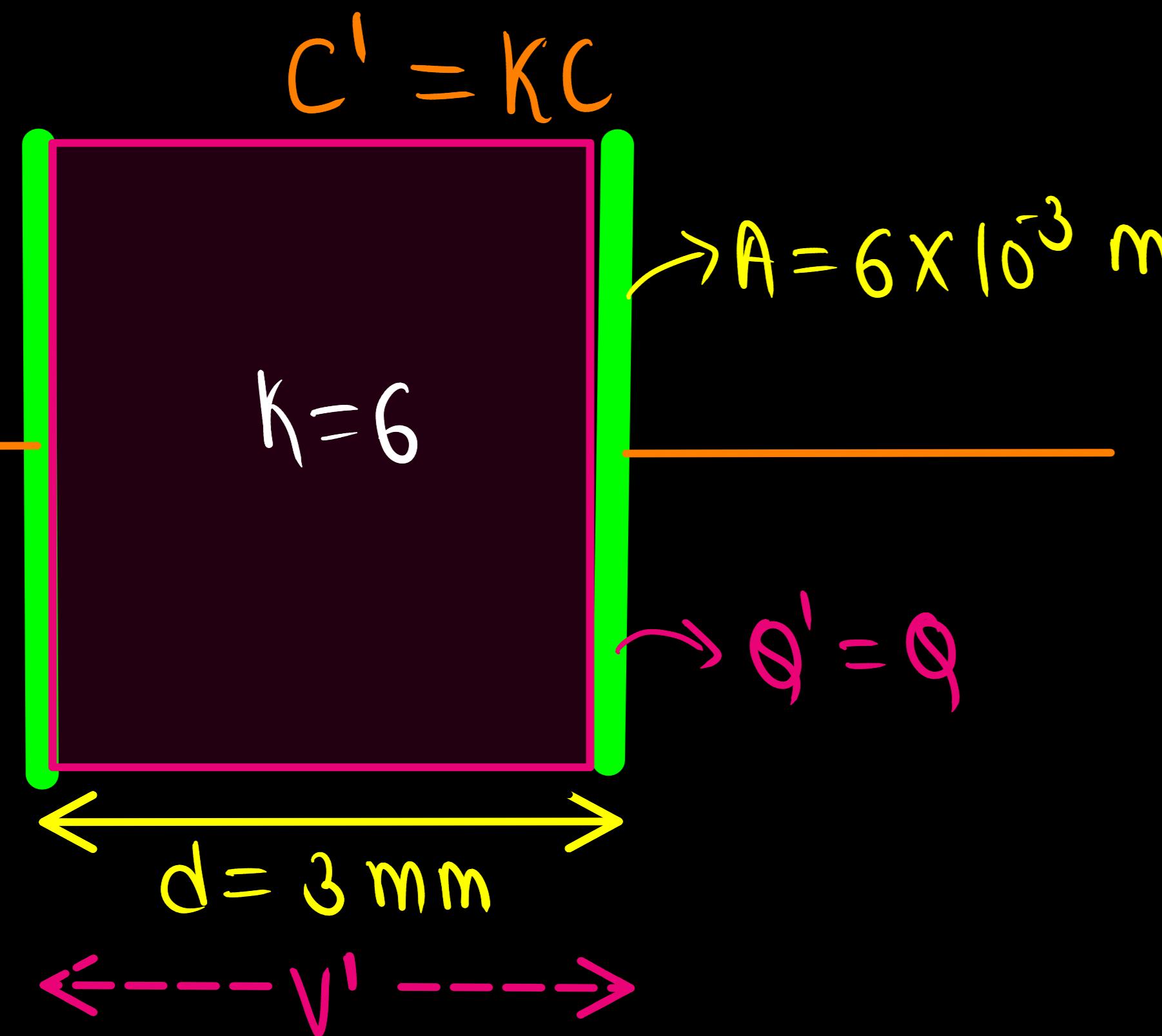

* When dielectric is inserted after the supply was disconnected.

$Q' = Q$ → Charge on Capacitor plate remains constant


$C' = KC$ → Capacitance increases

$$V' = \frac{Q'}{C'}$$

2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,

- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.

b)

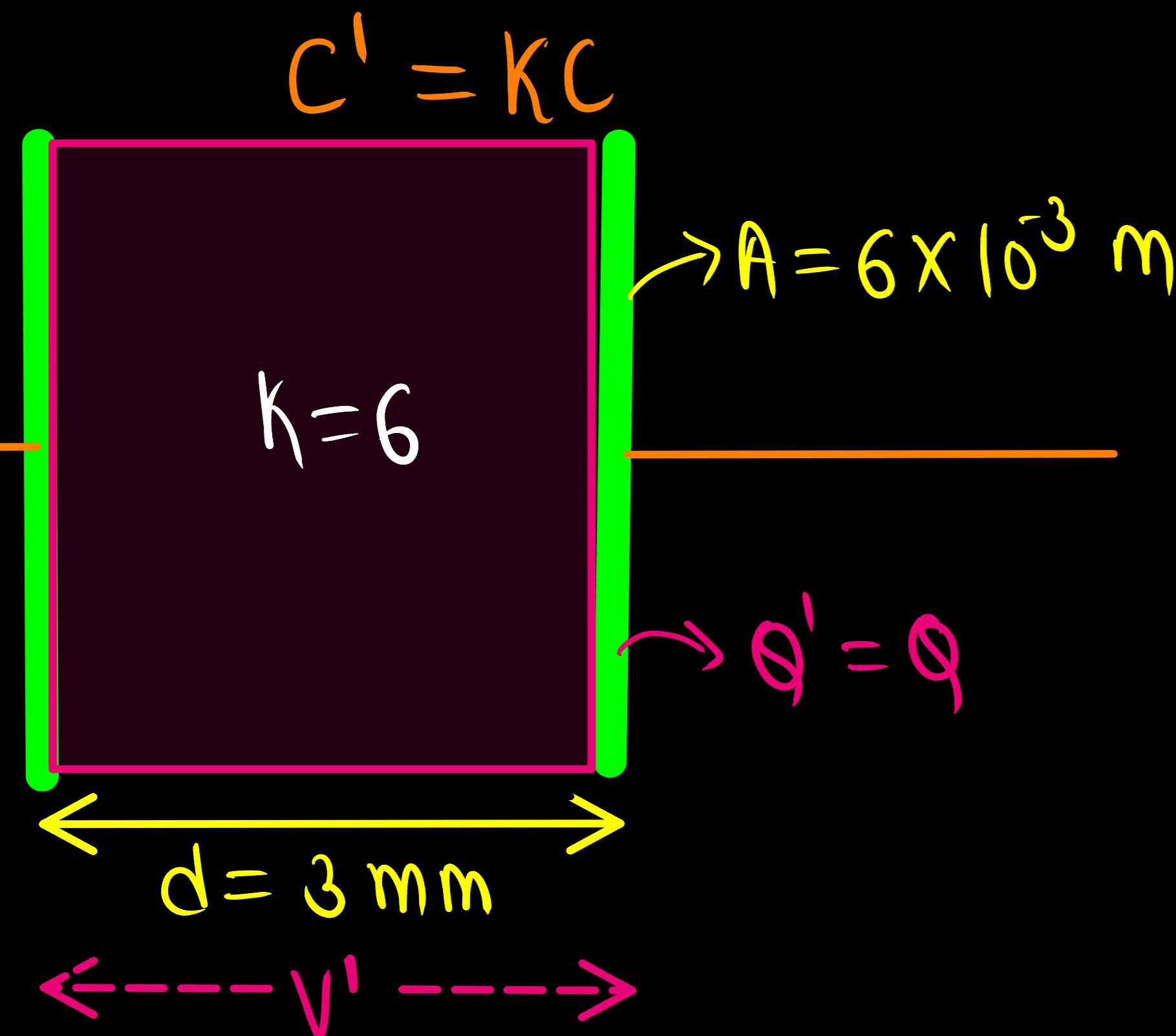

* When dielectric is inserted after the supply was disconnected.

$Q' = Q$ → Charge on Capacitor plate remains constant

$C' = kC$ → Capacitance increases


$$V' = \frac{Q'}{C'}$$

$$V' = \frac{Q}{kC}$$

2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,

- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.

b)

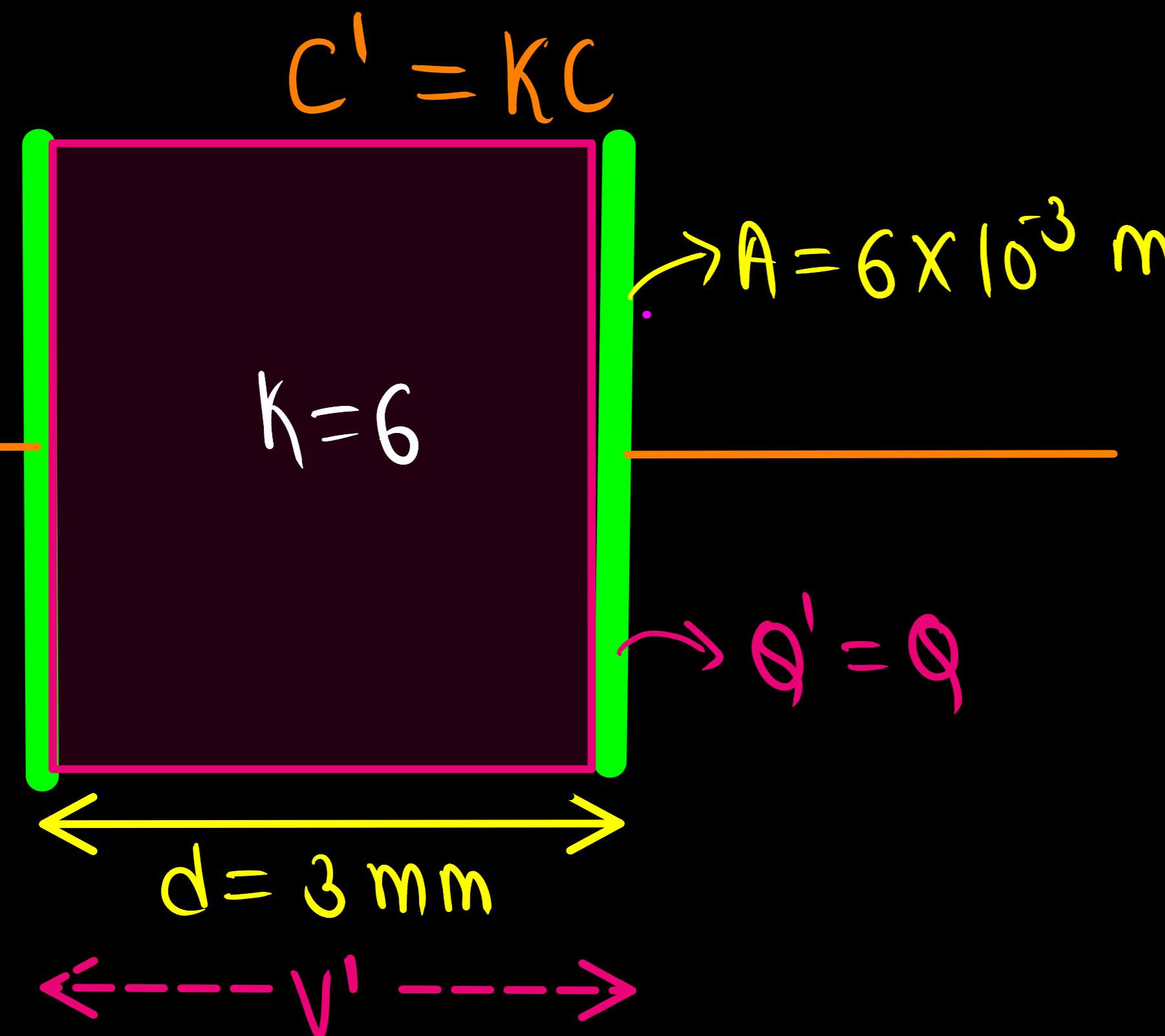

* When dielectric is inserted after the supply was disconnected.

$Q' = Q$ → Charge on Capacitor plate remains constant

$C' = KC$ → Capacitance increases

$$V' = \frac{Q'}{C'}$$


$$V' = \frac{Q}{KC}$$

$$V' = \frac{V}{K} \quad (\because \frac{Q}{C} = V)$$



↳ Voltage decreases $\frac{1}{K}$ times.

Example 2.8 A slab of material of dielectric constant K has the same area as the plates of a parallel-plate capacitor but has a thickness $(3/4)d$, where d is the separation of the plates. How is the capacitance changed when the slab is inserted between the plates?

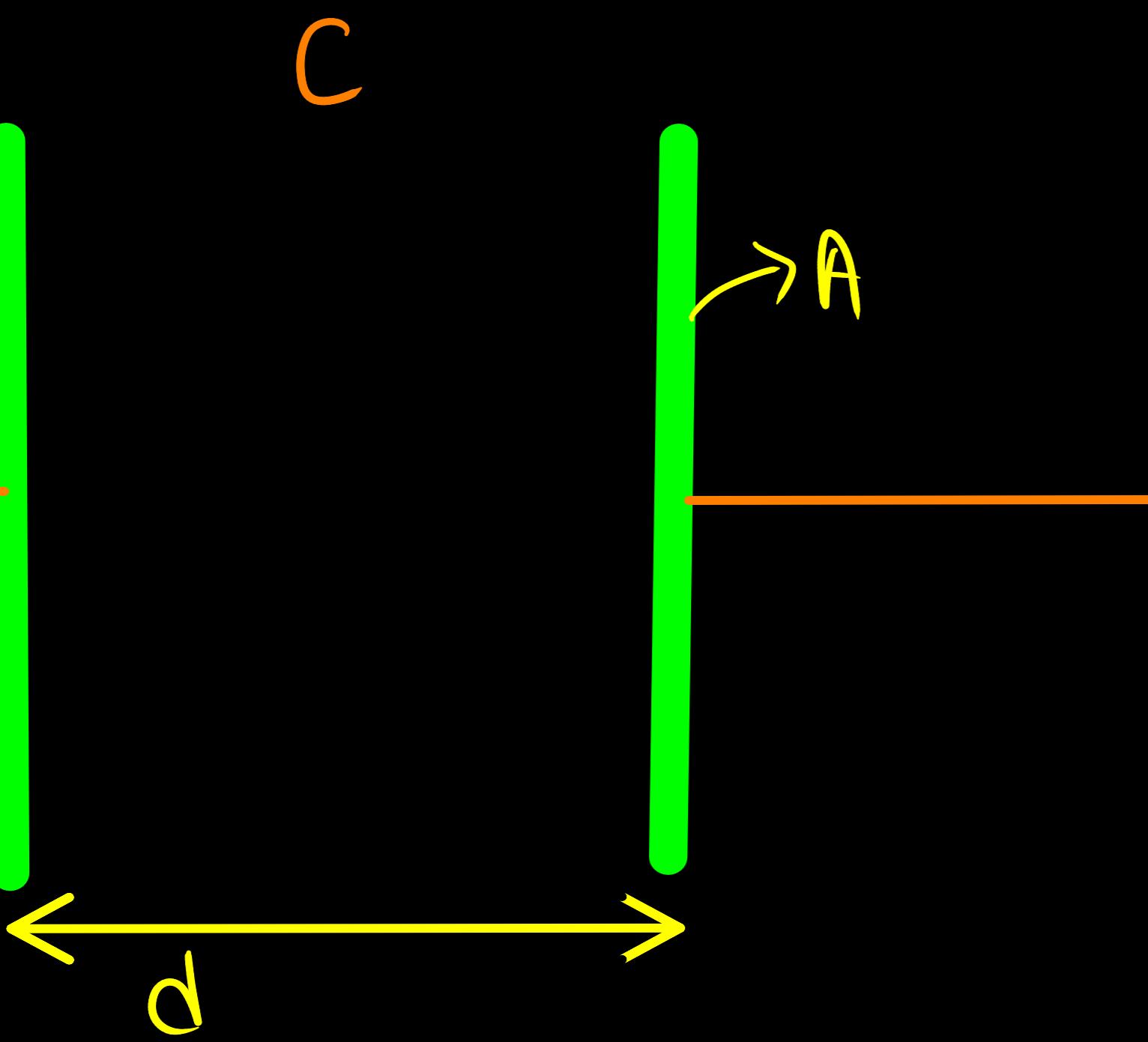
Example 2.8 A slab of material of dielectric constant K has the same area as the plates of a parallel-plate capacitor but has a thickness $(3/4)d$, where d is the separation of the plates. How is the capacitance changed when the slab is inserted between the plates?



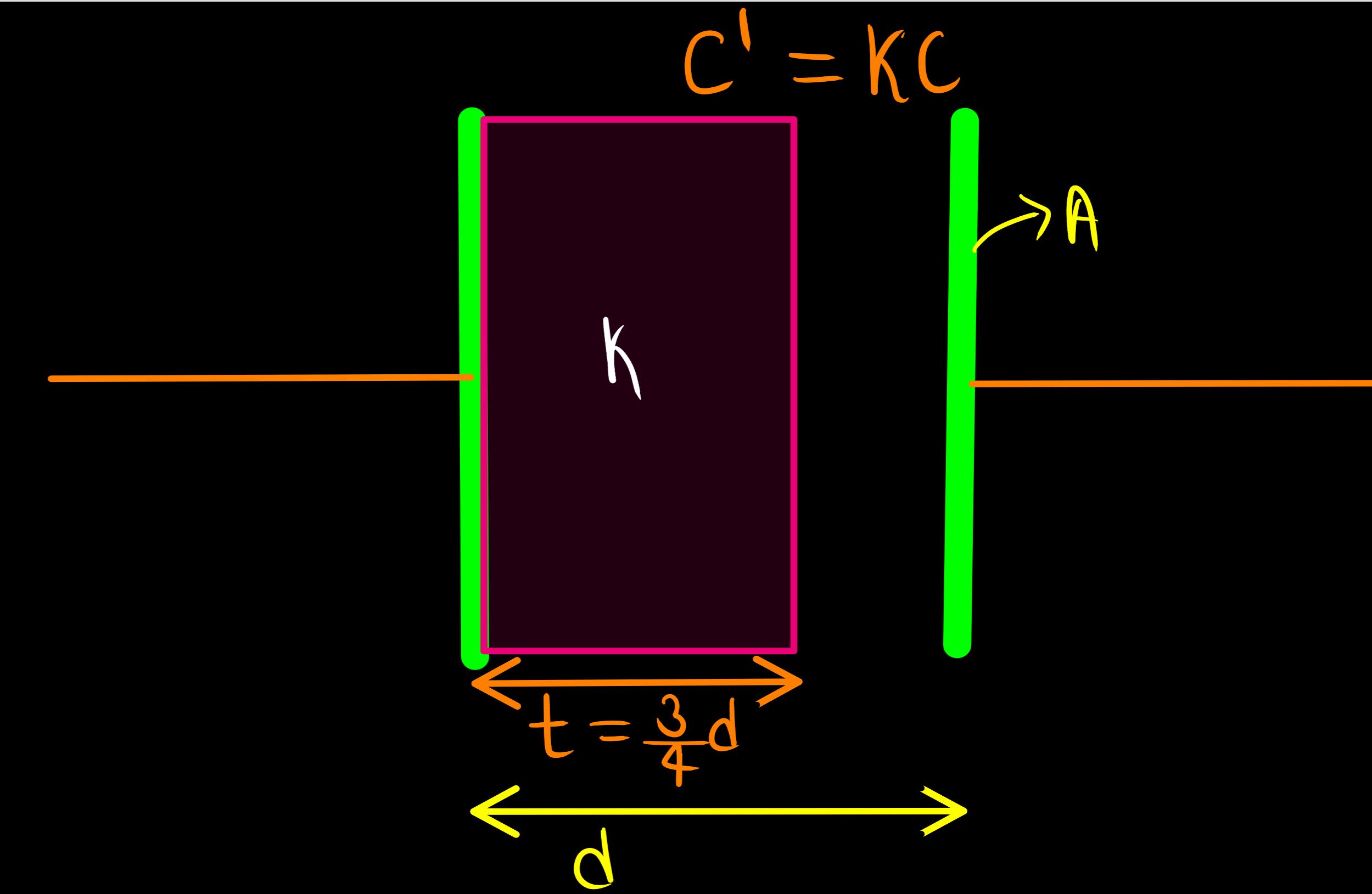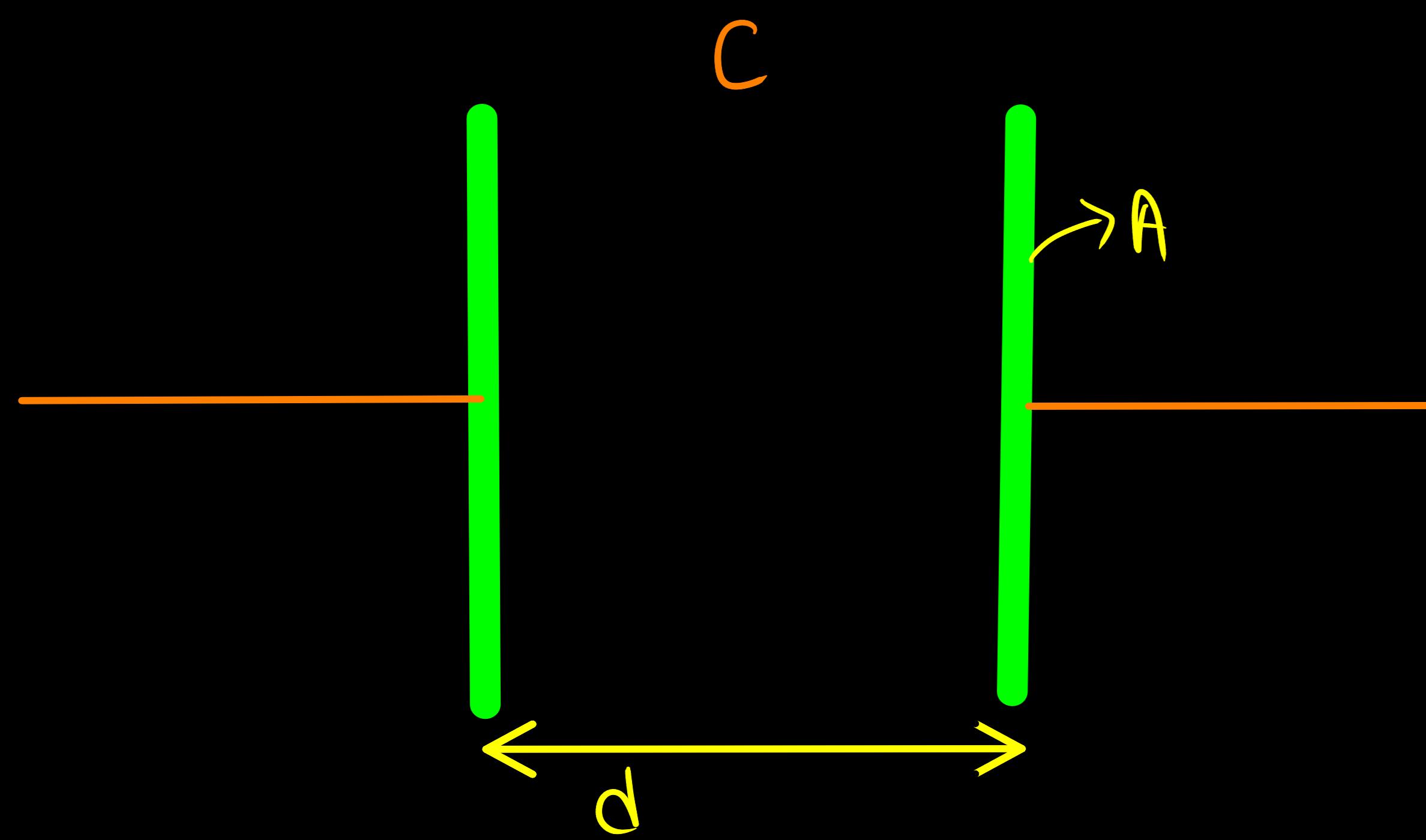
Example 2.8 A slab of material of dielectric constant K has the same area as the plates of a parallel-plate capacitor but has a thickness $(3/4)d$, where d is the separation of the plates. How is the capacitance changed when the slab is inserted between the plates?



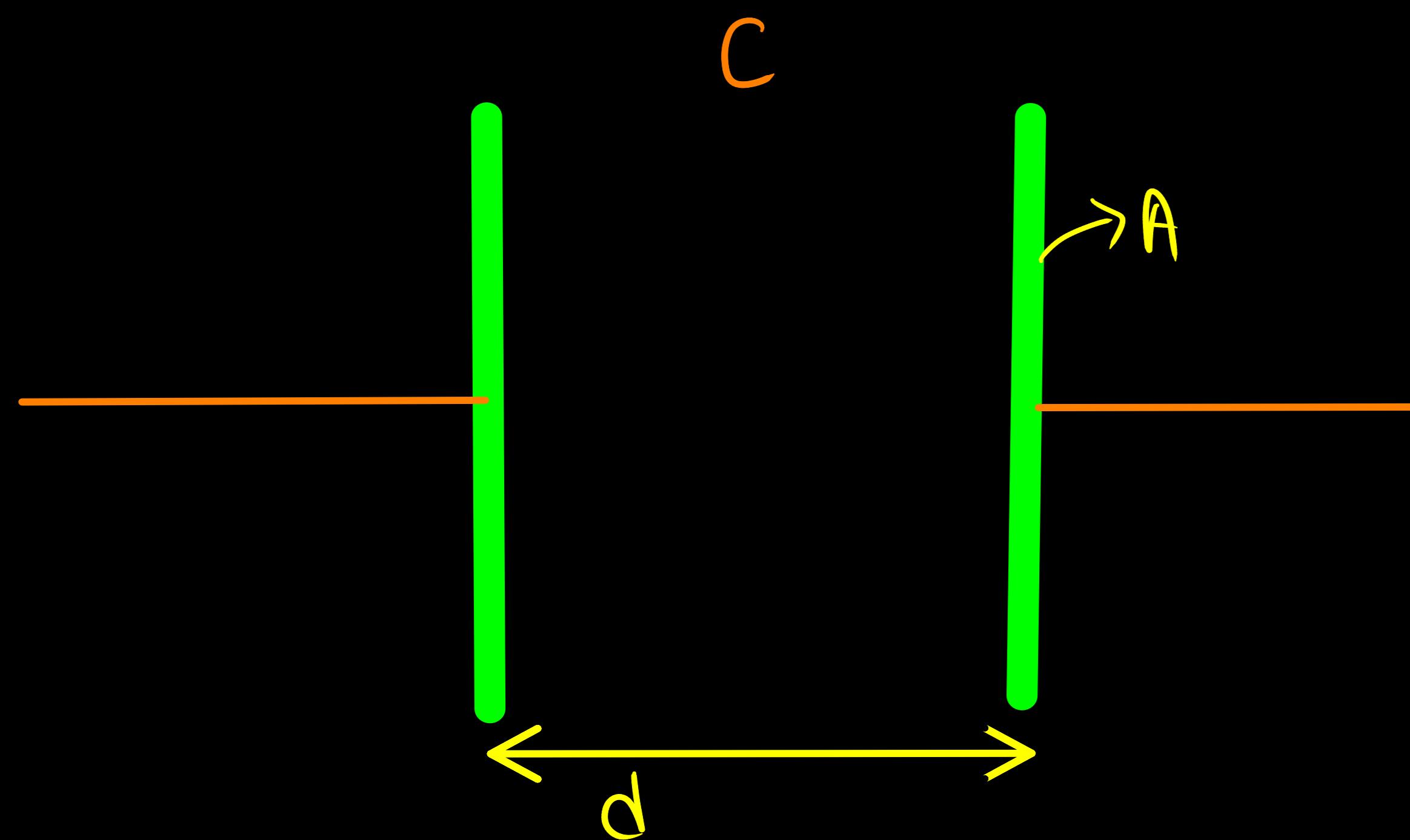
Example 2.8 A slab of material of dielectric constant K has the same area as the plates of a parallel-plate capacitor but has a thickness $(3/4)d$, where d is the separation of the plates. How is the capacitance changed when the slab is inserted between the plates?




$$C = \frac{\epsilon_0 A}{d}$$

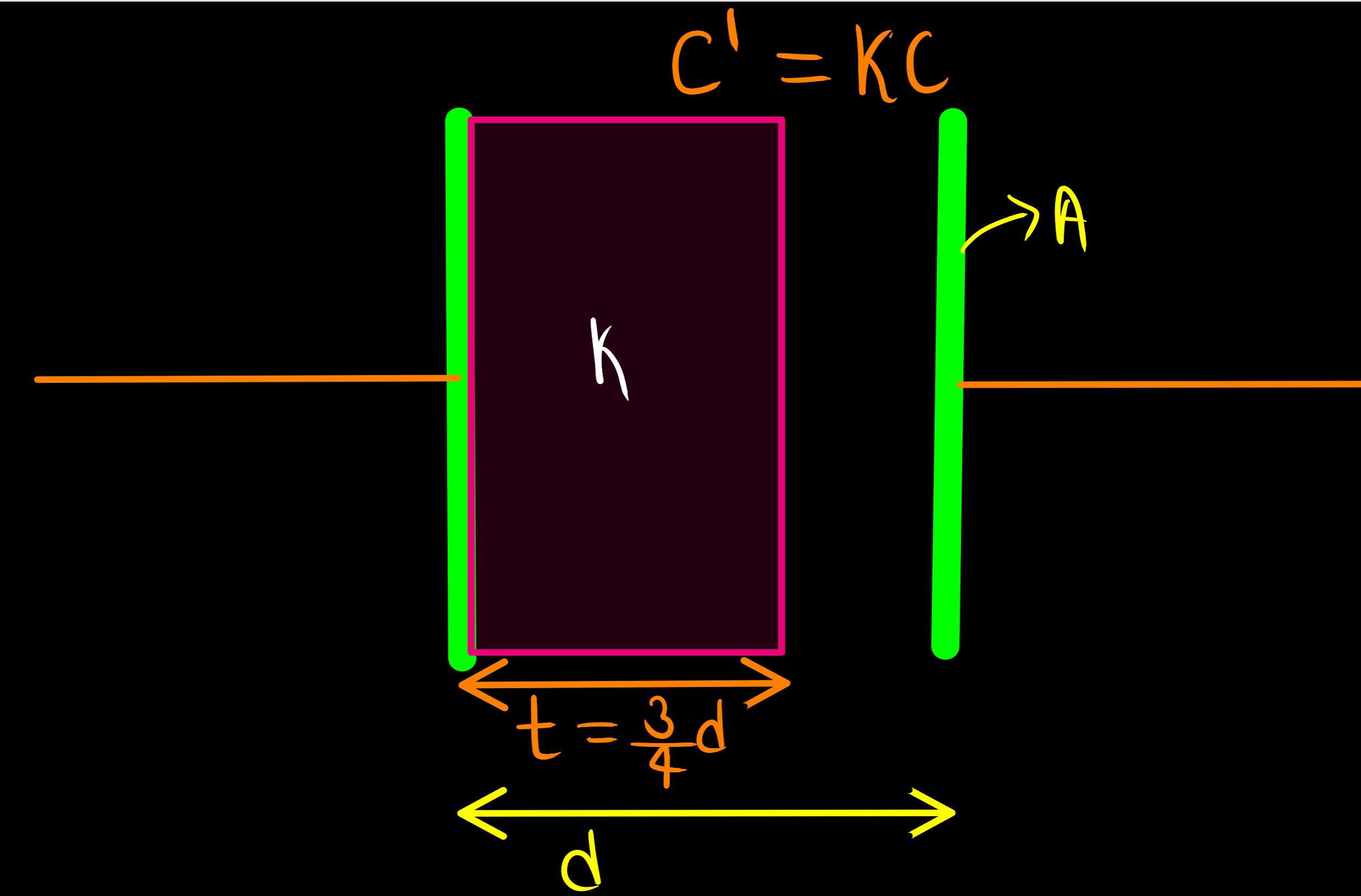

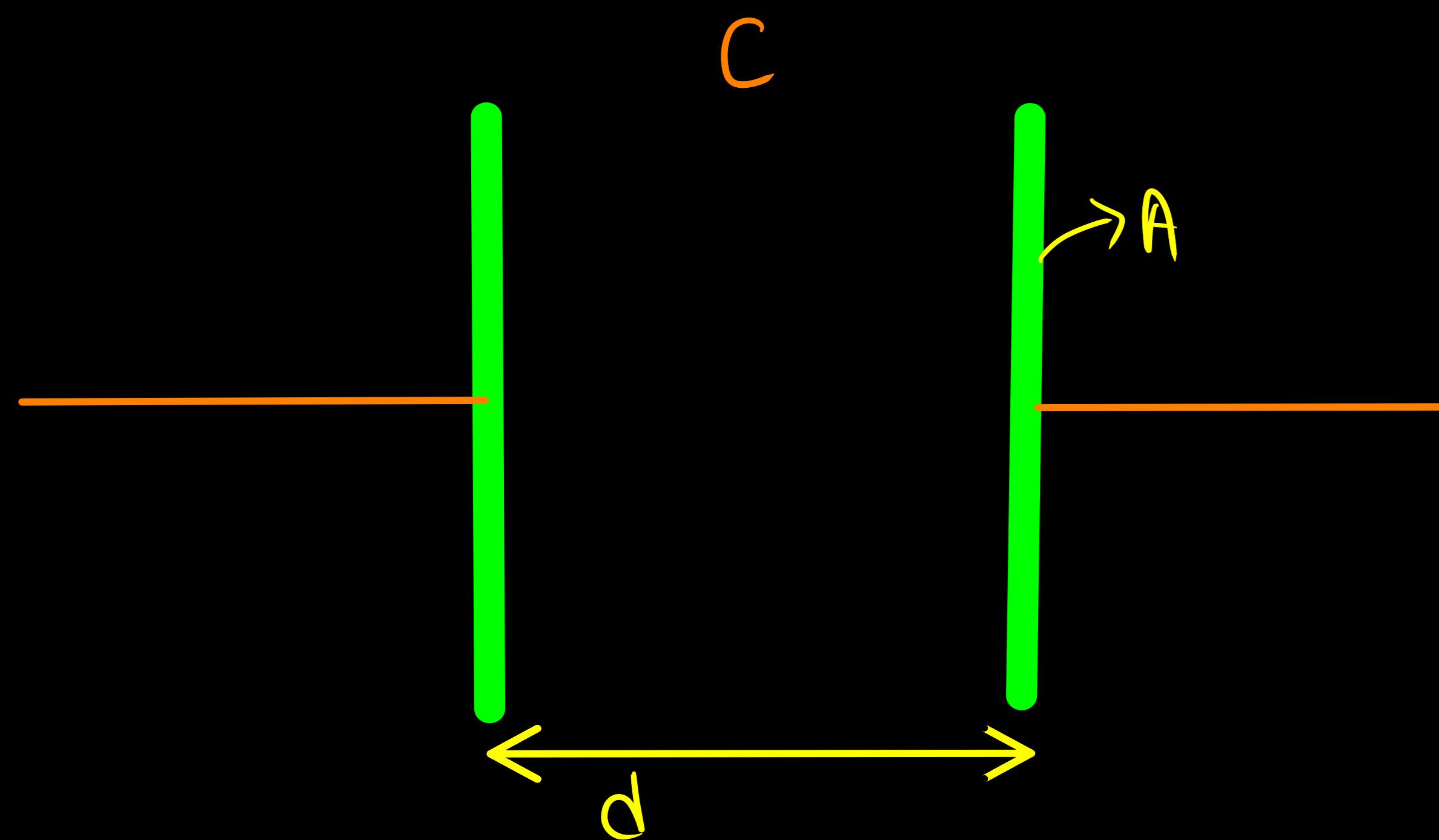Example 2.8 A slab of material of dielectric constant K has the same area as the plates of a parallel-plate capacitor but has a thickness $(3/4)d$, where d is the separation of the plates. How is the capacitance changed when the slab is inserted between the plates?




$$C = \frac{\epsilon_0 A}{d}$$

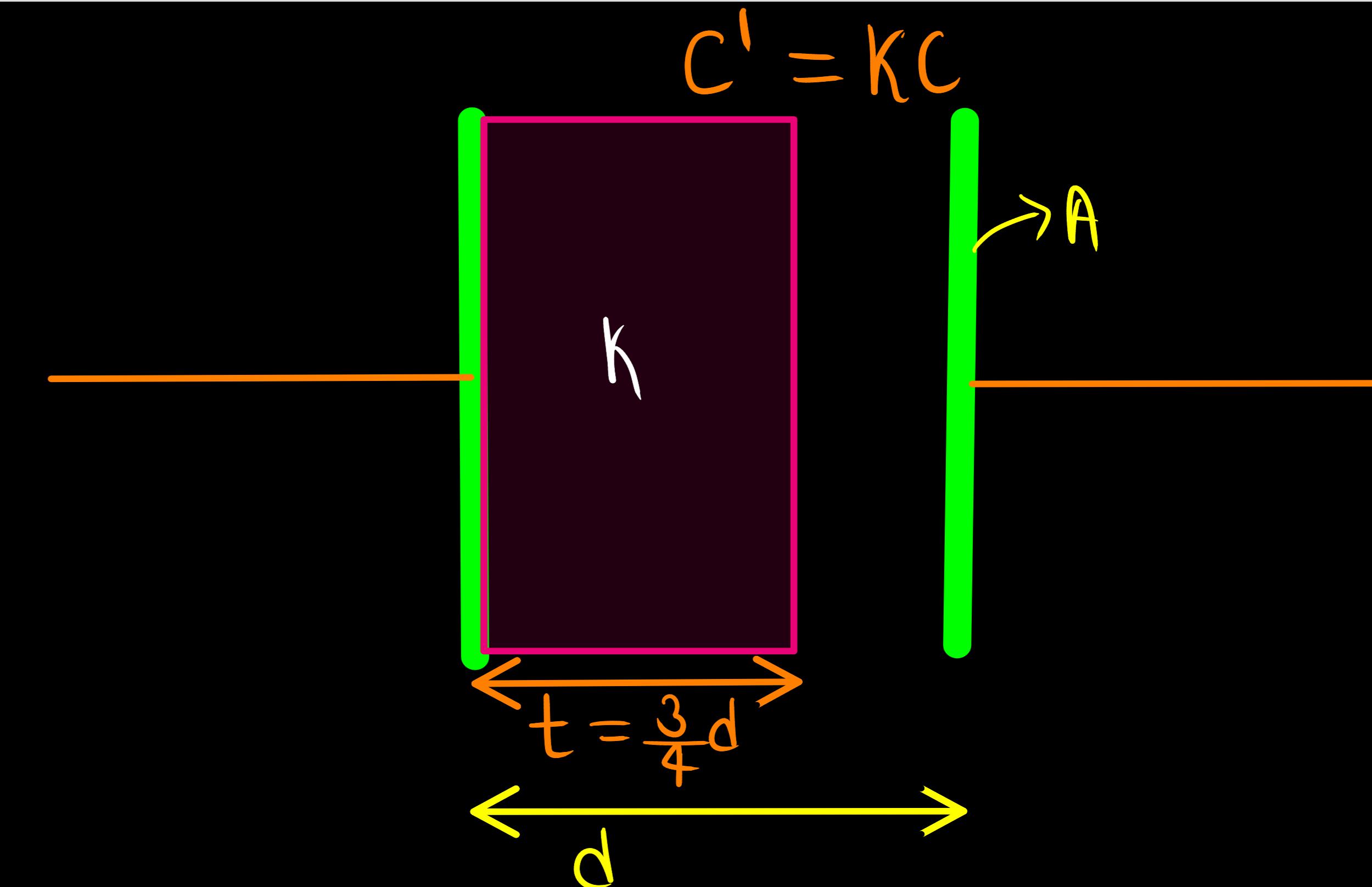


$$C' = \frac{\epsilon_0 A}{\left(d - t + \frac{t}{K}\right)}$$

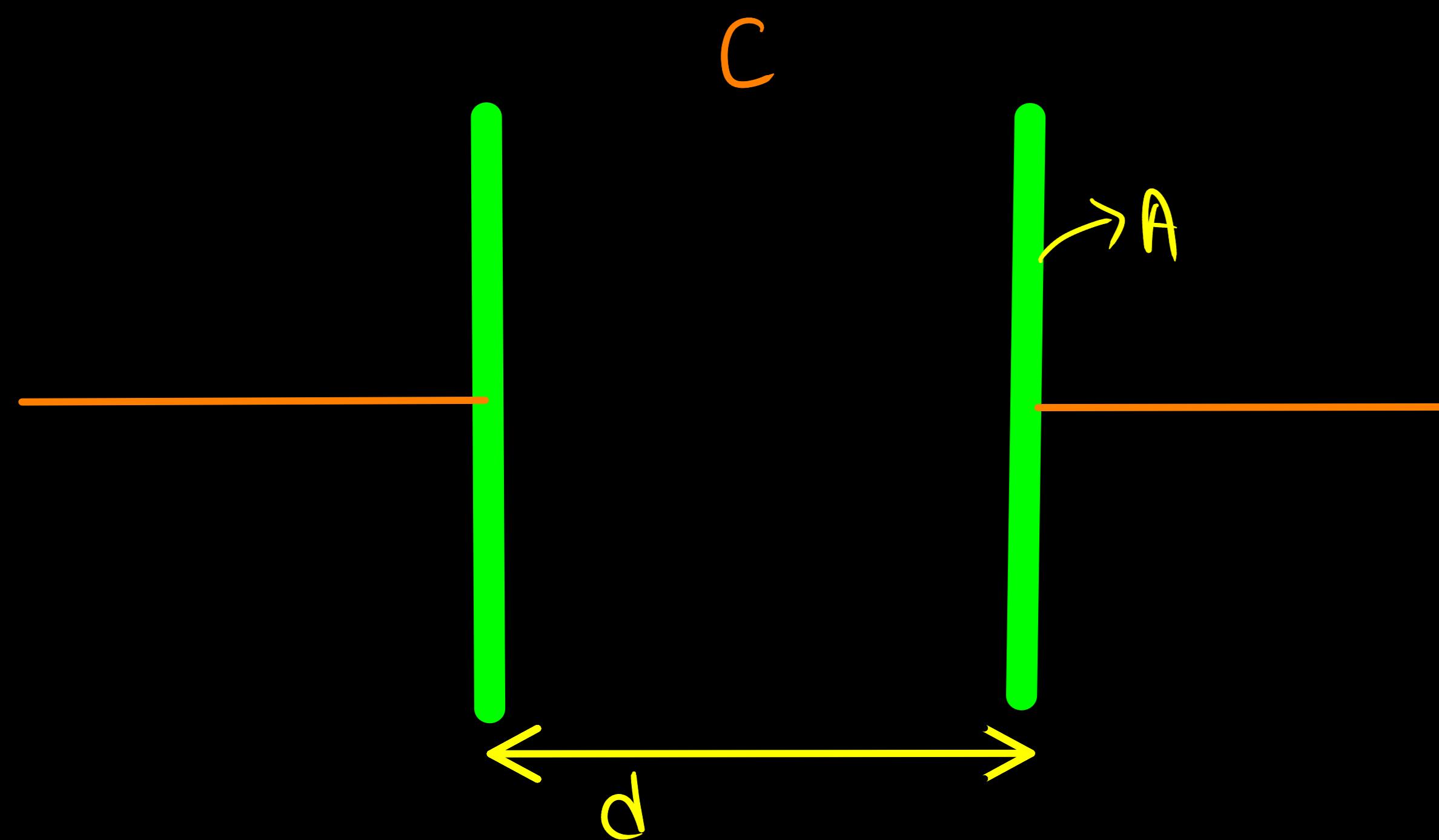Example 2.8 A slab of material of dielectric constant K has the same area as the plates of a parallel-plate capacitor but has a thickness $(3/4)d$, where d is the separation of the plates. How is the capacitance changed when the slab is inserted between the plates?




$$C = \frac{\epsilon_0 A}{d}$$

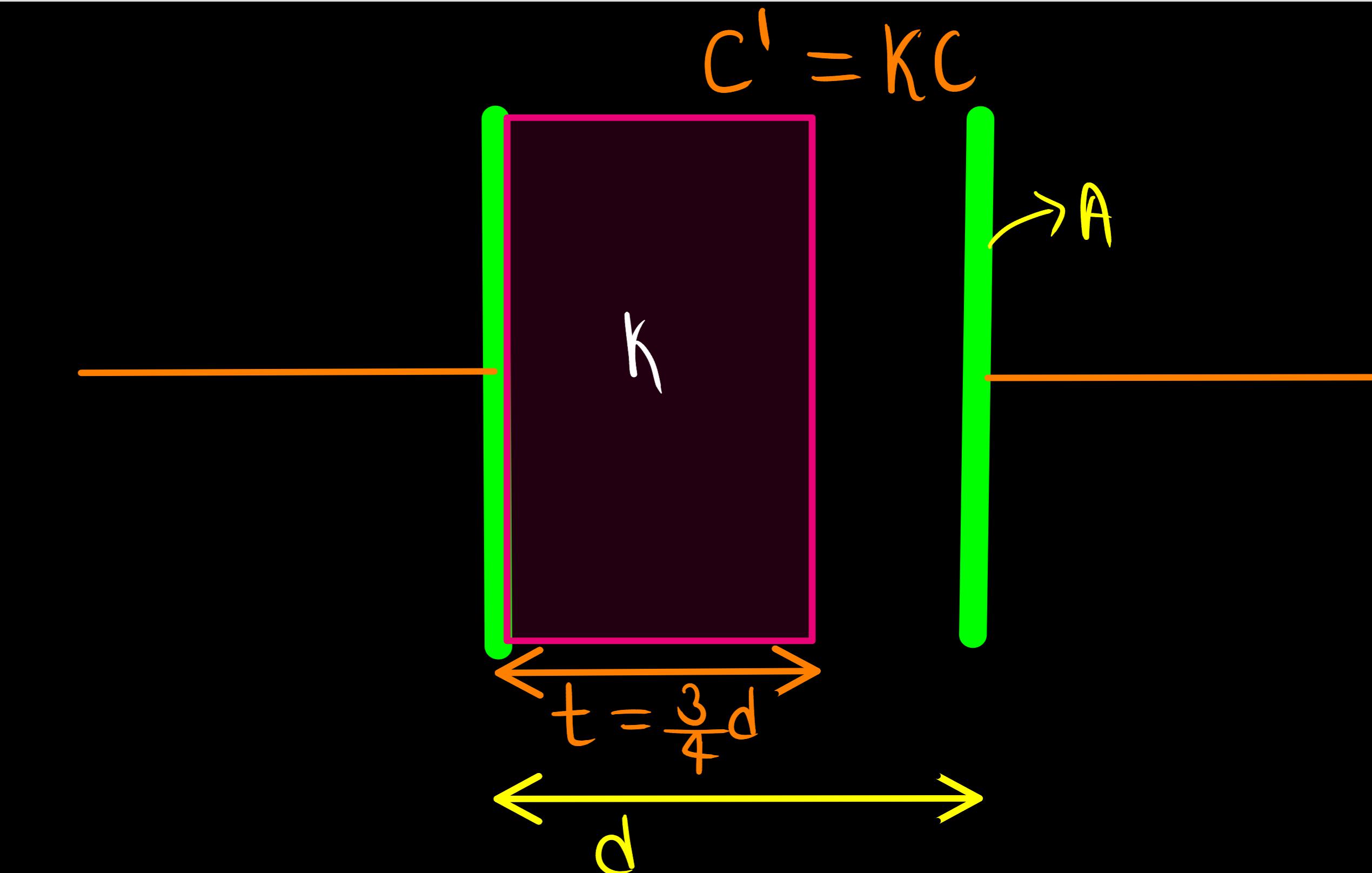


$$C' = \frac{\epsilon_0 A}{(d - t + \frac{t}{K})}$$

$$C' = \frac{\epsilon_0 A}{\left(d - \frac{3d}{4} + \frac{3d}{4K}\right)}$$

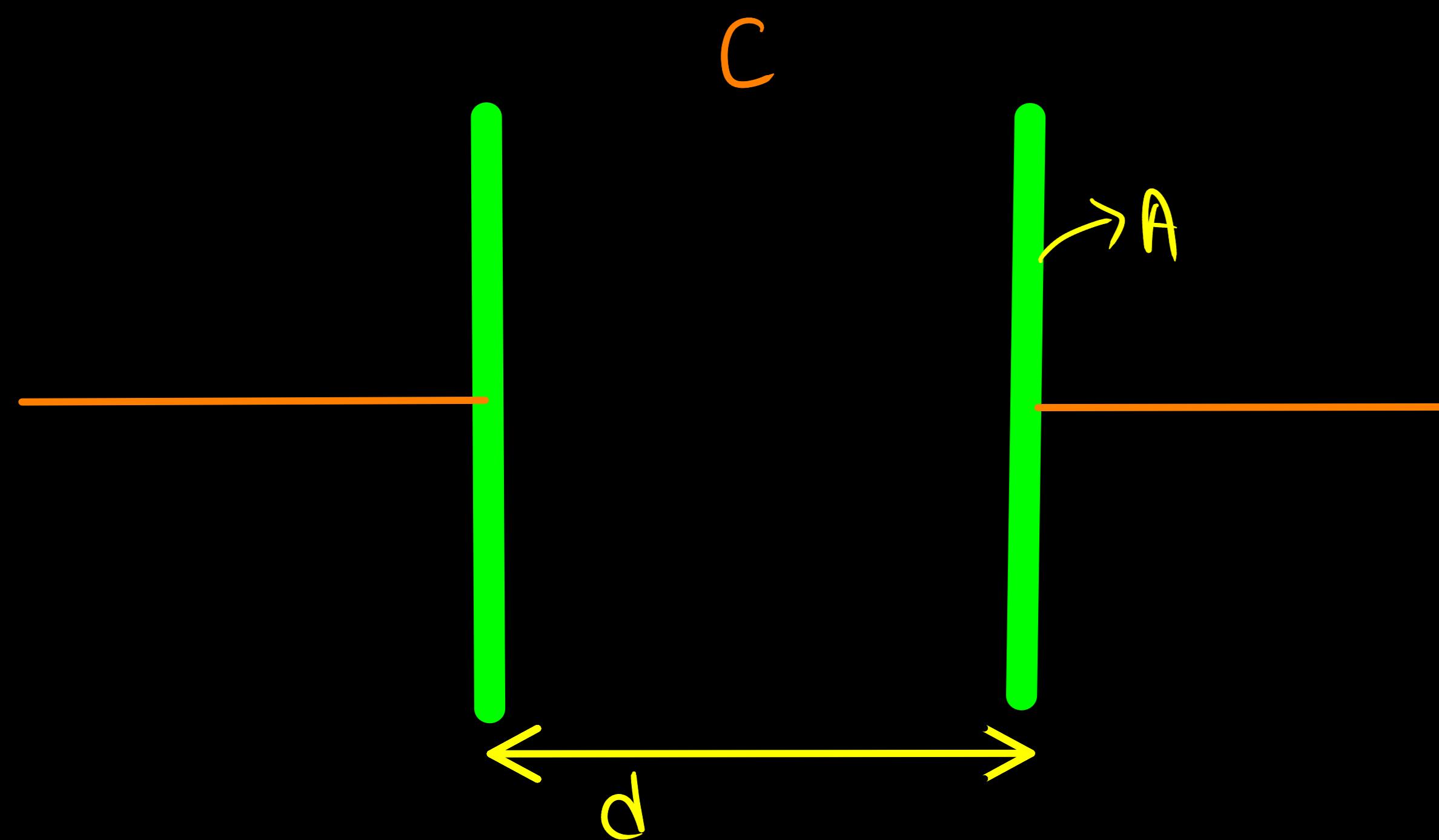Example 2.8 A slab of material of dielectric constant K has the same area as the plates of a parallel-plate capacitor but has a thickness $(3/4)d$, where d is the separation of the plates. How is the capacitance changed when the slab is inserted between the plates?



$$C = \frac{\epsilon_0 A}{d}$$

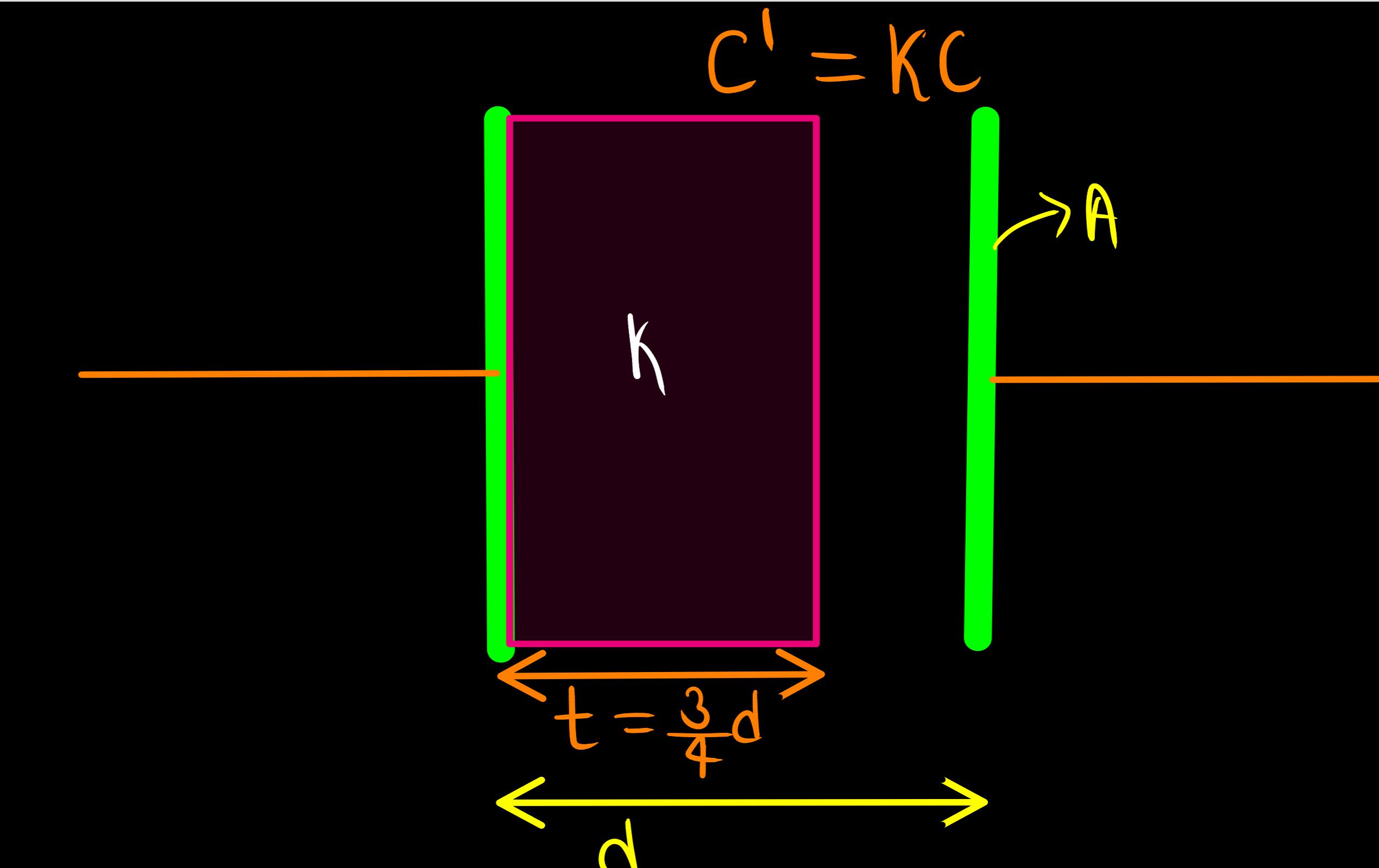


$$C' = \frac{\epsilon_0 A}{(d - t + \frac{t}{K})}$$


$$C' = \frac{\epsilon_0 A}{\left(d - \frac{3d}{4} + \frac{3d}{4K}\right)} = \frac{\epsilon_0 A}{\left(\frac{d}{4} + \frac{3d}{4K}\right)}$$

$$C' = \frac{4\epsilon_0 A}{d(1 + \frac{3}{K})}$$

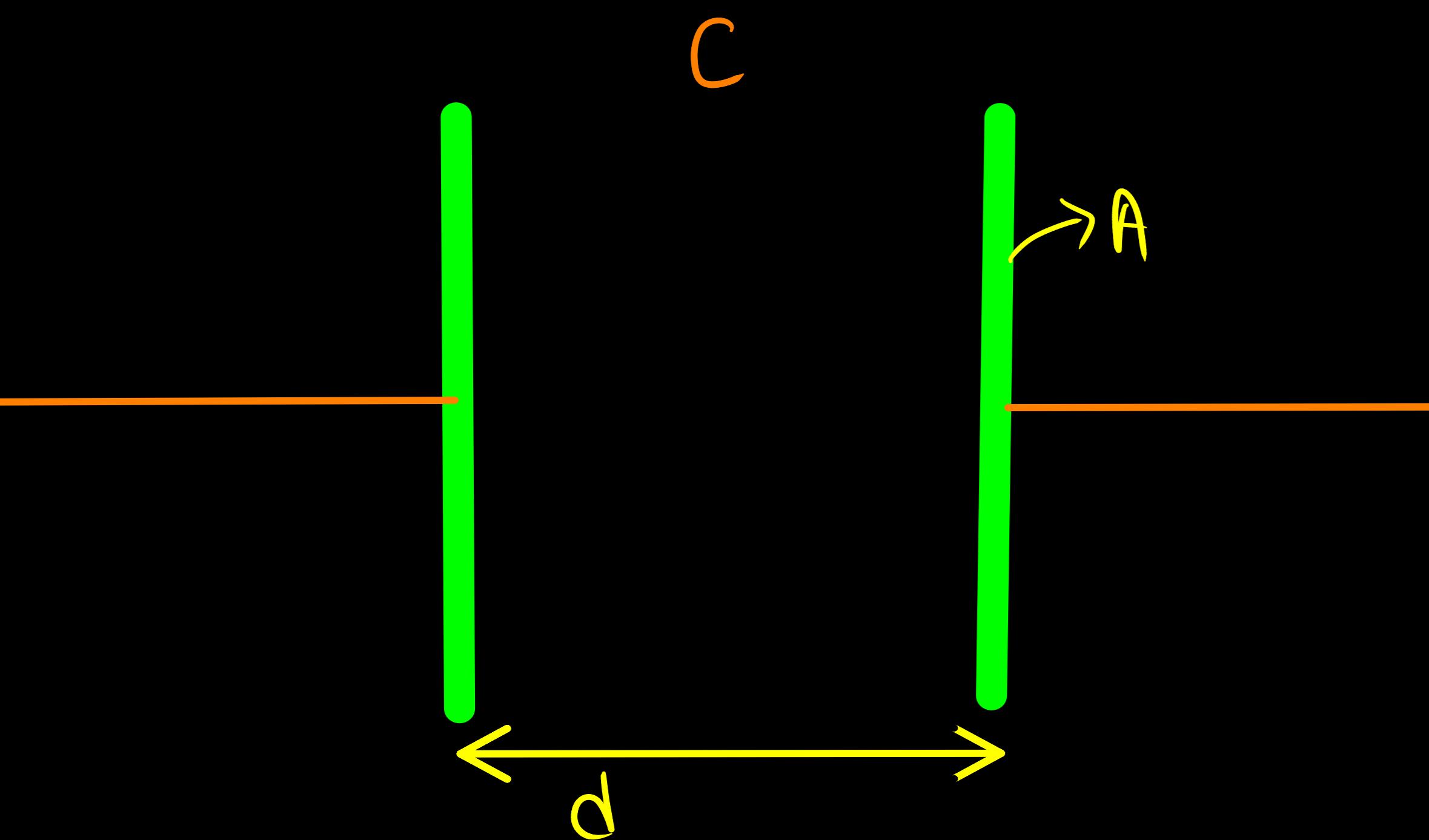Example 2.8 A slab of material of dielectric constant K has the same area as the plates of a parallel-plate capacitor but has a thickness $(3/4)d$, where d is the separation of the plates. How is the capacitance changed when the slab is inserted between the plates?



$$C = \frac{\epsilon_0 A}{d}$$

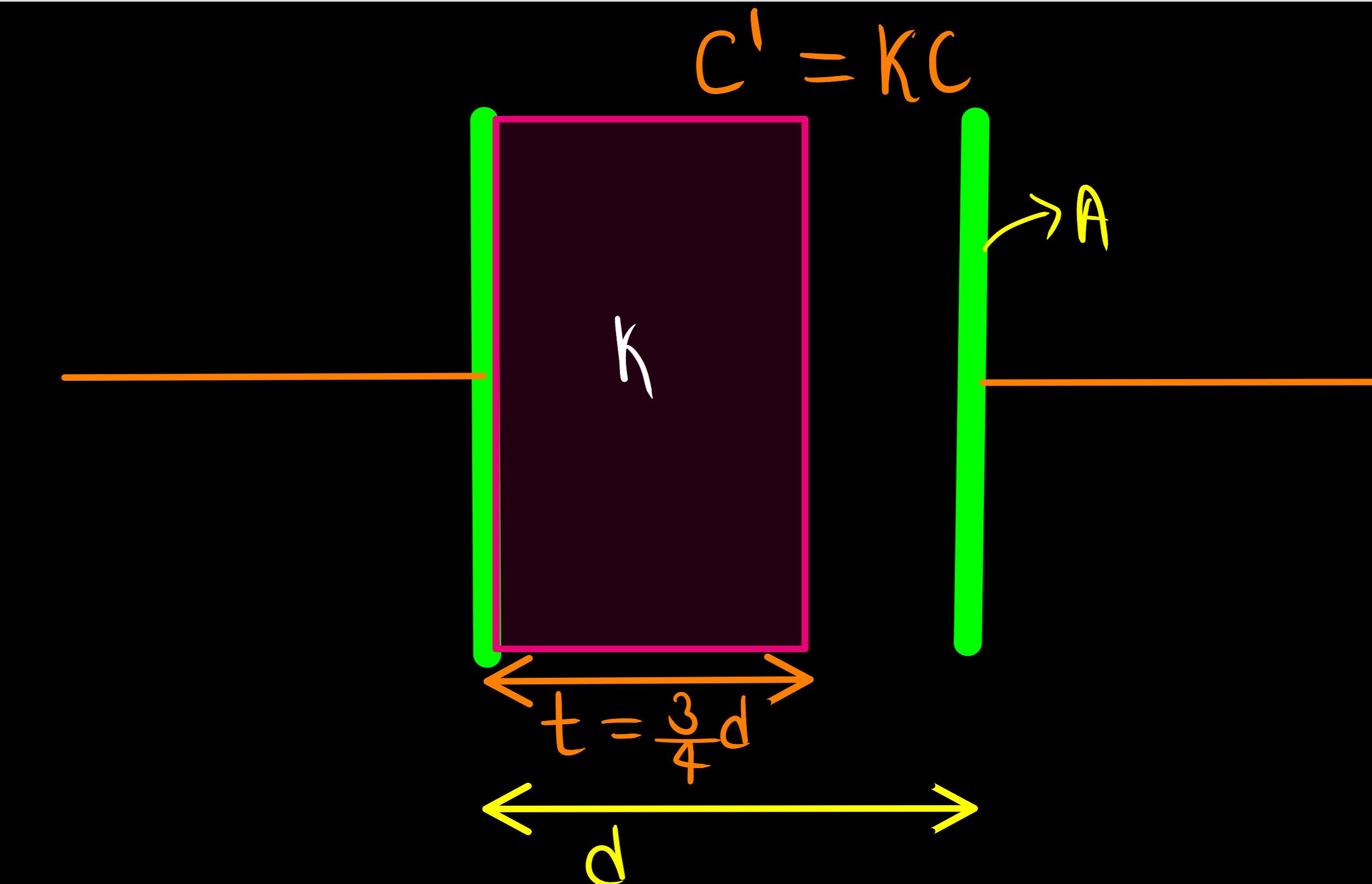


$$C' = \frac{\epsilon_0 A}{(d - t + \frac{t}{K})}$$

$$C' = \frac{\epsilon_0 A}{\left(d - \frac{3d}{4} + \frac{3d}{4K}\right)} = \frac{\epsilon_0 A}{\left(\frac{d}{4} + \frac{3d}{4K}\right)}$$

$$C' = \frac{4\epsilon_0 A}{d(1 + \frac{3}{K})} = \frac{4K}{(K+3)} C$$

- 2.6** Three capacitors each of capacitance 9 pF are connected in series.
- (a) What is the total capacitance of the combination?
 - (b) What is the potential difference across each capacitor if the combination is connected to a 120 V supply?

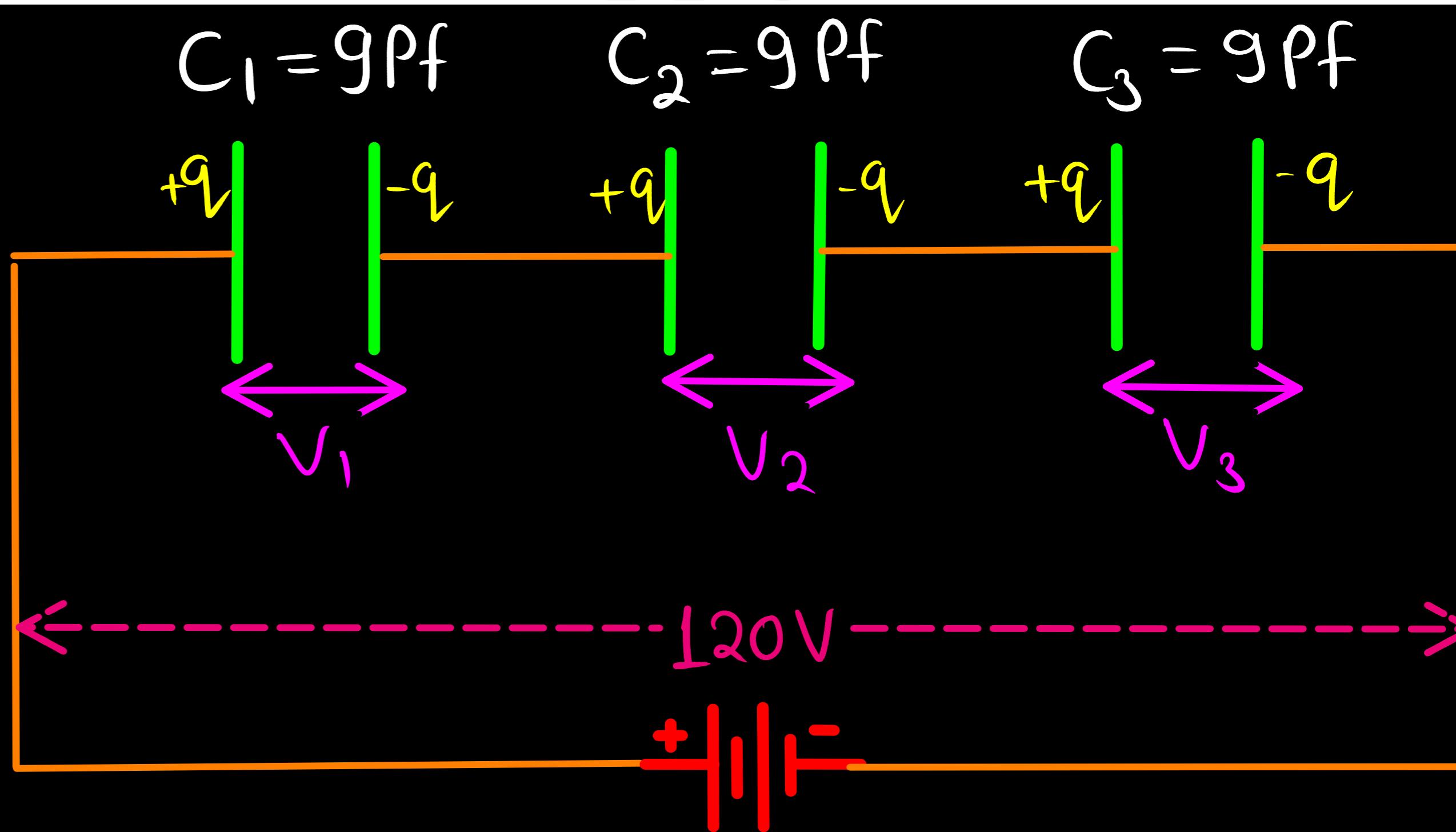- 2.6** Three capacitors each of capacitance 9 pF are connected in series.
- What is the total capacitance of the combination?
 - What is the potential difference across each capacitor if the combination is connected to a 120 V supply?




2.6 Three capacitors each of capacitance 9 pF are connected in series.

- (a) What is the total capacitance of the combination?
- (b) What is the potential difference across each capacitor if the combination is connected to a 120 V supply?

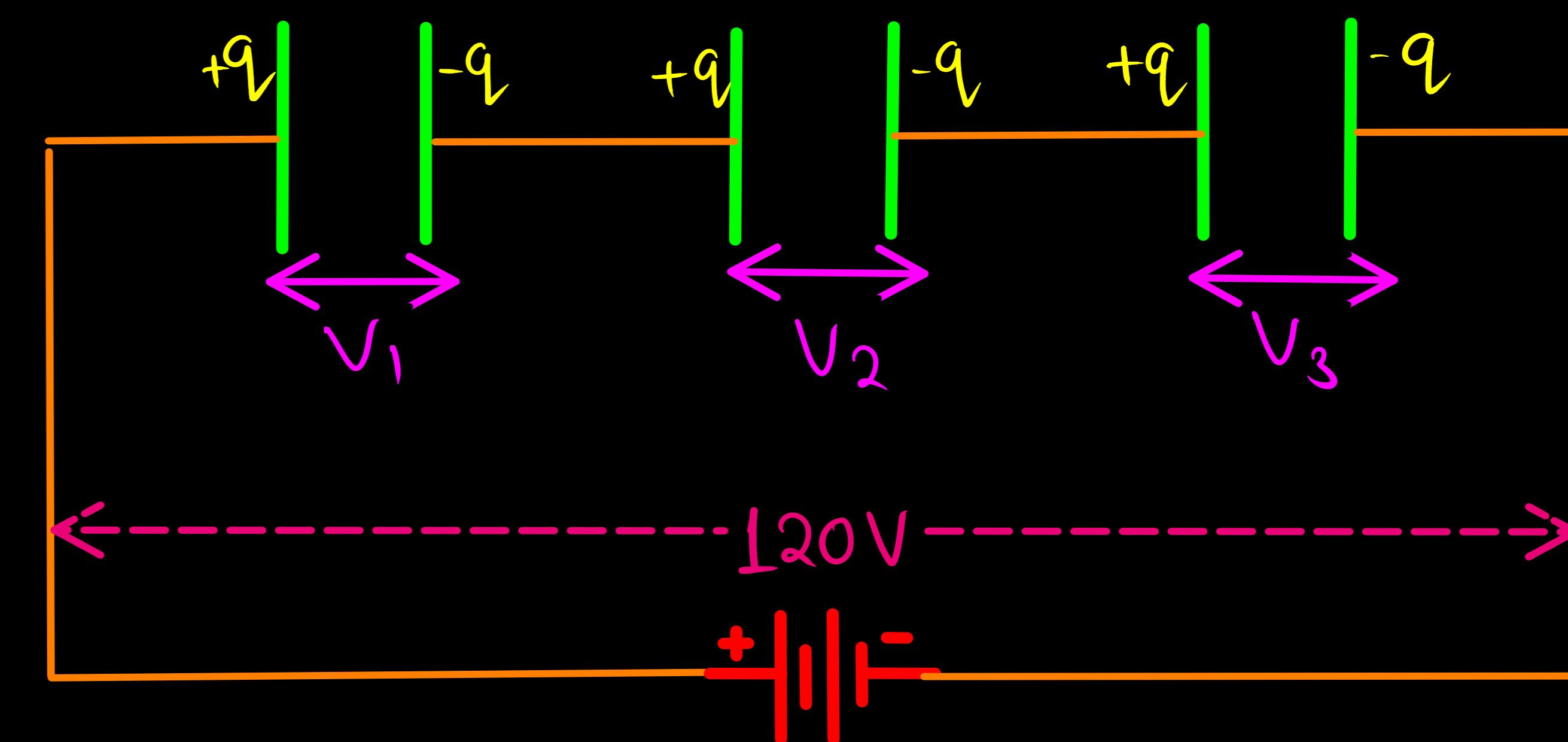*(a) $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$

$$C_1 = 9 \text{ pF} \quad C_2 = 9 \text{ pF} \quad C_3 = 9 \text{ pF}$$



2.6 Three capacitors each of capacitance 9 pF are connected in series.


- (a) What is the total capacitance of the combination?
- (b) What is the potential difference across each capacitor if the combination is connected to a 120 V supply?

*(a)

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C} = \frac{1}{9} + \frac{1}{9} + \frac{1}{9}$$
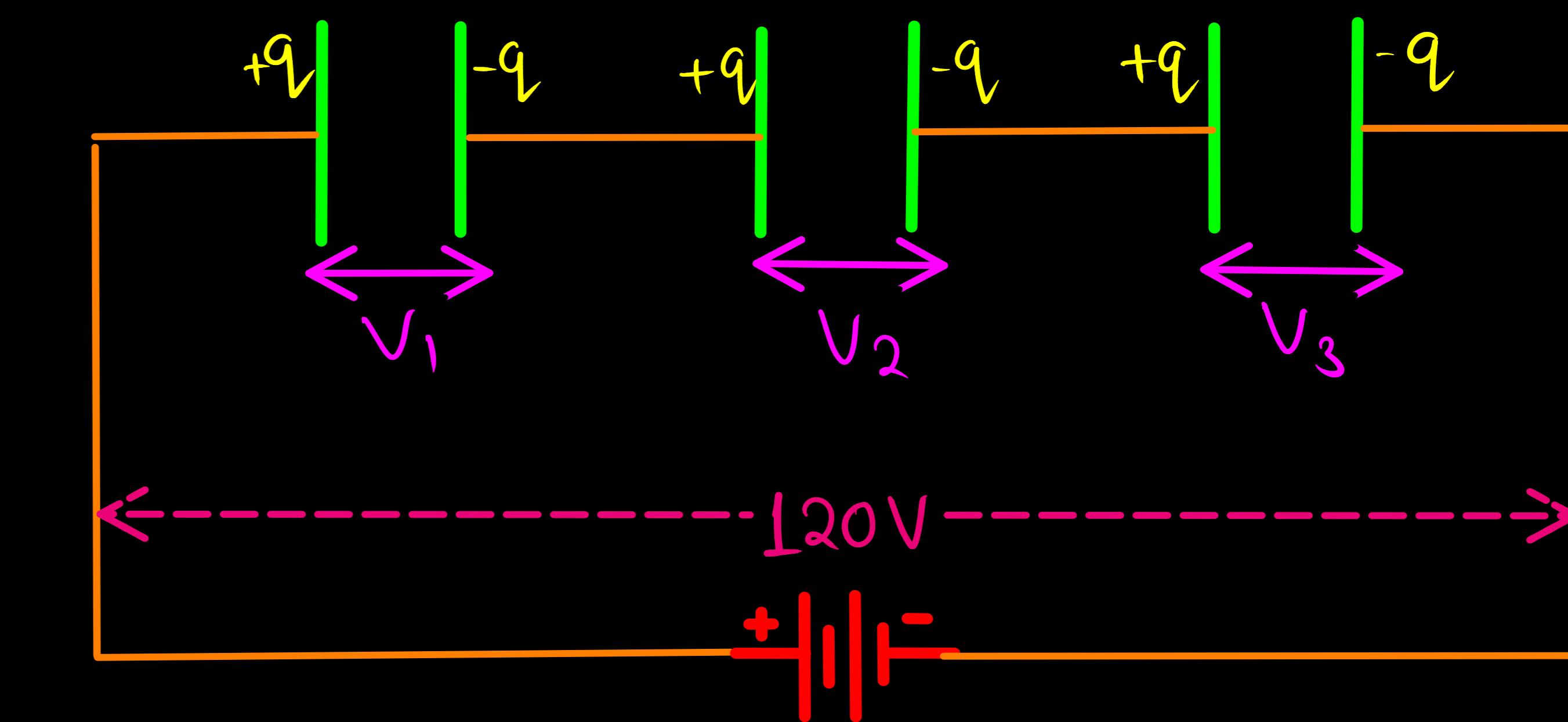
$$C_1 = 9 \text{ pF} \quad C_2 = 9 \text{ pF} \quad C_3 = 9 \text{ pF}$$



- 2.6** Three capacitors each of capacitance 9 pF are connected in series.
- What is the total capacitance of the combination?
 - What is the potential difference across each capacitor if the combination is connected to a 120 V supply?


*(a)

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C} = \frac{1}{9} + \frac{1}{9} + \frac{1}{9}$$

$$\frac{1}{C} = \frac{3}{9}$$
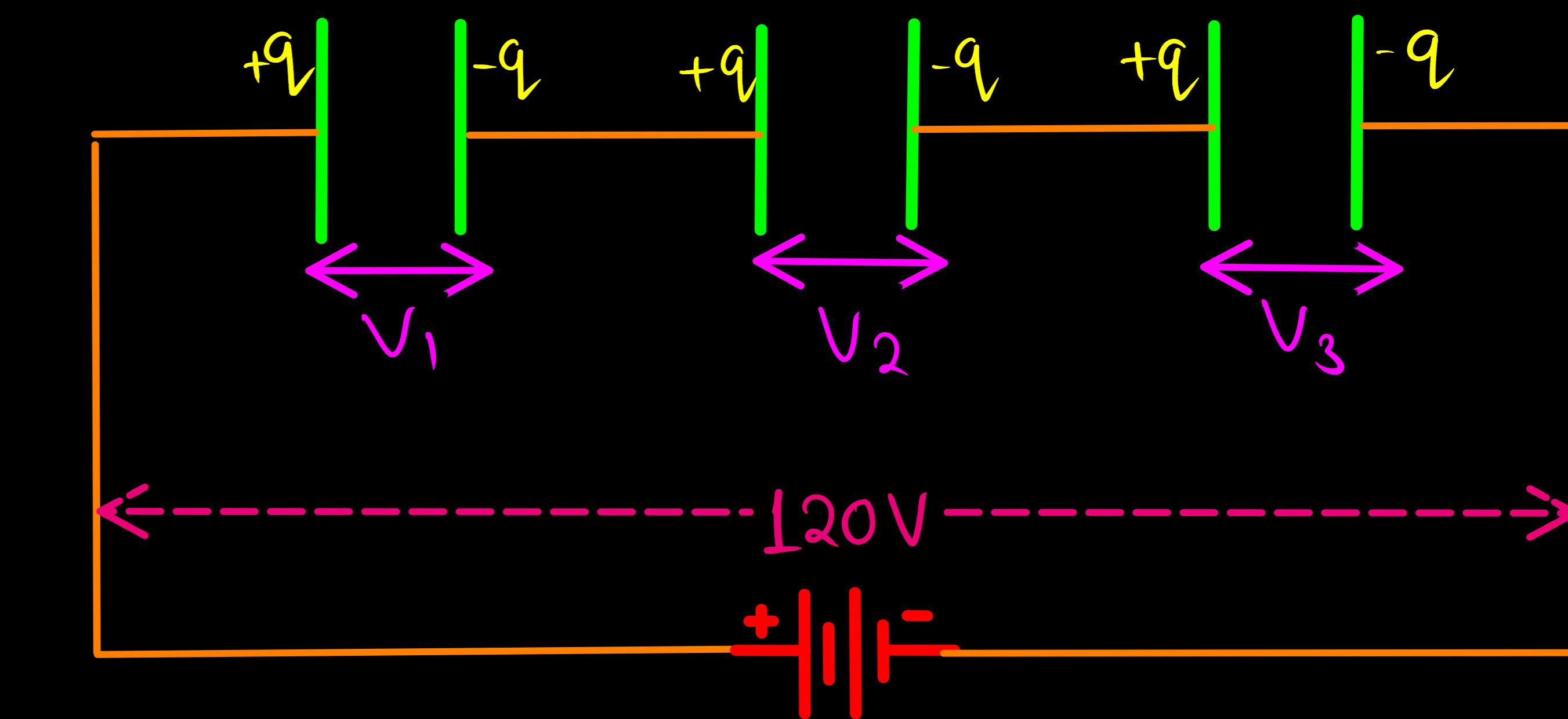
$$C_1 = 9 \text{ pF} \quad C_2 = 9 \text{ pF} \quad C_3 = 9 \text{ pF}$$



2.6 Three capacitors each of capacitance 9 pF are connected in series.

- (a) What is the total capacitance of the combination?
- (b) What is the potential difference across each capacitor if the combination is connected to a 120 V supply?

*(a)


$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C} = \frac{1}{9} + \frac{1}{9} + \frac{1}{9}$$

$$\frac{1}{C} = \frac{3}{9} \quad \frac{1}{3}$$

$$C = 3 \text{ pF}$$
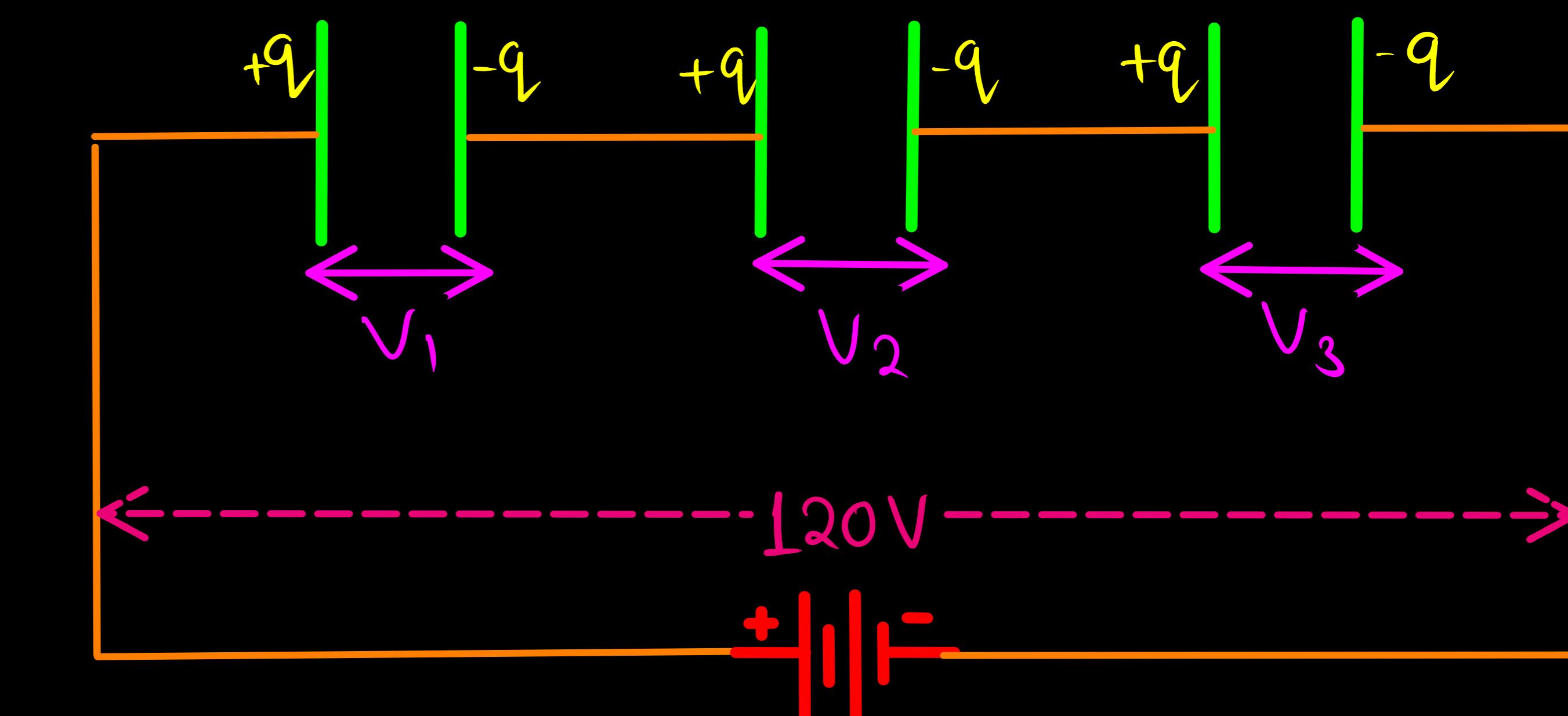
$$C_1 = 9 \text{ pF} \quad C_2 = 9 \text{ pF} \quad C_3 = 9 \text{ pF}$$



2.6 Three capacitors each of capacitance 9 pF are connected in series.

- (a) What is the total capacitance of the combination?
- (b) What is the potential difference across each capacitor if the combination is connected to a 120 V supply?


* (a)

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C} = \frac{1}{9} + \frac{1}{9} + \frac{1}{9}$$

$$\frac{1}{C} = \frac{3}{9} \cdot \frac{1}{3}$$

$$C = 3 \text{ pF}$$

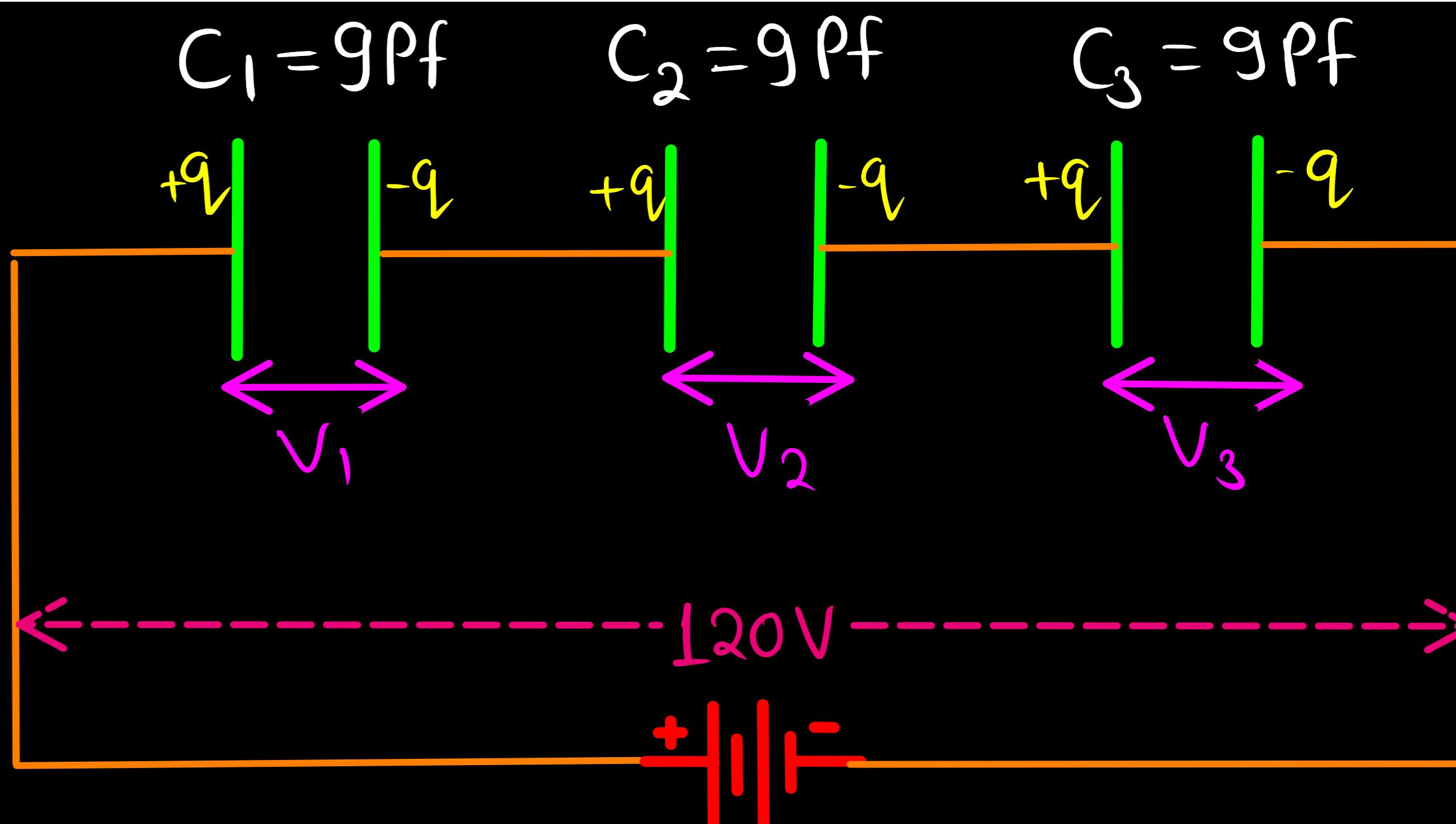

* b)

Charge stored by all Capacitors -

$$q_{V_1} = q_{V_2} = q_{V_3} = q \rightarrow (\text{In series } q \text{ - same})$$

2.6 Three capacitors each of capacitance 9 pF are connected in series.

- (a) What is the total capacitance of the combination?
- (b) What is the potential difference across each capacitor if the combination is connected to a 120 V supply?


* (a)

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C} = \frac{1}{9} + \frac{1}{9} + \frac{1}{9}$$

$$\frac{1}{C} = \frac{3}{9} \cdot \frac{1}{3}$$

$$C = 3 \text{ pF}$$

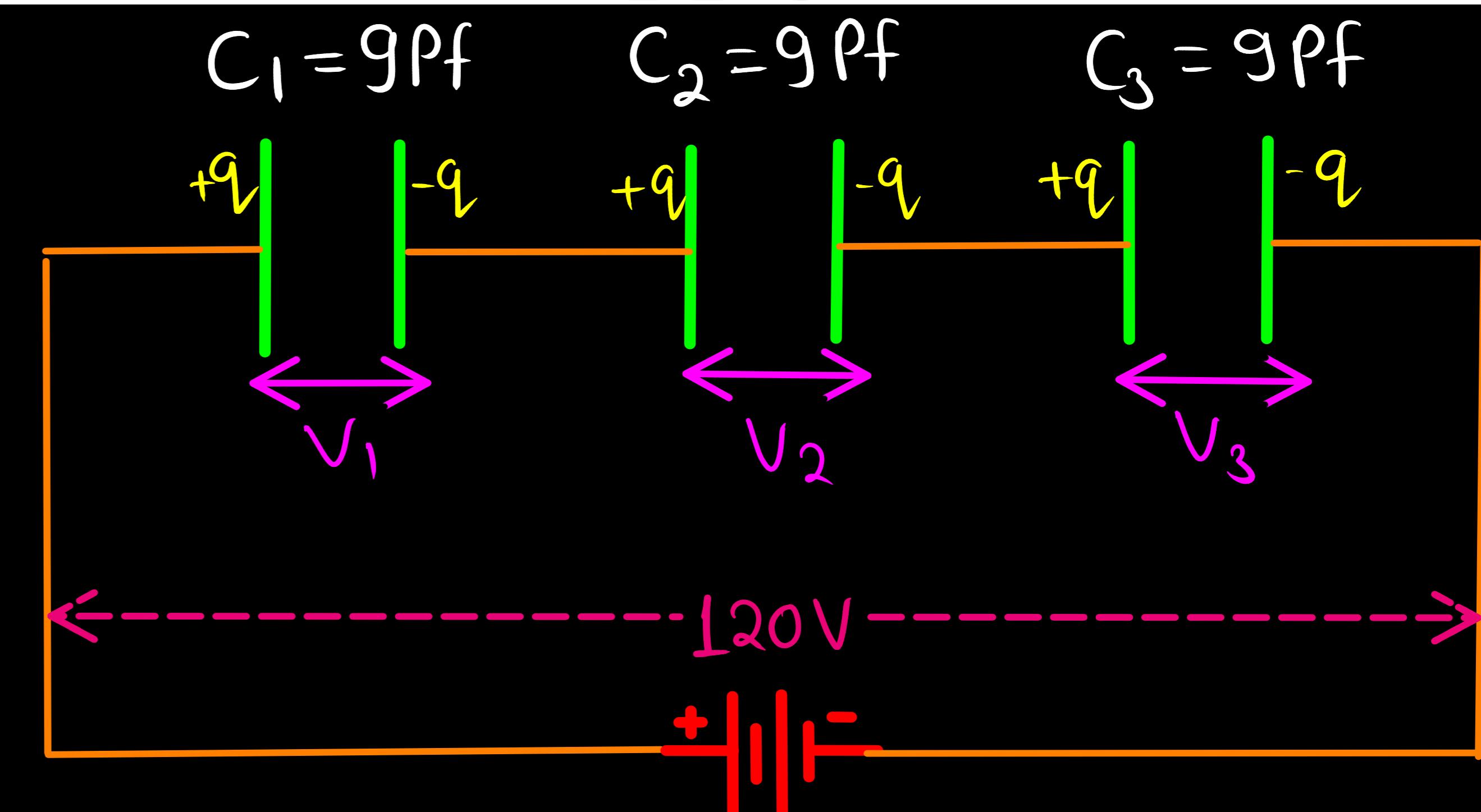

* b)

Charge stored by all Capacitors -

$$q_{V_1} = q_{V_2} = q_{V_3} = q \rightarrow (\text{In series } q \text{ - same})$$

$$q = CV$$

2.6 Three capacitors each of capacitance 9 pF are connected in series.

- (a) What is the total capacitance of the combination?
- (b) What is the potential difference across each capacitor if the combination is connected to a 120 V supply?


* (a)

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C} = \frac{1}{9} + \frac{1}{9} + \frac{1}{9}$$

$$\frac{1}{C} = \frac{3}{9} \cdot \frac{1}{3}$$

$$C = 3 \text{ pF}$$

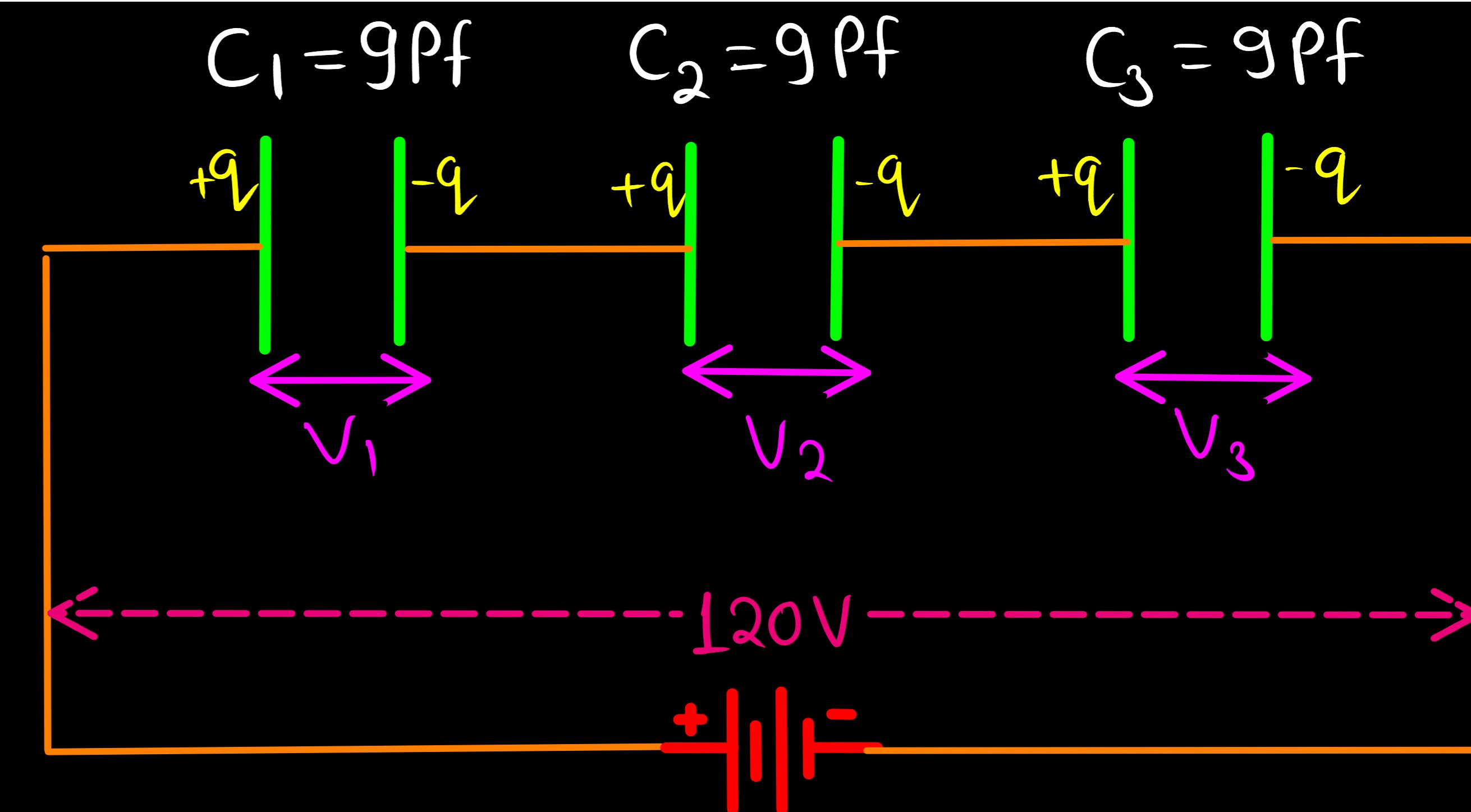

* b)

Charge stored by all Capacitors -

$$q_{V_1} = q_{V_2} = q_{V_3} = q \rightarrow (\text{In series } q \text{ - same})$$

$$q = CV = 3 \times 10^{-12} \times 120$$

2.6 Three capacitors each of capacitance 9 pF are connected in series.

- (a) What is the total capacitance of the combination?
- (b) What is the potential difference across each capacitor if the combination is connected to a 120 V supply?


* (a)

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C} = \frac{1}{9} + \frac{1}{9} + \frac{1}{9}$$

$$\frac{1}{C} = \frac{3}{9} \cdot \frac{1}{3}$$

$$C = 3 \text{ pF}$$

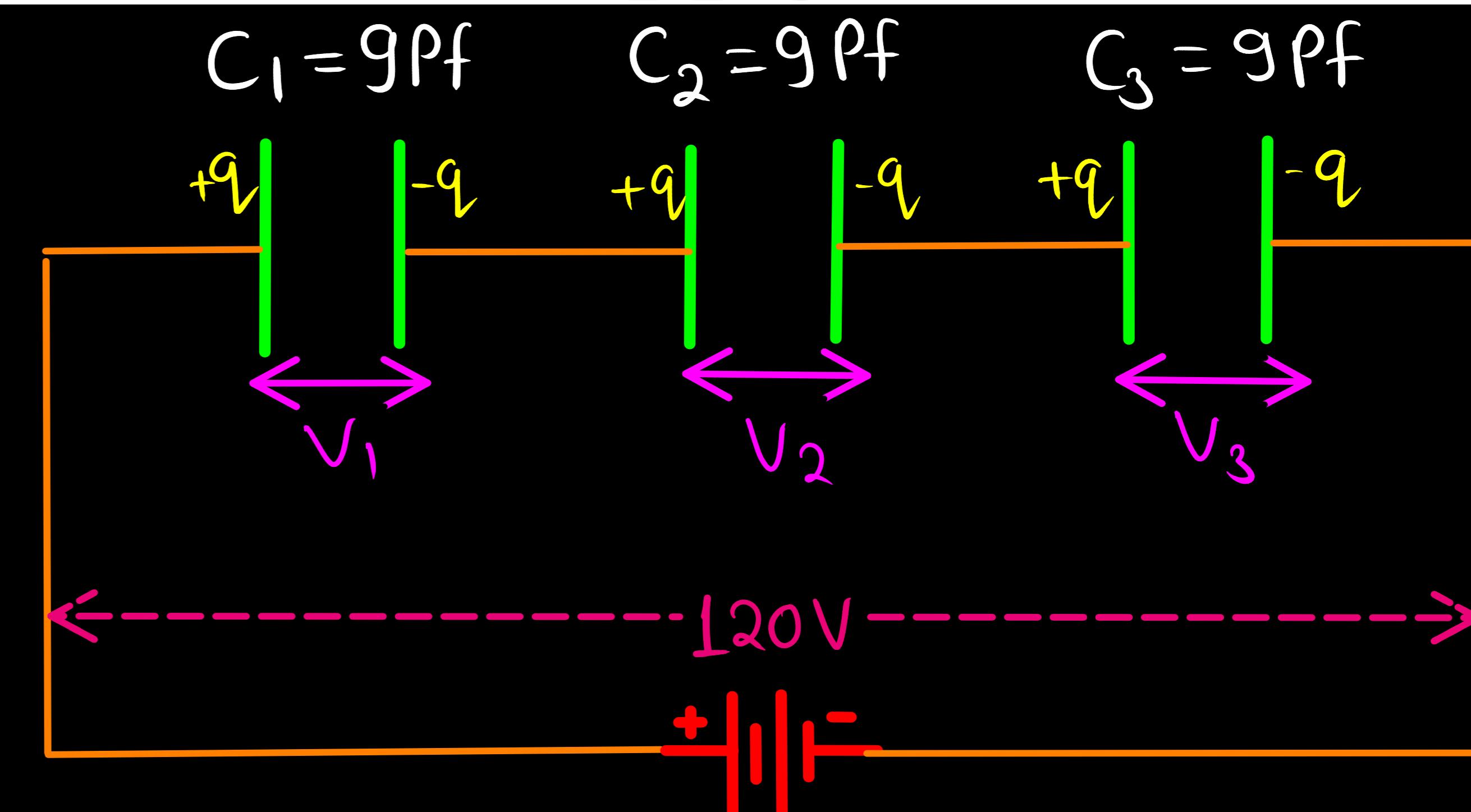

* b)

Charge stored by all Capacitors -

$$q_{V_1} = q_{V_2} = q_{V_3} = q \rightarrow (\text{In series } q \text{ - same})$$

$$q = CV = 3 \times 10^{-12} \times 120$$

$$q = 360 \times 10^{-12} \text{ C}$$

2.6 Three capacitors each of capacitance 9 pF are connected in series.

- (a) What is the total capacitance of the combination?
(b) What is the potential difference across each capacitor if the combination is connected to a 120 V supply?

*(a)

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C} = \frac{1}{9} + \frac{1}{9} + \frac{1}{9}$$

$$\frac{1}{C} = \frac{3}{9} \cdot \frac{1}{3}$$

$$C = 3 \text{ pF}$$

* b)


Charge stored by all Capacitors -

$$q_{V_1} = q_{V_2} = q_{V_3} = q \rightarrow (\text{In series } q \text{ - same})$$

$$q = CV = 3 \times 10^{-12} \times 120$$

$$q = 360 \times 10^{-12} \text{ C}$$
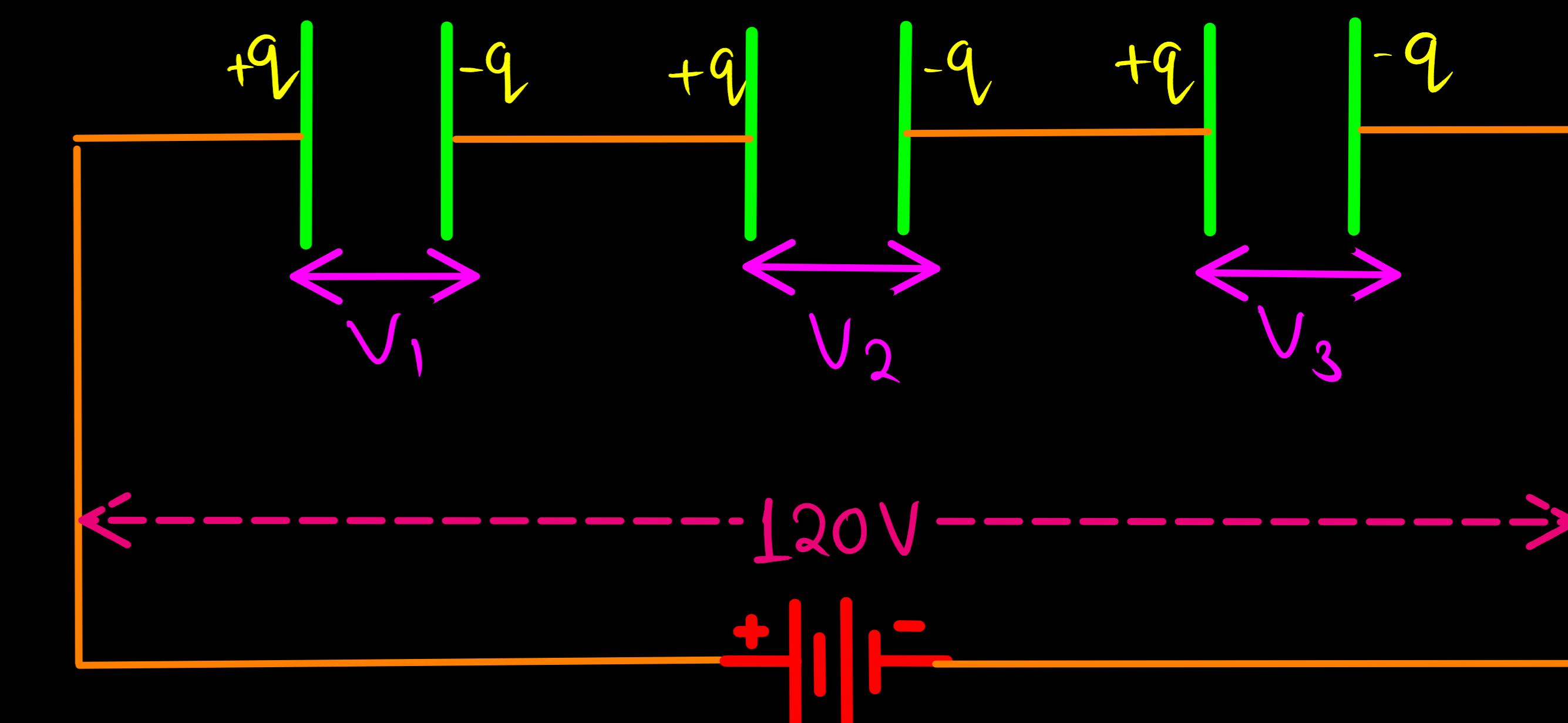
$$C_1 = 9 \text{ pF} \quad C_2 = 9 \text{ pF} \quad C_3 = 9 \text{ pF}$$



$$V_1 = \frac{q_1}{C_1} = \frac{q}{C}$$

2.6 Three capacitors each of capacitance 9 pF are connected in series.

- (a) What is the total capacitance of the combination?
- (b) What is the potential difference across each capacitor if the combination is connected to a 120 V supply?

*(a)

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C} = \frac{1}{9} + \frac{1}{9} + \frac{1}{9}$$

$$\frac{1}{C} = \frac{3}{9} \cdot \frac{1}{3}$$

$$C = 3 \text{ pF}$$

* b)


Charge stored by all Capacitors -

$$q_{V_1} = q_{V_2} = q_{V_3} = q \rightarrow (\text{In series } q \text{ - same})$$

$$q = C V = 3 \times 10^{-12} \times 120$$

$$q = 360 \times 10^{-12} \text{ C}$$
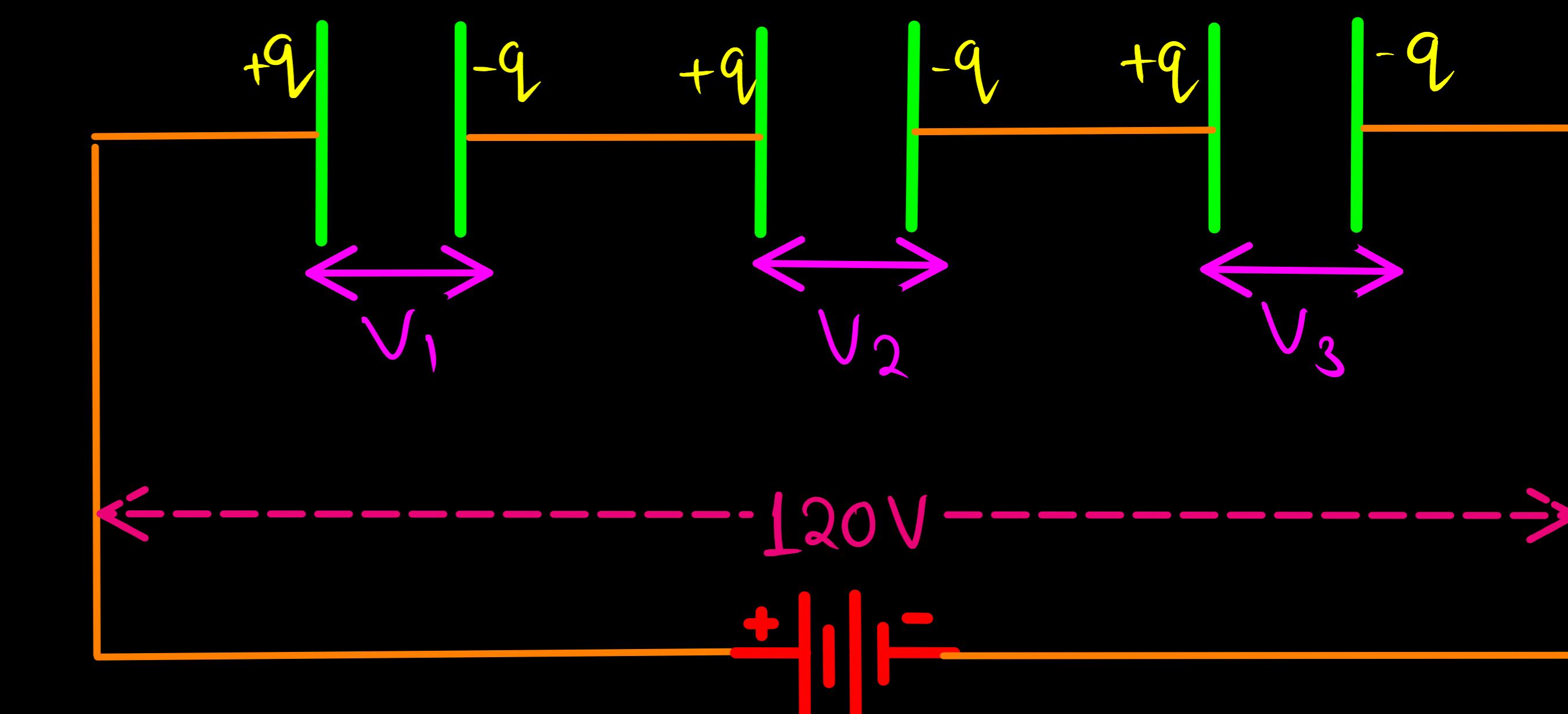
$$C_1 = 9 \text{ pF} \quad C_2 = 9 \text{ pF} \quad C_3 = 9 \text{ pF}$$



$$V_1 = \frac{q_{V_1}}{C_1} = \frac{q}{C_1}$$

$$V_1 = \frac{360 \times 10^{-12}}{9 \times 10^{-12}}$$

2.6 Three capacitors each of capacitance 9 pF are connected in series.

- (a) What is the total capacitance of the combination?
(b) What is the potential difference across each capacitor if the combination is connected to a 120 V supply?

*(a)

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C} = \frac{1}{9} + \frac{1}{9} + \frac{1}{9}$$

$$\frac{1}{C} = \frac{3}{9} \cdot \frac{1}{3}$$

$$C = 3 \text{ pF}$$

* b)


Charge stored by all Capacitors -

$$q_{V_1} = q_{V_2} = q_{V_3} = q \rightarrow (\text{In series } q \text{ - same})$$

$$q = CV = 3 \times 10^{-12} \times 120$$

$$q = 360 \times 10^{-12} \text{ C}$$
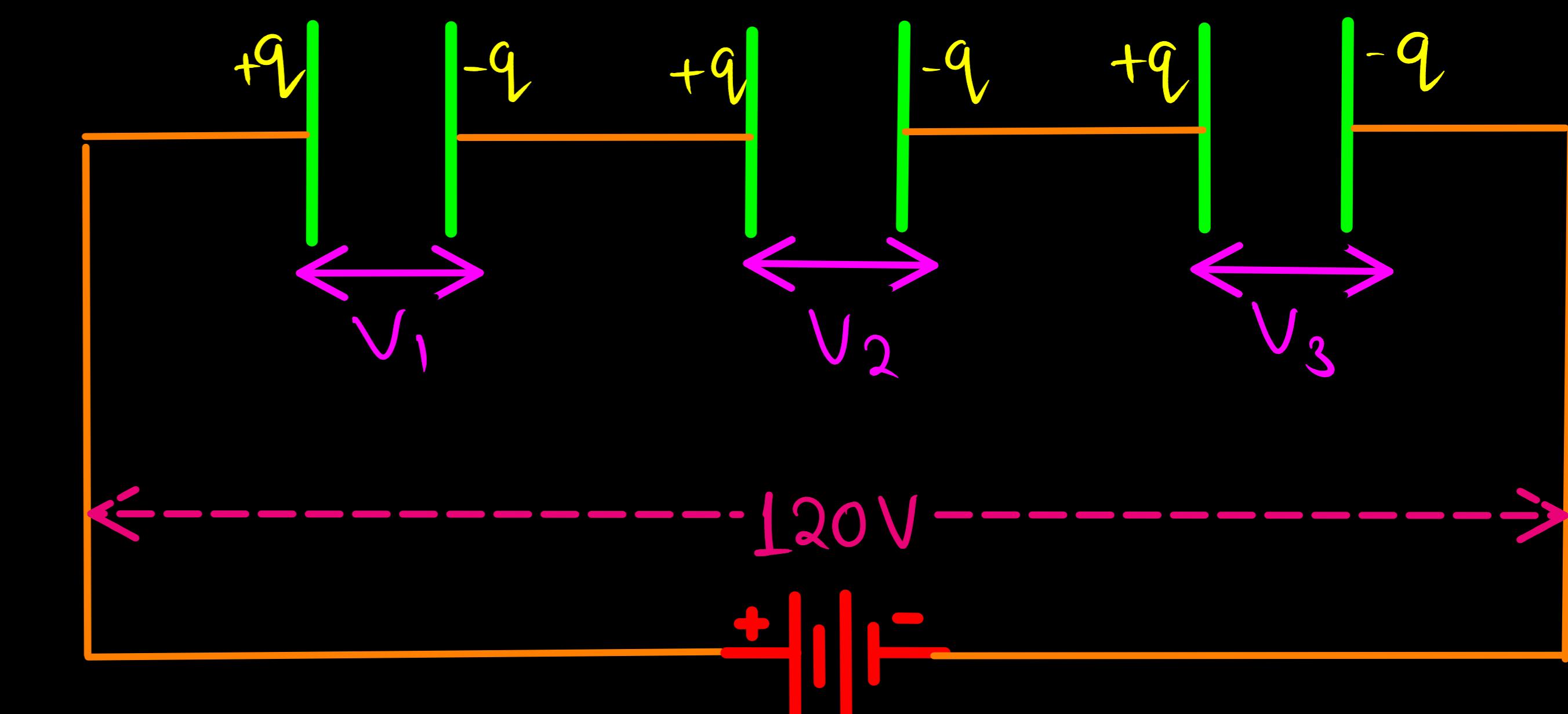
$$C_1 = 9 \text{ pF} \quad C_2 = 9 \text{ pF} \quad C_3 = 9 \text{ pF}$$



$$V_1 = \frac{q_{V_1}}{C_1} = \frac{q}{C_1}$$

$$V_1 = \frac{360 \times 10^{-12}}{9 \times 10^{-12}}$$

$$V_1 = 40 \text{ V}$$


$$V_2 = V_3 = V_1 = 40 \text{ V}$$

2.7 Three capacitors of capacitances 2 pF, 3 pF and 4 pF are connected in parallel.

- (a) What is the total capacitance of the combination?
- (b) Determine the charge on each capacitor if the combination is connected to a 100 V supply.

2.7 Three capacitors of capacitances 2 pF, 3 pF and 4 pF are connected in parallel.

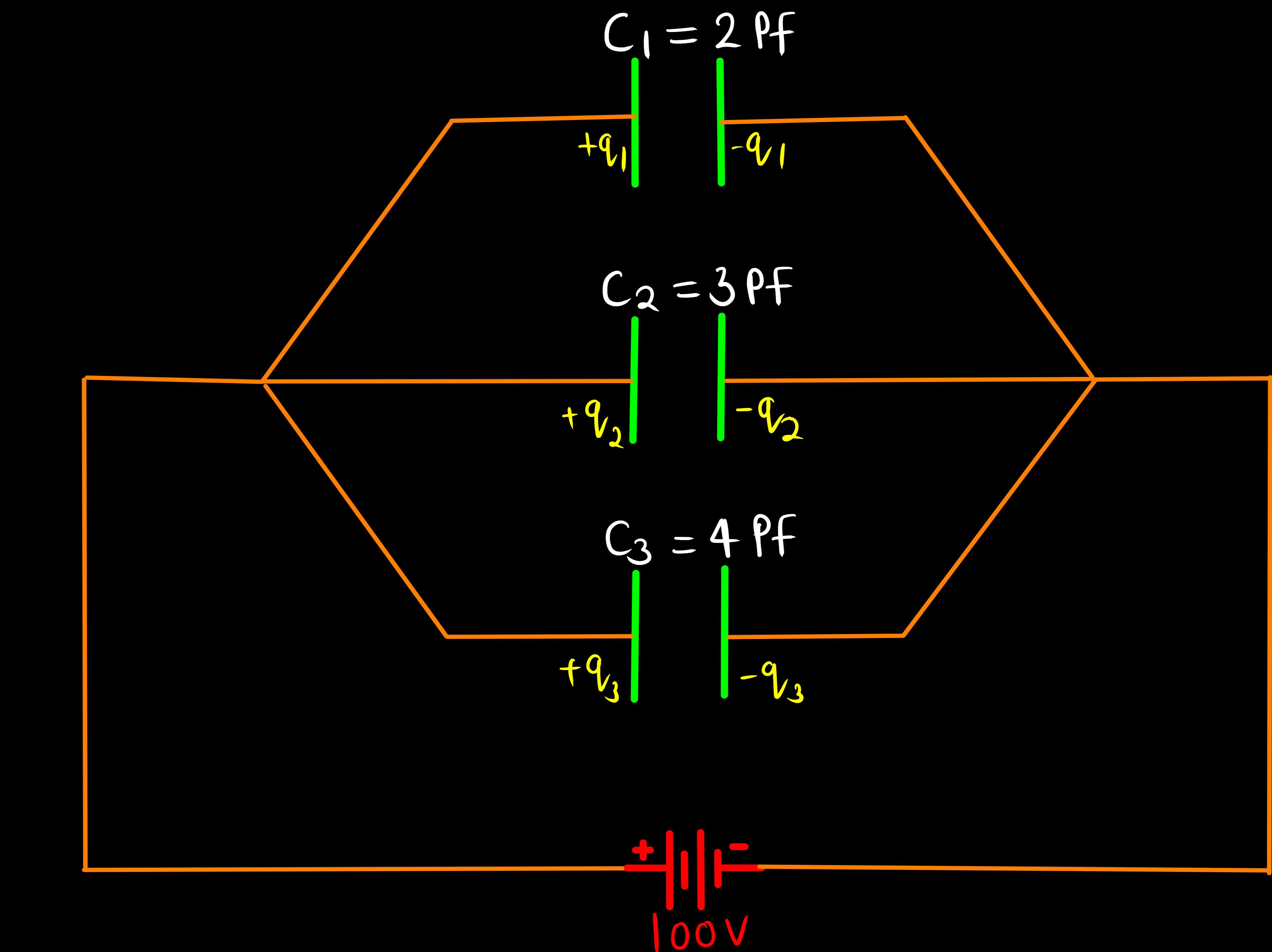
- (a) What is the total capacitance of the combination?
- (b) Determine the charge on each capacitor if the combination is connected to a 100 V supply.



2.7 Three capacitors of capacitances 2 pF, 3 pF and 4 pF are connected in parallel.

- What is the total capacitance of the combination?
- Determine the charge on each capacitor if the combination is connected to a 100 V supply.

a) $C = C_1 + C_2 + C_3$

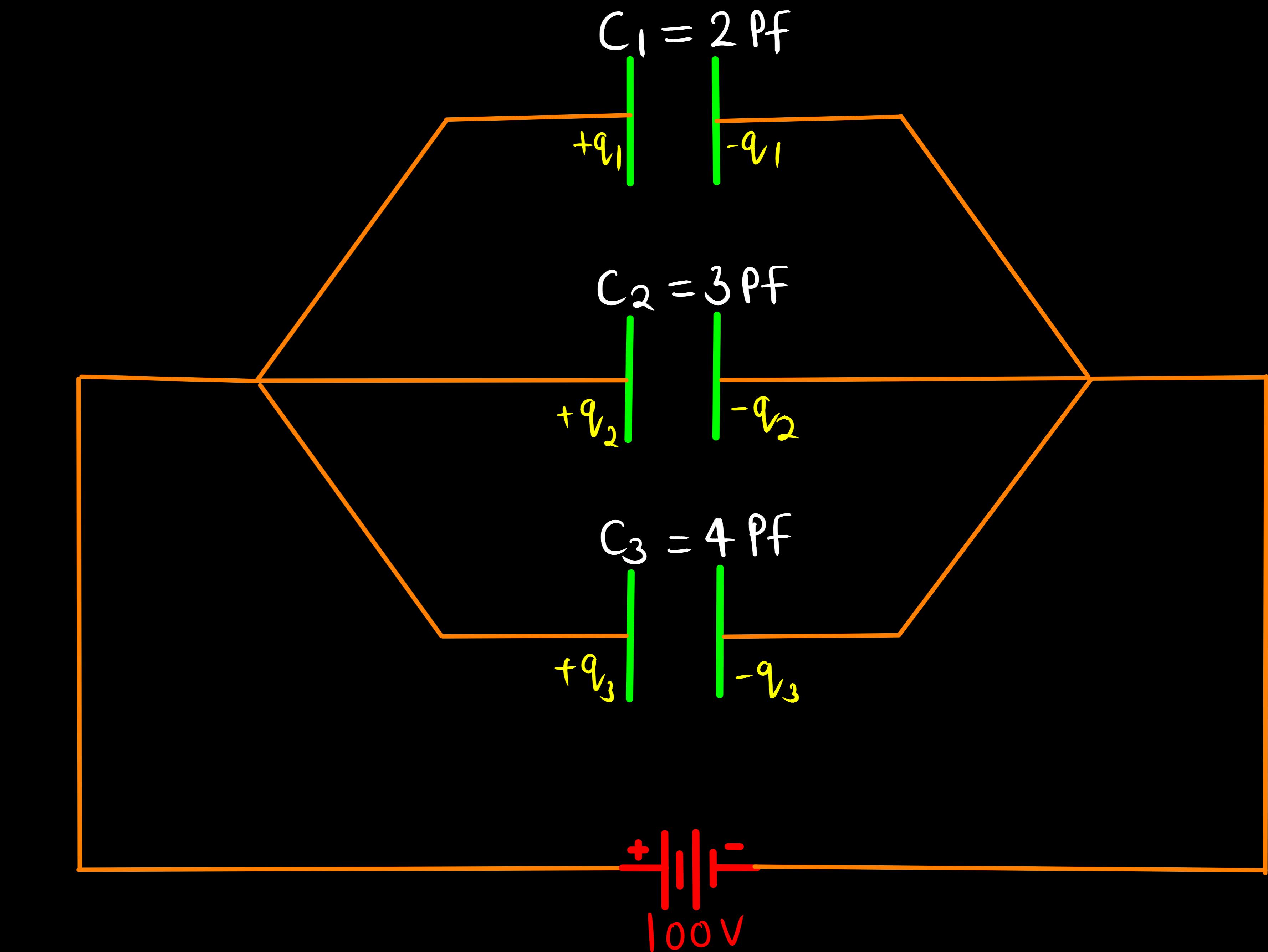

2.7 Three capacitors of capacitances 2 pF, 3 pF and 4 pF are connected in parallel.


- What is the total capacitance of the combination?
- Determine the charge on each capacitor if the combination is connected to a 100 V supply.

a)

$$C = C_1 + C_2 + C_3$$

$$C = 2 \text{ pF} + 3 \text{ pF} + 4 \text{ pF}$$

$$C = 9 \text{ pF}$$

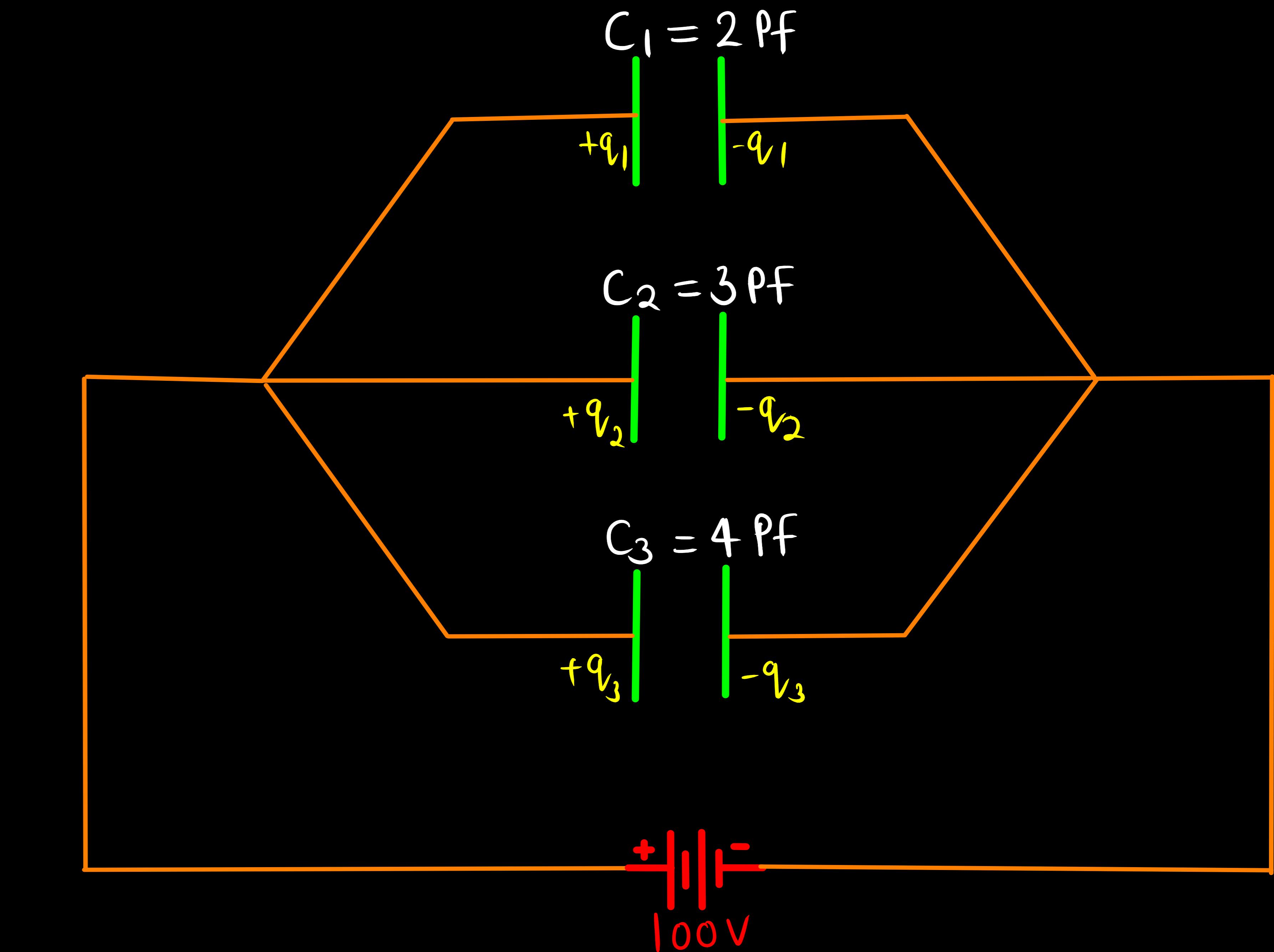

2.7 Three capacitors of capacitances 2 pF, 3 pF and 4 pF are connected in parallel.


- What is the total capacitance of the combination?
- Determine the charge on each capacitor if the combination is connected to a 100 V supply.

a) $C = C_1 + C_2 + C_3$

$$C = 2 \text{ pF} + 3 \text{ pF} + 4 \text{ pF}$$

$$\boxed{C = 9 \text{ pF}}$$

b) $q_1 = C_1 V$

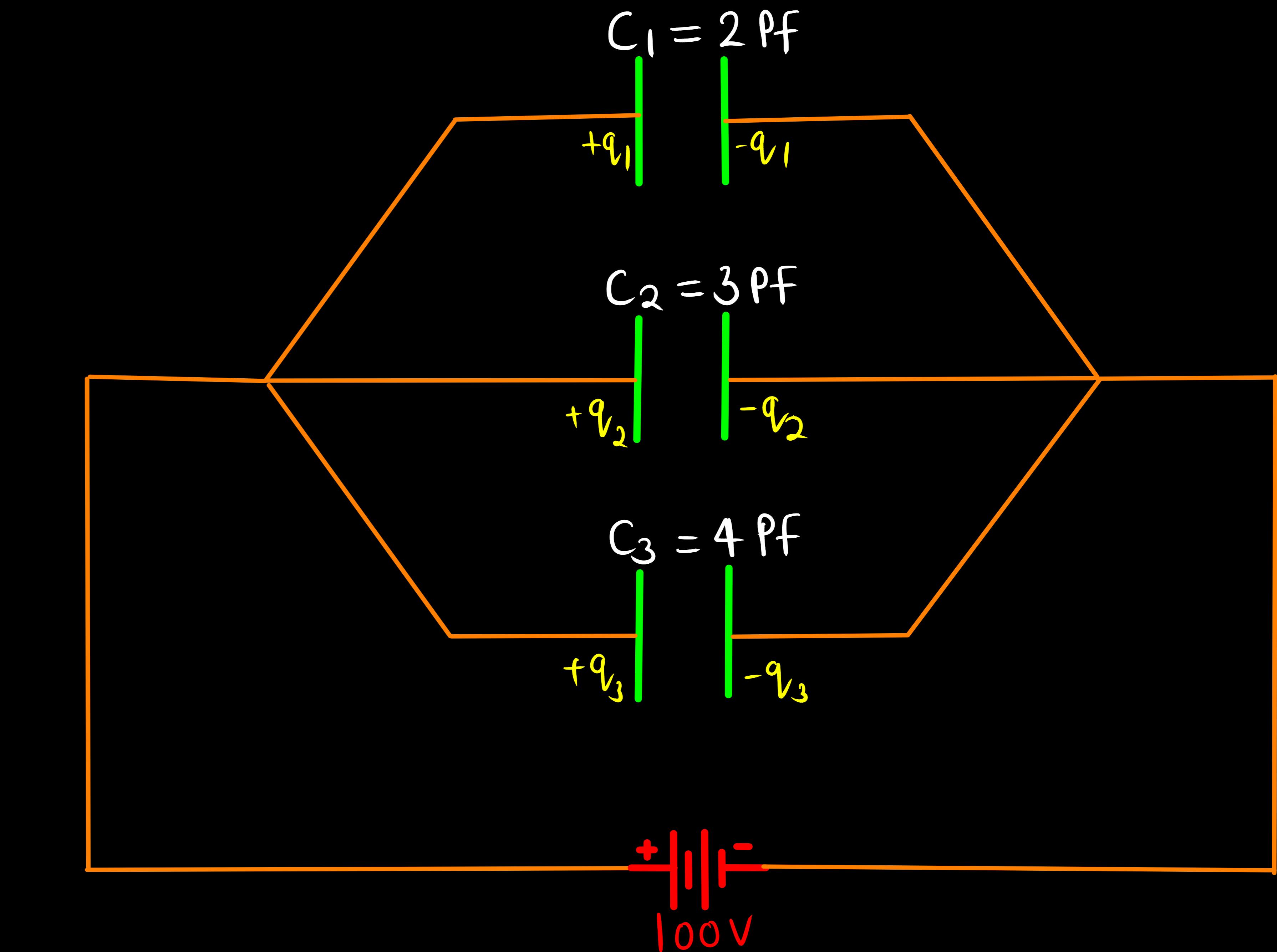

2.7 Three capacitors of capacitances 2 pF, 3 pF and 4 pF are connected in parallel.

- What is the total capacitance of the combination?
- Determine the charge on each capacitor if the combination is connected to a 100 V supply.

a) $C = C_1 + C_2 + C_3$


$$C = 2 \text{ pF} + 3 \text{ pF} + 4 \text{ pF}$$

$$C = 9 \text{ pF}$$

b) $q_1 = C_1 V$

$$q_1 = 2 \times 10^{-12} \times 100$$

$$q_1 = 2 \times 10^{-10} \text{ C}$$

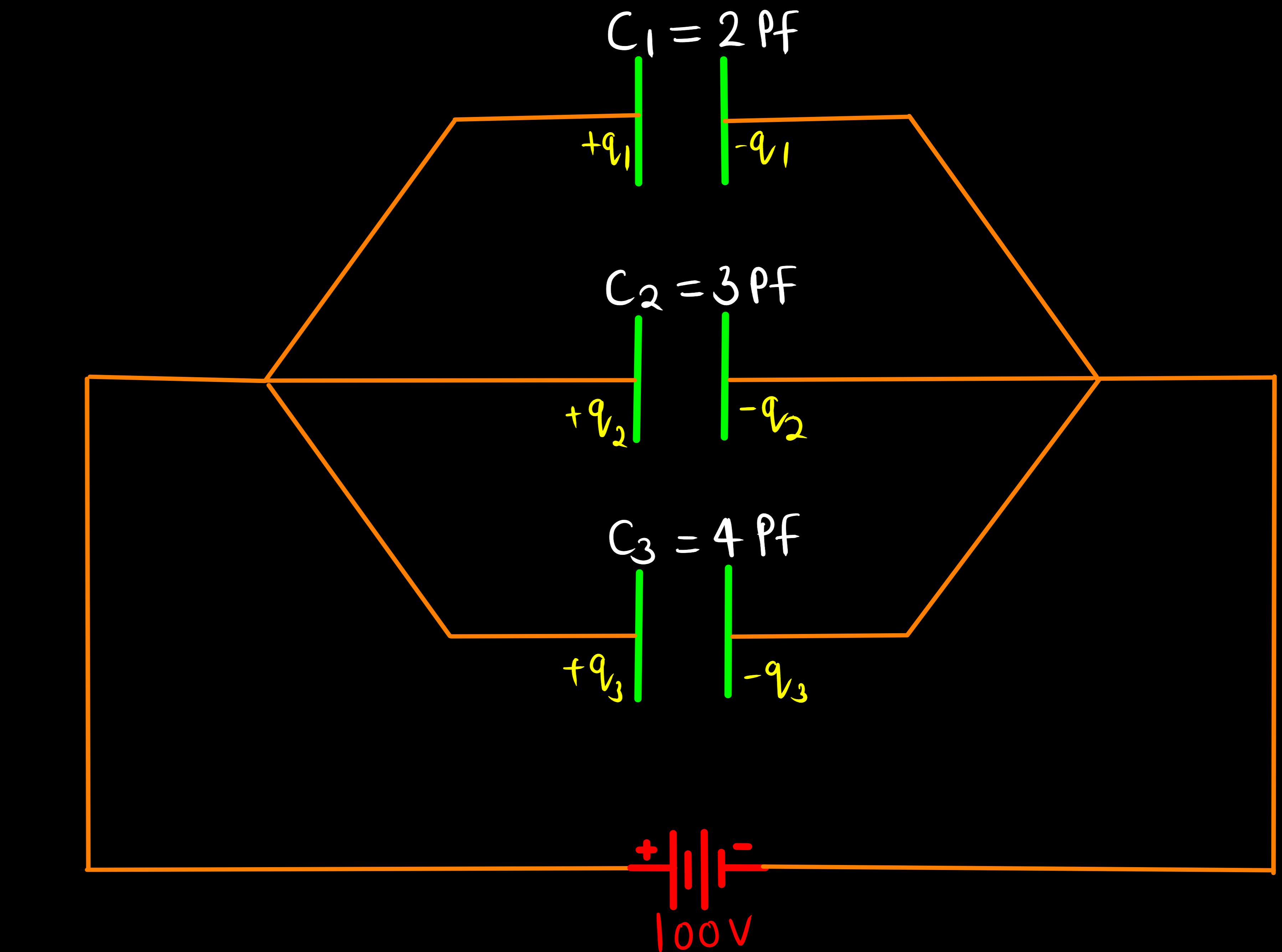

2.7 Three capacitors of capacitances 2 pF, 3 pF and 4 pF are connected in parallel.

- What is the total capacitance of the combination?
- Determine the charge on each capacitor if the combination is connected to a 100 V supply.


a)

$$C = C_1 + C_2 + C_3$$
$$C = 2 \text{ pF} + 3 \text{ pF} + 4 \text{ pF}$$

$$C = 9 \text{ pF}$$

b)
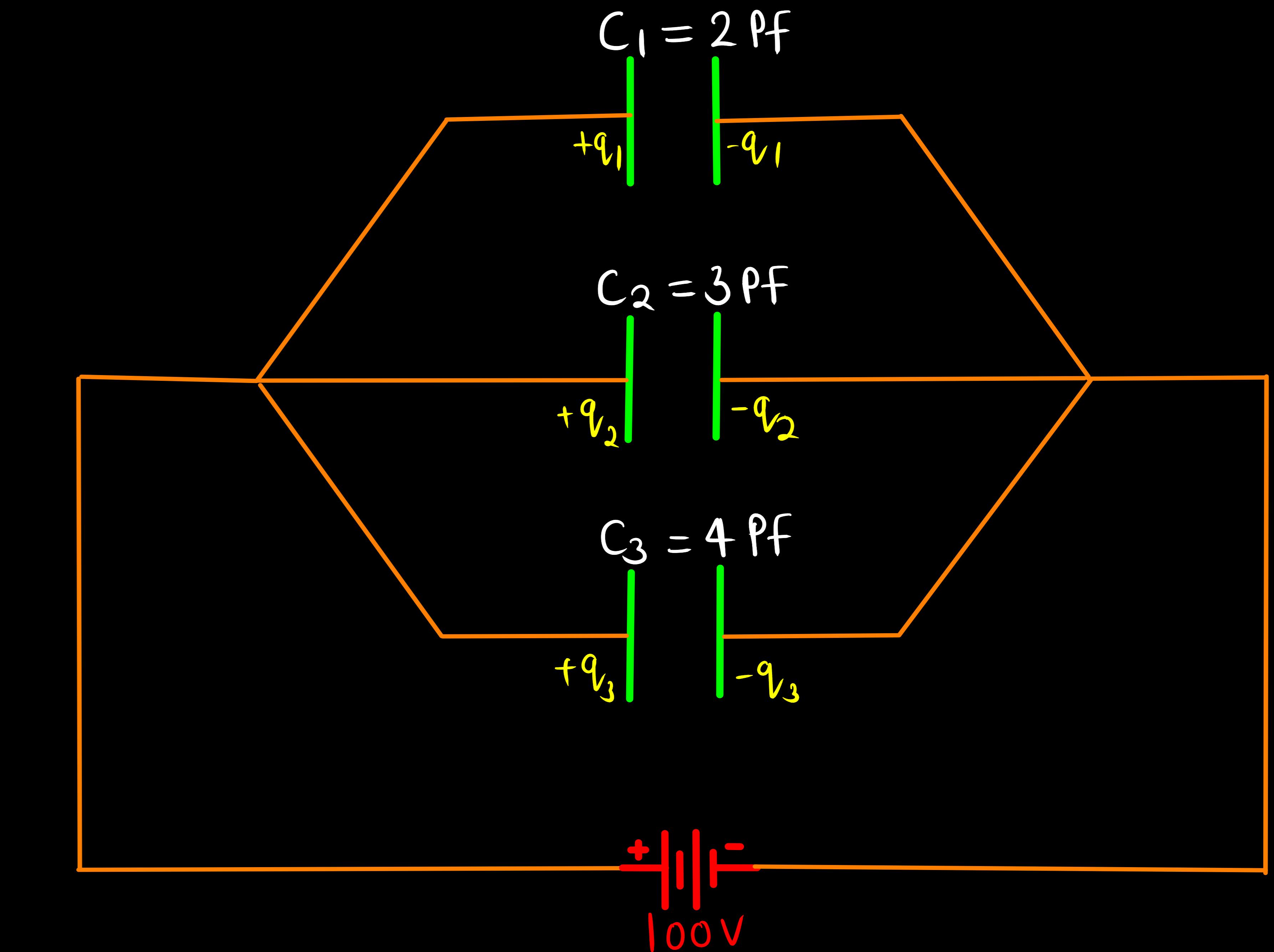
$$q_1 = C_1 V$$
$$q_1 = 2 \times 10^{-12} \times 100$$
$$q_1 = 2 \times 10^{-10} \text{ C}$$
$$q_2 = C_2 V$$
$$q_2 = 3 \times 10^{-12} \times 100 = 3 \times 10^{-10} \text{ C}$$



2.7 Three capacitors of capacitances 2 pF, 3 pF and 4 pF are connected in parallel.

- What is the total capacitance of the combination?
- Determine the charge on each capacitor if the combination is connected to a 100 V supply.

a) $C = C_1 + C_2 + C_3$

$$C = 2 \text{ pF} + 3 \text{ pF} + 4 \text{ pF}$$

$$\boxed{C = 9 \text{ pF}}$$

b) $q_1 = C_1 V$

$$q_1 = 2 \times 10^{-12} \times 100$$


$$\boxed{q_1 = 2 \times 10^{-10} \text{ C}}$$

$$q_2 = C_2 V$$


$$q_2 = 3 \times 10^{-12} \times 100 = 3 \times 10^{-10} \text{ C}$$

$$q_3 = C_3 V$$
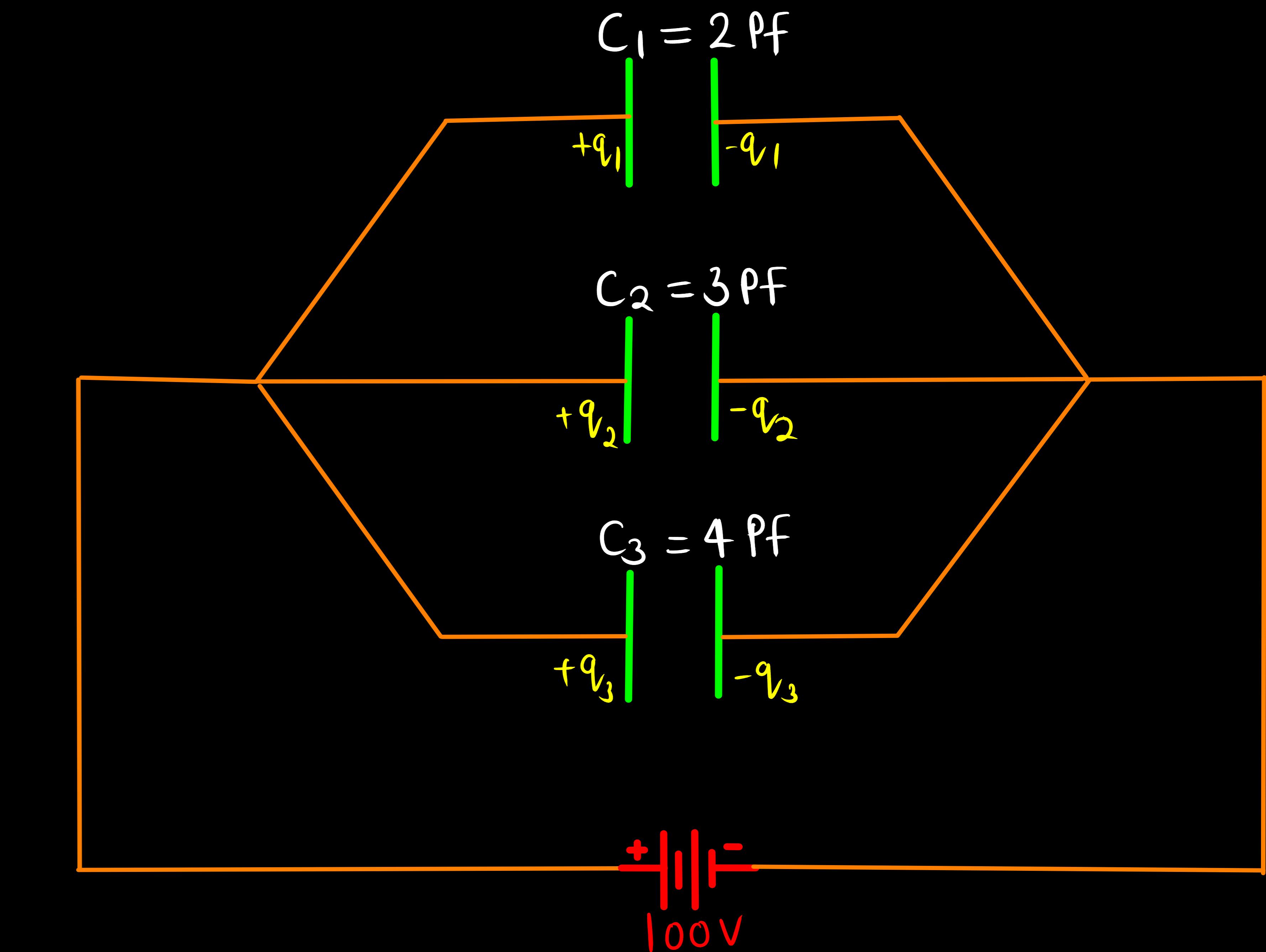
$$q_3 = 4 \times 10^{-12} \times 100 = 4 \times 10^{-10} \text{ C}$$




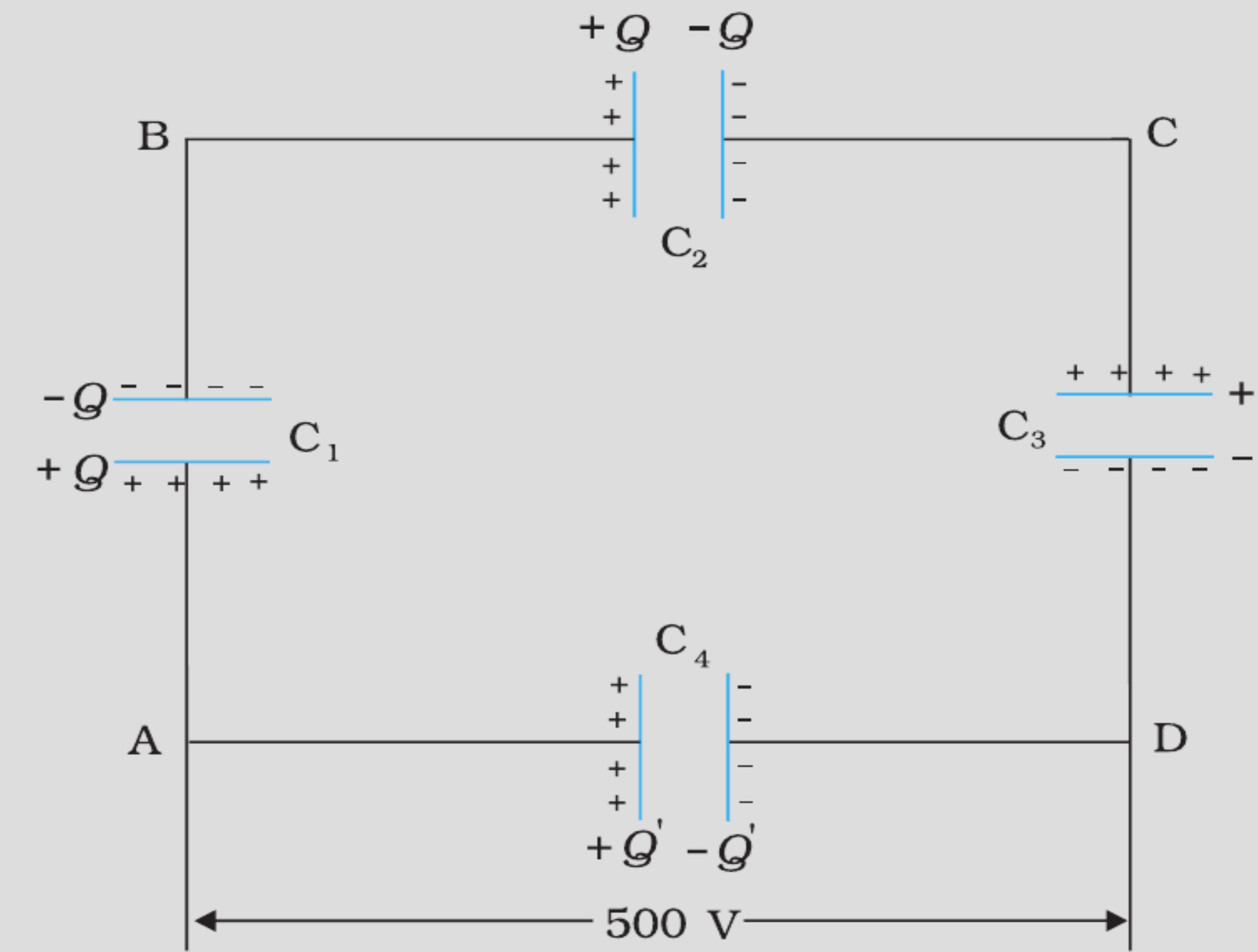Example 2.9 A network of four $10 \mu\text{F}$ capacitors is connected to a 500 V supply, as shown in Fig. 2.29. Determine (a) the equivalent capacitance of the network and (b) the charge on each capacitor. (Note, the *charge on a capacitor* is the charge on the plate with higher potential, equal and opposite to the charge on the plate with lower potential.)



a) C_1 , C_2 , and C_3 are in series-

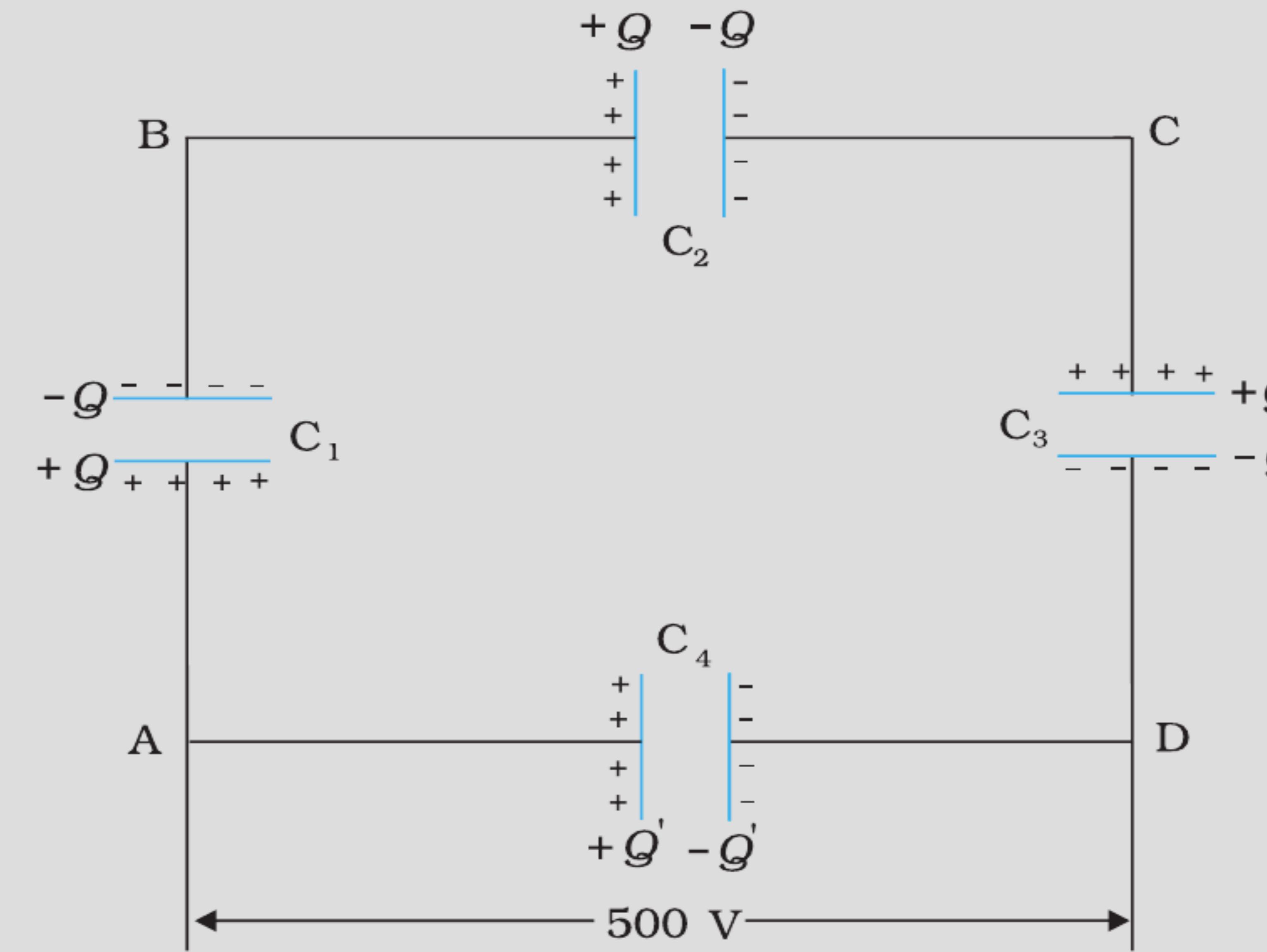Example 2.9 A network of four $10 \mu\text{F}$ capacitors is connected to a 500 V supply, as shown in Fig. 2.29. Determine (a) the equivalent capacitance of the network and (b) the charge on each capacitor. (Note, the *charge on a capacitor* is the charge on the plate with higher potential, equal and opposite to the charge on the plate with lower potential.)




a) C_1 , C_2 , and C_3 are in series-

$$\frac{1}{C'} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C'} = \frac{1}{10} + \frac{1}{10} + \frac{1}{10} = \frac{3}{10}$$

$$C' = \frac{10}{3} \mu\text{F}$$

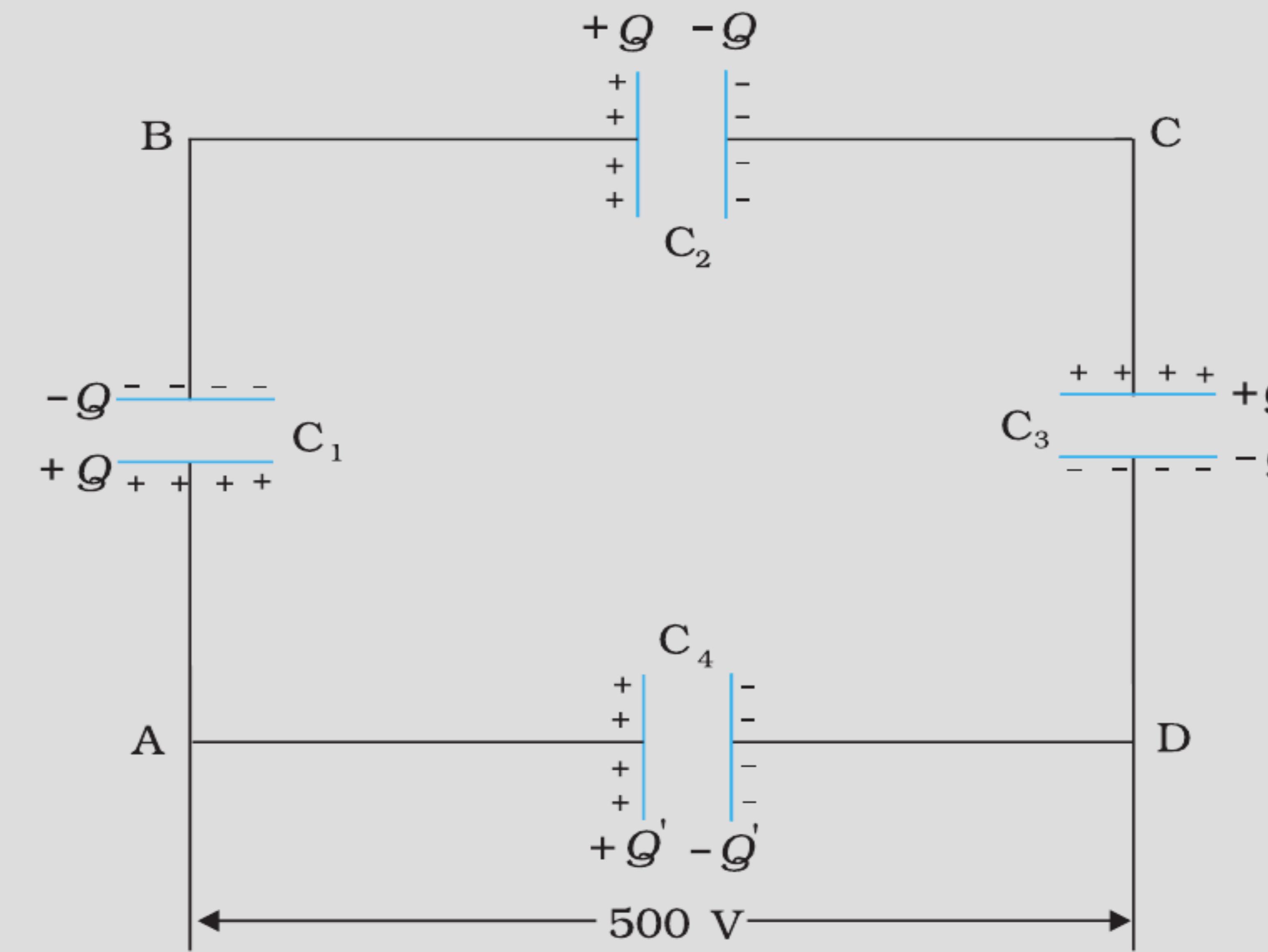Example 2.9 A network of four $10 \mu\text{F}$ capacitors is connected to a 500 V supply, as shown in Fig. 2.29. Determine (a) the equivalent capacitance of the network and (b) the charge on each capacitor. (Note, the *charge on a capacitor* is the charge on the plate with higher potential, equal and opposite to the charge on the plate with lower potential.)



a) C_1 , C_2 , and C_3 are in series-

$$\frac{1}{C'} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C'} = \frac{1}{10} + \frac{1}{10} + \frac{1}{10} = \frac{3}{10}$$

$$C' = \frac{10}{3} \mu\text{F}$$


Now, C' and C_4 are in parallel

$$C = C' + C_4$$

$$C = \left(\frac{10}{3} + 10\right) \mu\text{F}$$

$$C = \frac{40}{3} \mu\text{F}$$

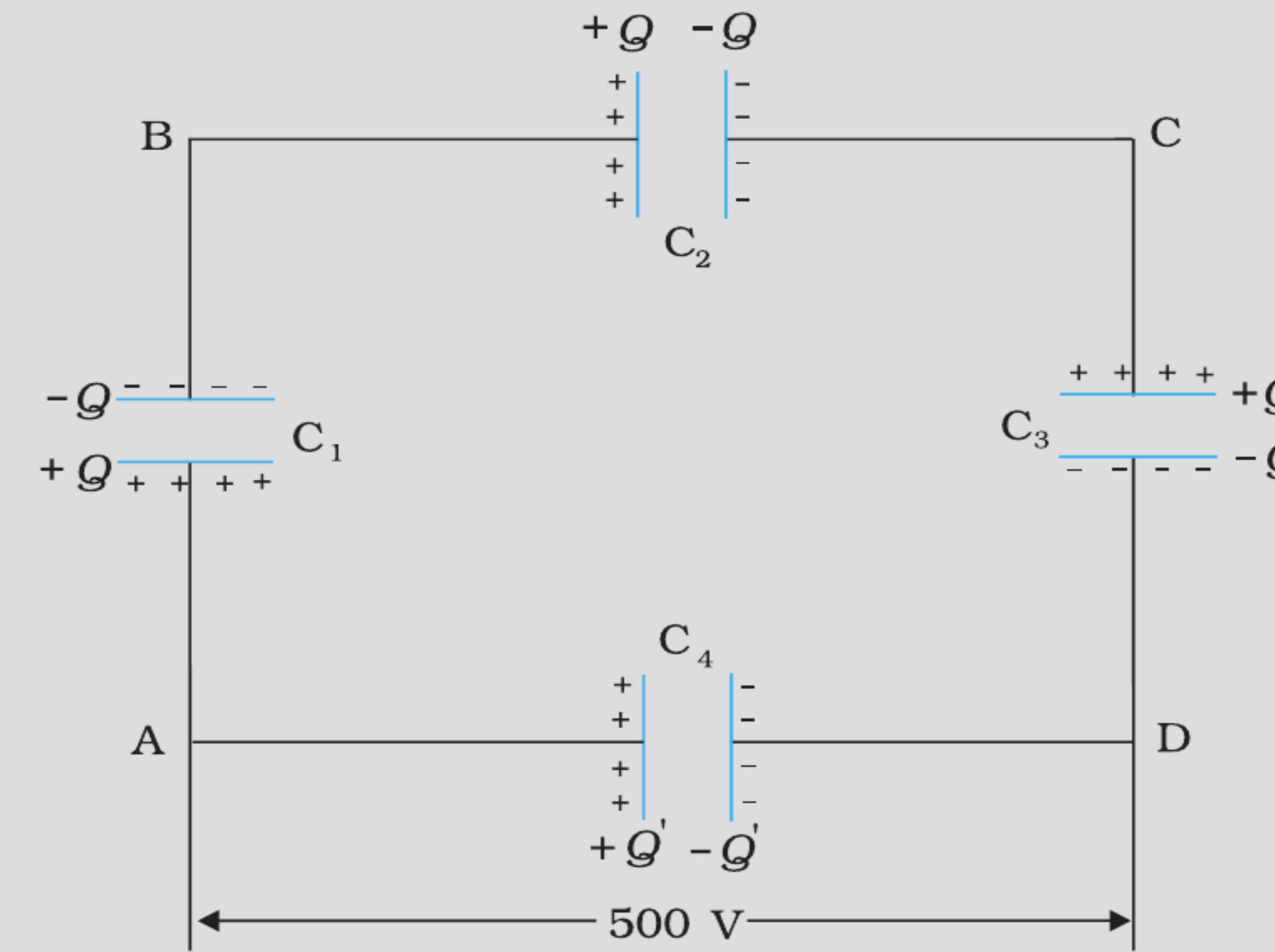Example 2.9 A network of four $10 \mu\text{F}$ capacitors is connected to a 500 V supply, as shown in Fig. 2.29. Determine (a) the equivalent capacitance of the network and (b) the charge on each capacitor. (Note, the *charge on a capacitor* is the charge on the plate with higher potential, equal and opposite to the charge on the plate with lower potential.)



a) C_1 , C_2 , and C_3 are in series-

$$\frac{1}{C'} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C'} = \frac{1}{10} + \frac{1}{10} + \frac{1}{10} = \frac{3}{10}$$

$$C' = \frac{10}{3} \mu\text{F}$$

Now, C' and C_4 are in parallel


$$C = C' + C_4$$

$$C = \left(\frac{10}{3} + 10\right) \mu\text{F}$$

$$C = \frac{40}{3} \mu\text{F}$$

b) $q_4 = C_4 V$

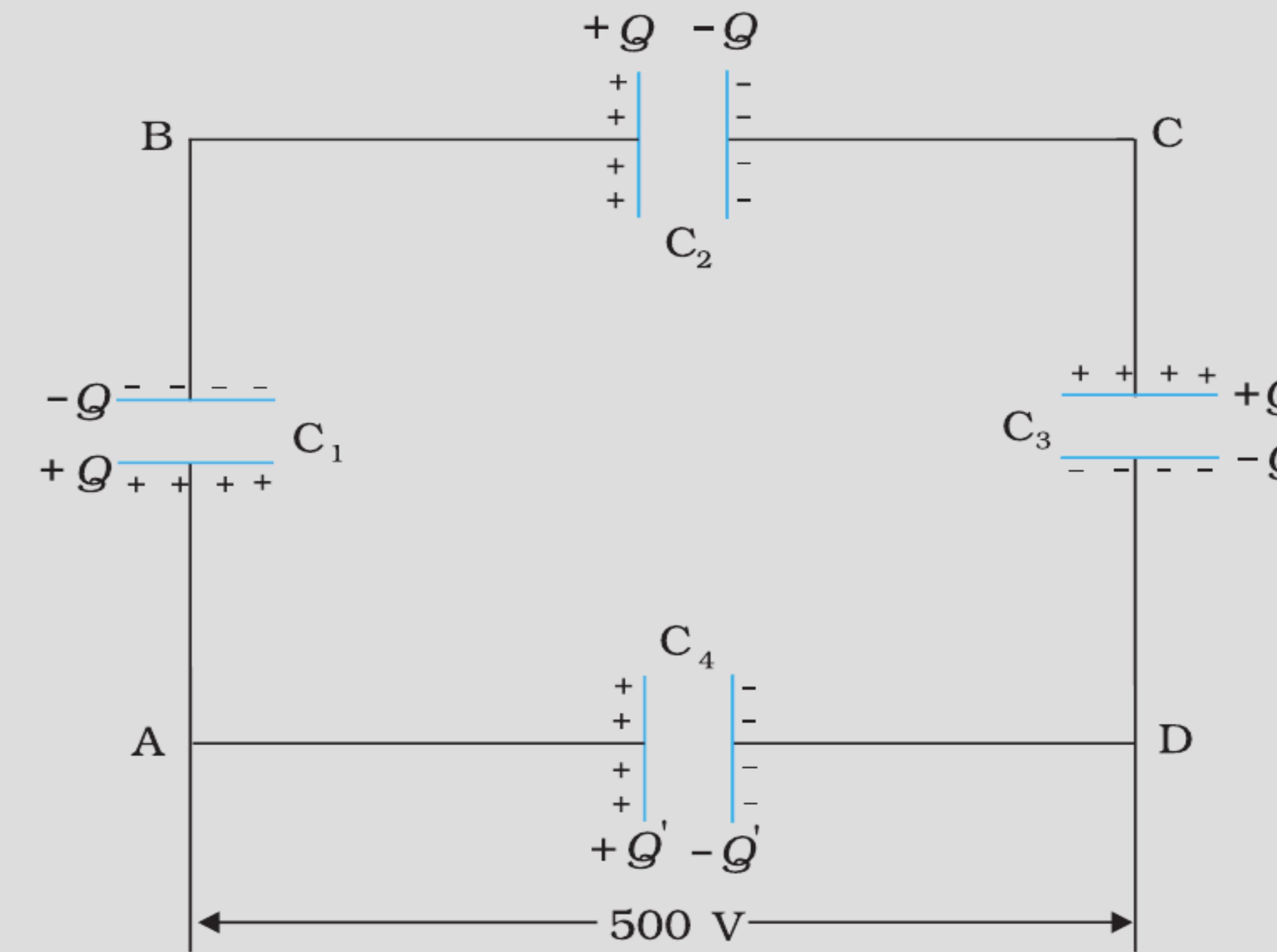Example 2.9 A network of four $10 \mu\text{F}$ capacitors is connected to a 500 V supply, as shown in Fig. 2.29. Determine (a) the equivalent capacitance of the network and (b) the charge on each capacitor. (Note, the *charge on a capacitor* is the charge on the plate with higher potential, equal and opposite to the charge on the plate with lower potential.)



a) C_1 , C_2 , and C_3 are in series-

$$\frac{1}{C'} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C'} = \frac{1}{10} + \frac{1}{10} + \frac{1}{10} = \frac{3}{10}$$

$$C' = \frac{10}{3} \mu\text{F}$$

Now, C' and C_4 are in parallel

$$C = C' + C_4$$

$$C = \left(\frac{10}{3} + 10\right) \mu\text{F}$$

$$C = \frac{40}{3} \mu\text{F}$$


b)

$$q_4 = C_4 V$$

$$q_4 = 10 \times 10^{-6} \times 500$$

$$q_4 = 5 \times 10^{-3} \text{ C}$$

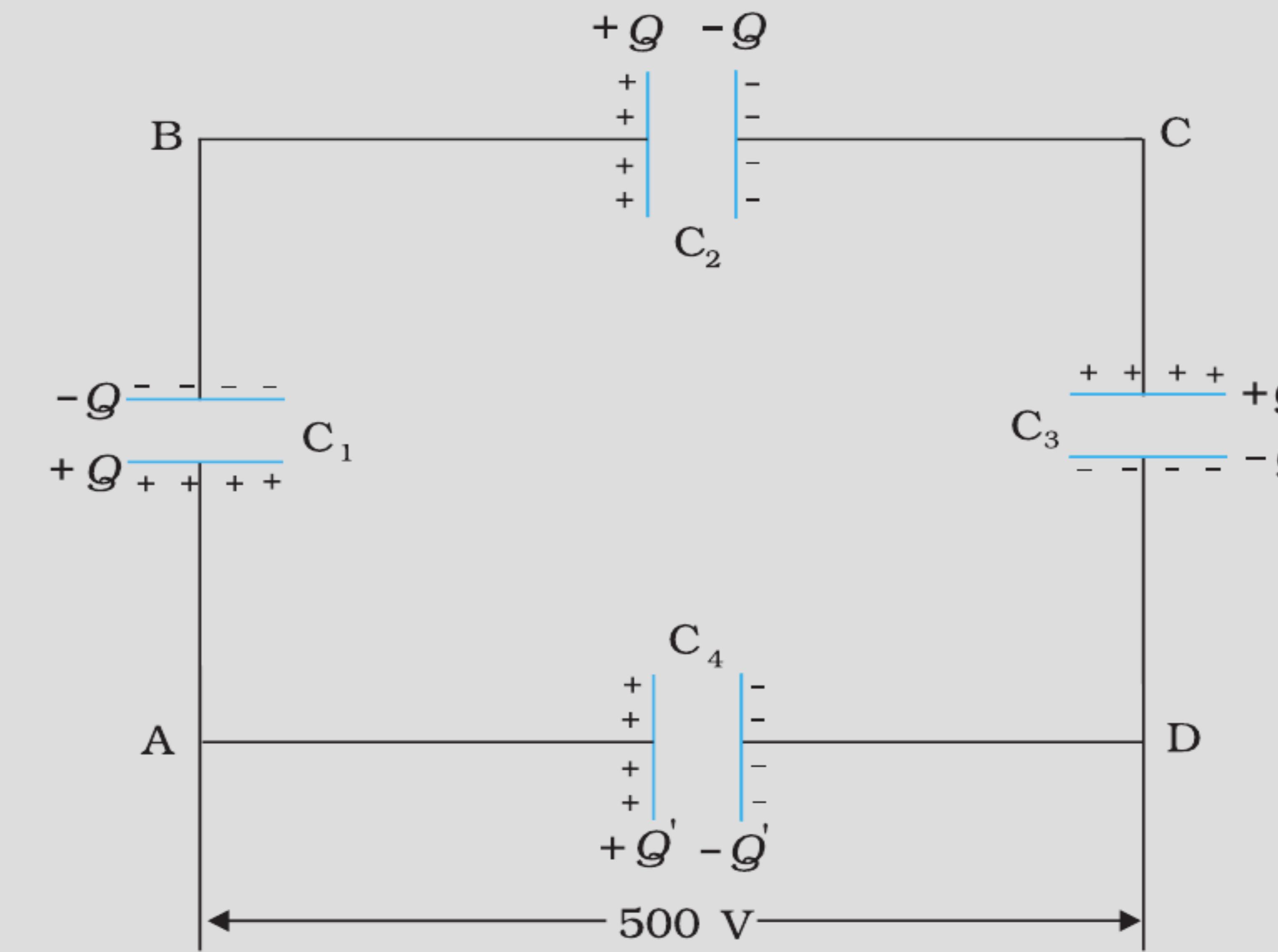Example 2.9 A network of four $10 \mu\text{F}$ capacitors is connected to a 500 V supply, as shown in Fig. 2.29. Determine (a) the equivalent capacitance of the network and (b) the charge on each capacitor. (Note, the *charge on a capacitor* is the charge on the plate with higher potential, equal and opposite to the charge on the plate with lower potential.)



a) C_1 , C_2 , and C_3 are in series-

$$\frac{1}{C'} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C'} = \frac{1}{10} + \frac{1}{10} + \frac{1}{10} = \frac{3}{10}$$

$$C' = \frac{10}{3} \mu\text{F}$$

Now, C' and C_4 are in parallel

$$C = C' + C_4$$

$$C = \left(\frac{10}{3} + 10\right) \mu\text{F}$$

$$C = \frac{40}{3} \mu\text{F}$$

b)


$$q_4 = C_4 V$$

$$q_4 = 10 \times 10^{-6} \times 500$$

$$q_4 = 5 \times 10^{-3} \text{ C}$$

$$V_1 + V_2 + V_3 = V$$

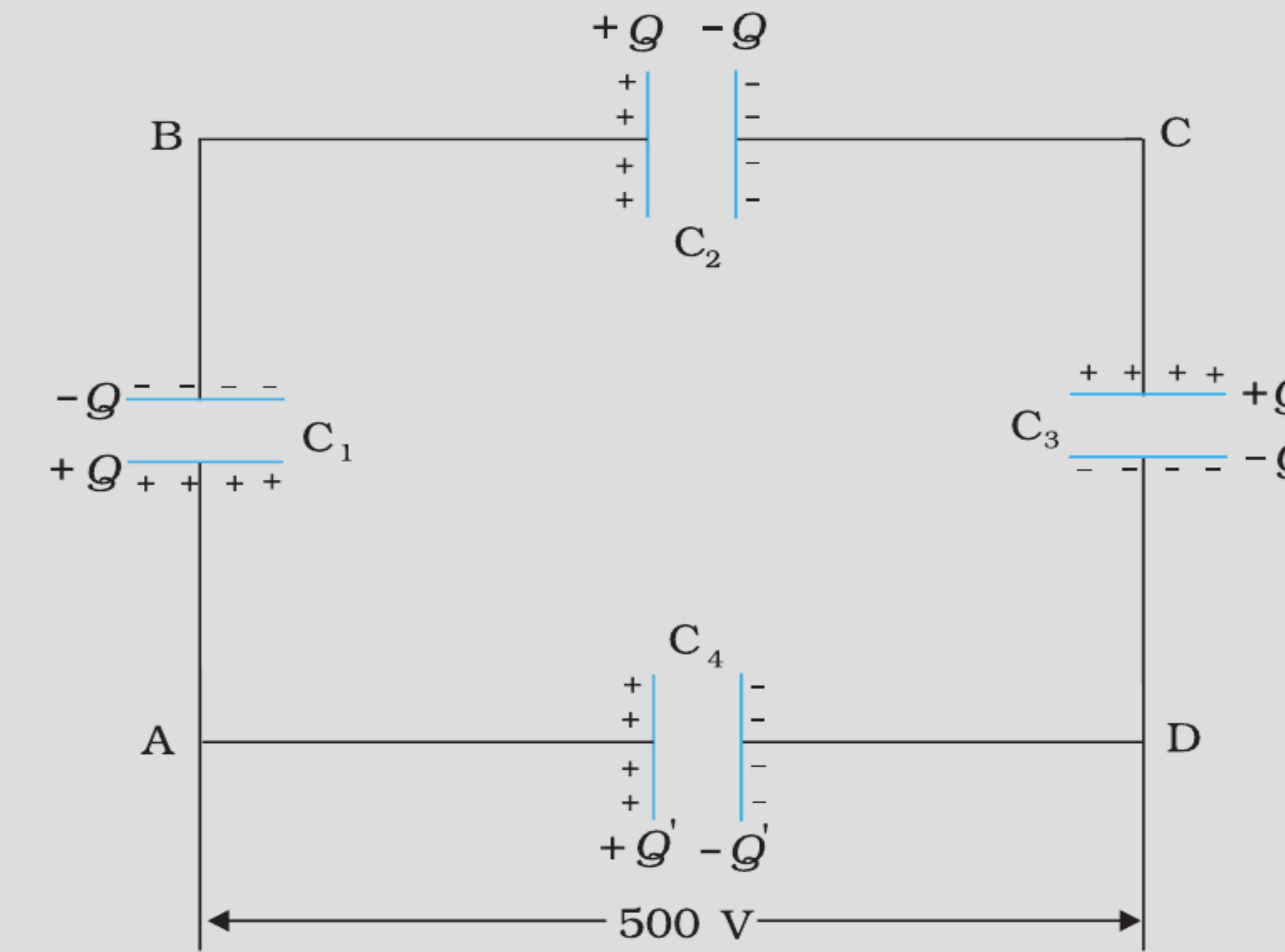Example 2.9 A network of four $10 \mu\text{F}$ capacitors is connected to a 500 V supply, as shown in Fig. 2.29. Determine (a) the equivalent capacitance of the network and (b) the charge on each capacitor. (Note, the *charge on a capacitor* is the charge on the plate with higher potential, equal and opposite to the charge on the plate with lower potential.)



a) C_1 , C_2 , and C_3 are in series-

$$\frac{1}{C'} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C'} = \frac{1}{10} + \frac{1}{10} + \frac{1}{10} = \frac{3}{10}$$

$$C' = \frac{10}{3} \mu\text{F}$$

Now, C' and C_4 are in parallel

$$C = C' + C_4$$

$$C = \left(\frac{10}{3} + 10\right) \mu\text{F}$$

$$C = \frac{40}{3} \mu\text{F}$$

b)

$$q_4 = C_4 V$$


$$q_4 = 10 \times 10^{-6} \times 500$$

$$q_4 = 5 \times 10^{-3} \text{ C}$$

$$V_1 + V_2 + V_3 = V$$

$$\frac{q_1}{C} + \frac{q_2}{C} + \frac{q_3}{C} = 500$$

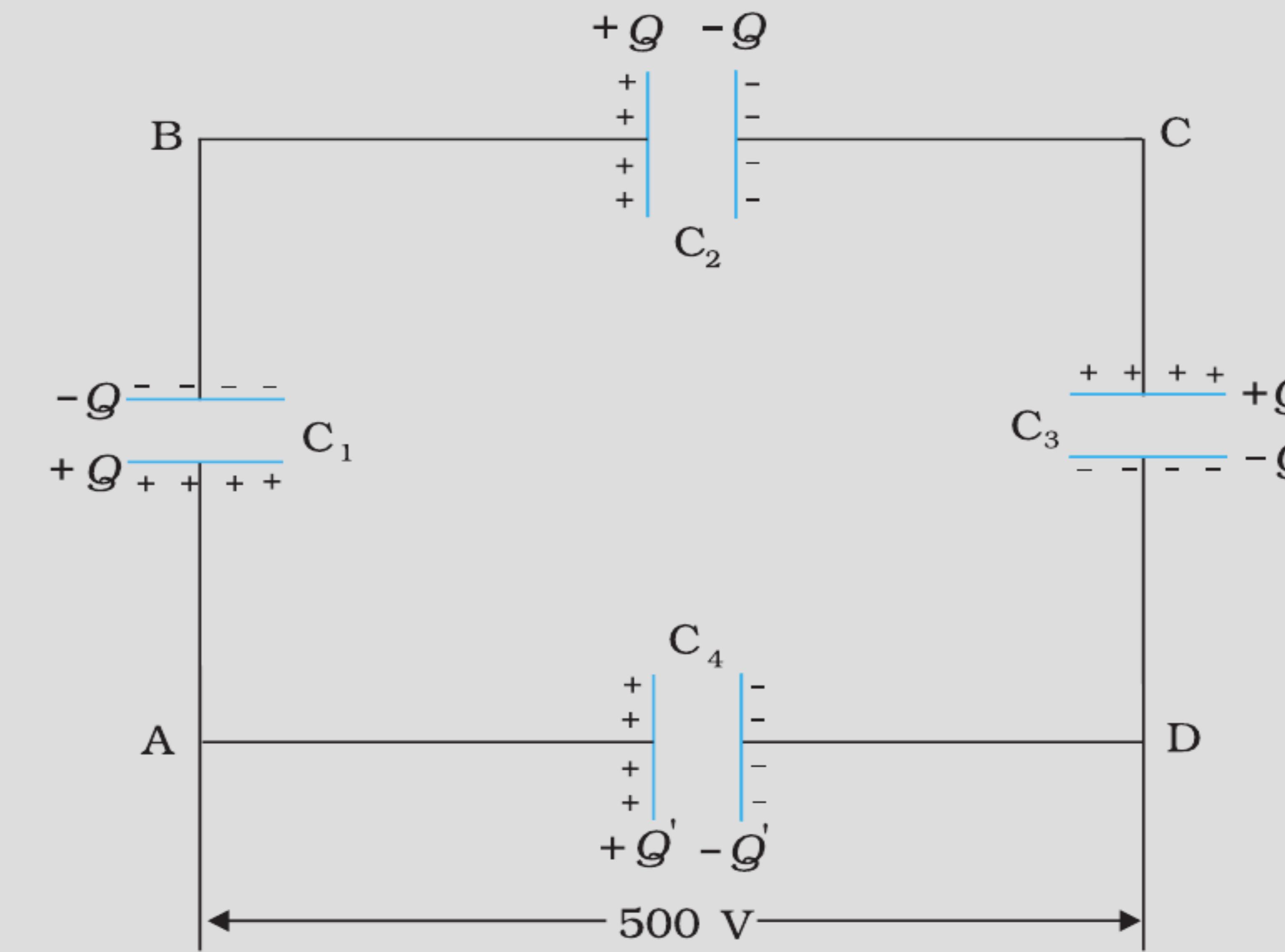Example 2.9 A network of four $10 \mu\text{F}$ capacitors is connected to a 500 V supply, as shown in Fig. 2.29. Determine (a) the equivalent capacitance of the network and (b) the charge on each capacitor. (Note, the *charge on a capacitor* is the charge on the plate with higher potential, equal and opposite to the charge on the plate with lower potential.)



a) C_1 , C_2 , and C_3 are in series-

$$\frac{1}{C'} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C'} = \frac{1}{10} + \frac{1}{10} + \frac{1}{10} = \frac{3}{10}$$

$$C' = \frac{10}{3} \mu\text{F}$$

Now, C' and C_4 are in parallel

$$C = C' + C_4$$

$$C = \left(\frac{10}{3} + 10\right) \mu\text{F}$$

$$C = \frac{40}{3} \mu\text{F}$$

b)

$$q_4 = C_4 V$$


$$q_4 = 10 \times 10^{-6} \times 500$$

$$q_4 = 5 \times 10^{-3} \text{ C}$$

$$V_1 + V_2 + V_3 = V$$

$$\frac{q_1}{C} + \frac{q_2}{C} + \frac{q_3}{C} = 500$$

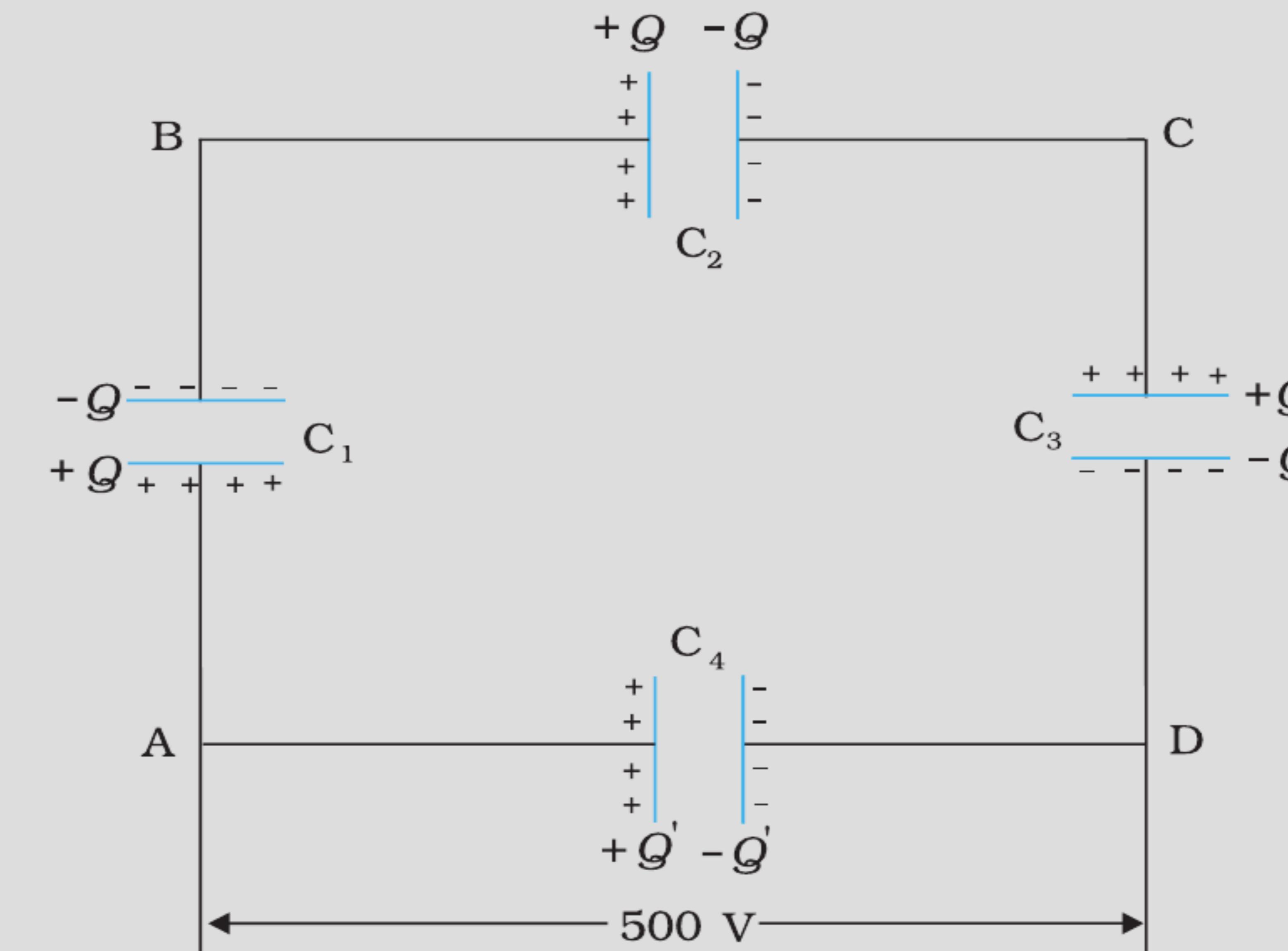Example 2.9 A network of four $10 \mu\text{F}$ capacitors is connected to a 500 V supply, as shown in Fig. 2.29. Determine (a) the equivalent capacitance of the network and (b) the charge on each capacitor. (Note, the *charge on a capacitor* is the charge on the plate with higher potential, equal and opposite to the charge on the plate with lower potential.)



$$\frac{3q}{C} = 500$$

$$q = \frac{500 \times C}{3} = \frac{500 \times 10 \times 10^{-6}}{3}$$

$$q = \frac{5}{3} \times 10^{-3} \text{ C}$$

a) C_1 , C_2 , and C_3 are in series-

$$\frac{1}{C'} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C'} = \frac{1}{10} + \frac{1}{10} + \frac{1}{10} = \frac{3}{10}$$

$$C' = \frac{10}{3} \mu\text{F}$$

Now, C' and C_4 are in parallel

$$C = C' + C_4$$

$$C = \left(\frac{10}{3} + 10\right) \mu\text{F}$$

$$C = \frac{40}{3} \mu\text{F}$$

b)

$$q_4 = C_4 V$$


$$q_4 = 10 \times 10^{-6} \times 500$$

$$q_4 = 5 \times 10^{-3} \text{ C}$$

$$V_1 + V_2 + V_3 = V$$

$$\frac{q_1}{C} + \frac{q_2}{C} + \frac{q_3}{C} = 500$$

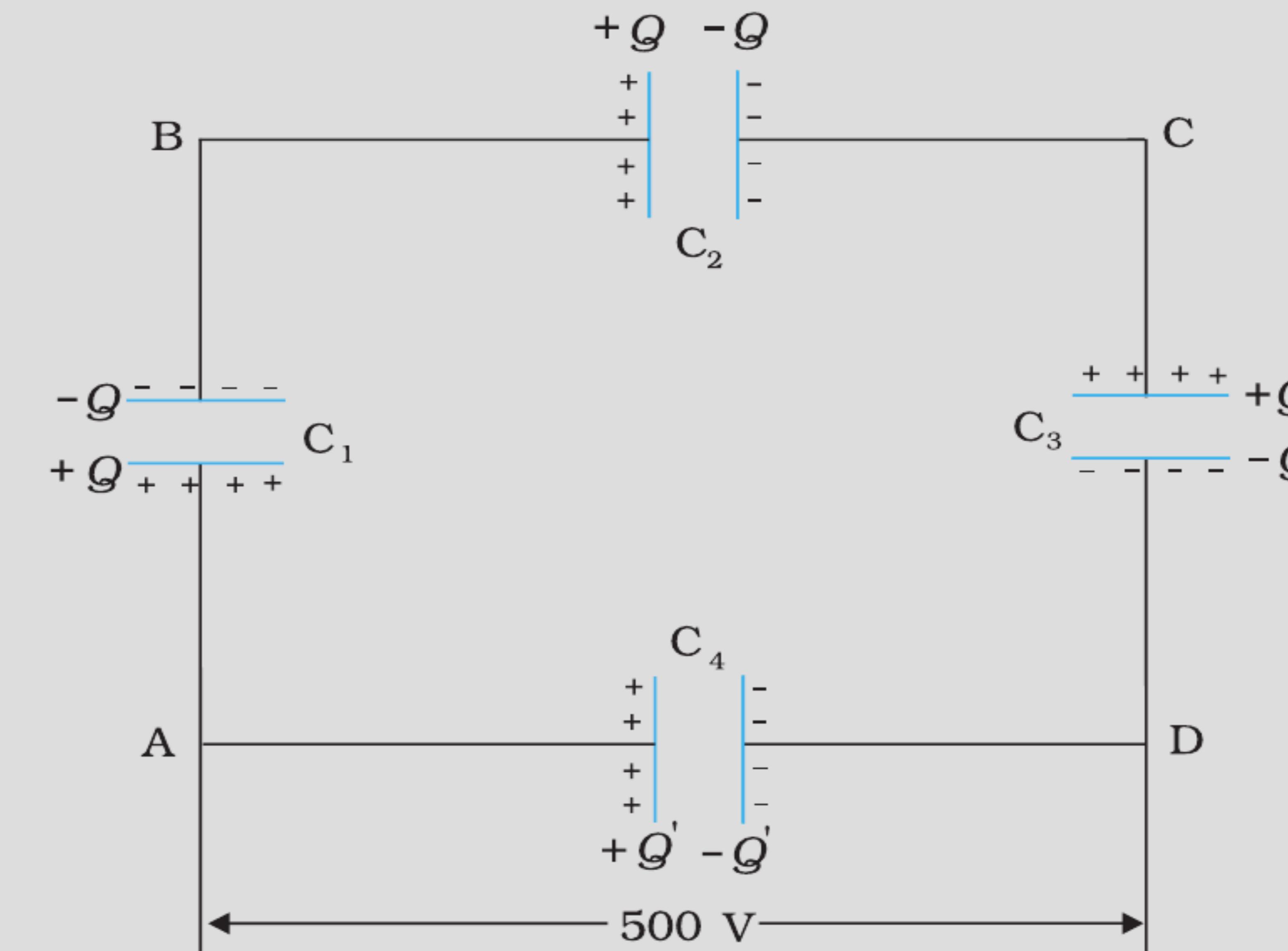Example 2.9 A network of four $10 \mu\text{F}$ capacitors is connected to a 500 V supply, as shown in Fig. 2.29. Determine (a) the equivalent capacitance of the network and (b) the charge on each capacitor. (Note, the *charge on a capacitor* is the charge on the plate with higher potential, equal and opposite to the charge on the plate with lower potential.)



$$\frac{3q}{C} = 500$$

$$q = \frac{500 \times C}{3} = \frac{500 \times 10 \times 10^{-6}}{3}$$

$$q = \frac{5}{3} \times 10^{-3} \text{ C}$$

$$q_1 = q_2 = q_3 = \frac{5}{3} \times 10^{-3} \text{ C}$$

2.10 A 12pF capacitor is connected to a 50V battery. How much electrostatic energy is stored in the capacitor?

2.10 A 12pF capacitor is connected to a 50V battery. How much electrostatic energy is stored in the capacitor?

$$C = 120 \text{ pF}, \quad V = 50 \text{ V}$$

2.10 A 12pF capacitor is connected to a 50V battery. How much electrostatic energy is stored in the capacitor?

$$C = 120 \text{ pF}, \quad V = 50 \text{ V}$$

$$U = \frac{1}{2} C V^2 \rightarrow \text{Energy stored in the capacitor}$$

2.10 A 12pF capacitor is connected to a 50V battery. How much electrostatic energy is stored in the capacitor?

$$C = 120 \text{ pF}, \quad V = 50 \text{ V}$$


$$U = \frac{1}{2} C V^2 \rightarrow \text{Energy stored in the capacitor}$$

$$U = \frac{1}{2} \times 120 \times 10^{-12} \times 50^2$$



$$U = 3 \times 10^{-3} \text{ J}$$

2.11 A 600pF capacitor is charged by a 200V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. How much electrostatic energy is lost in the process?

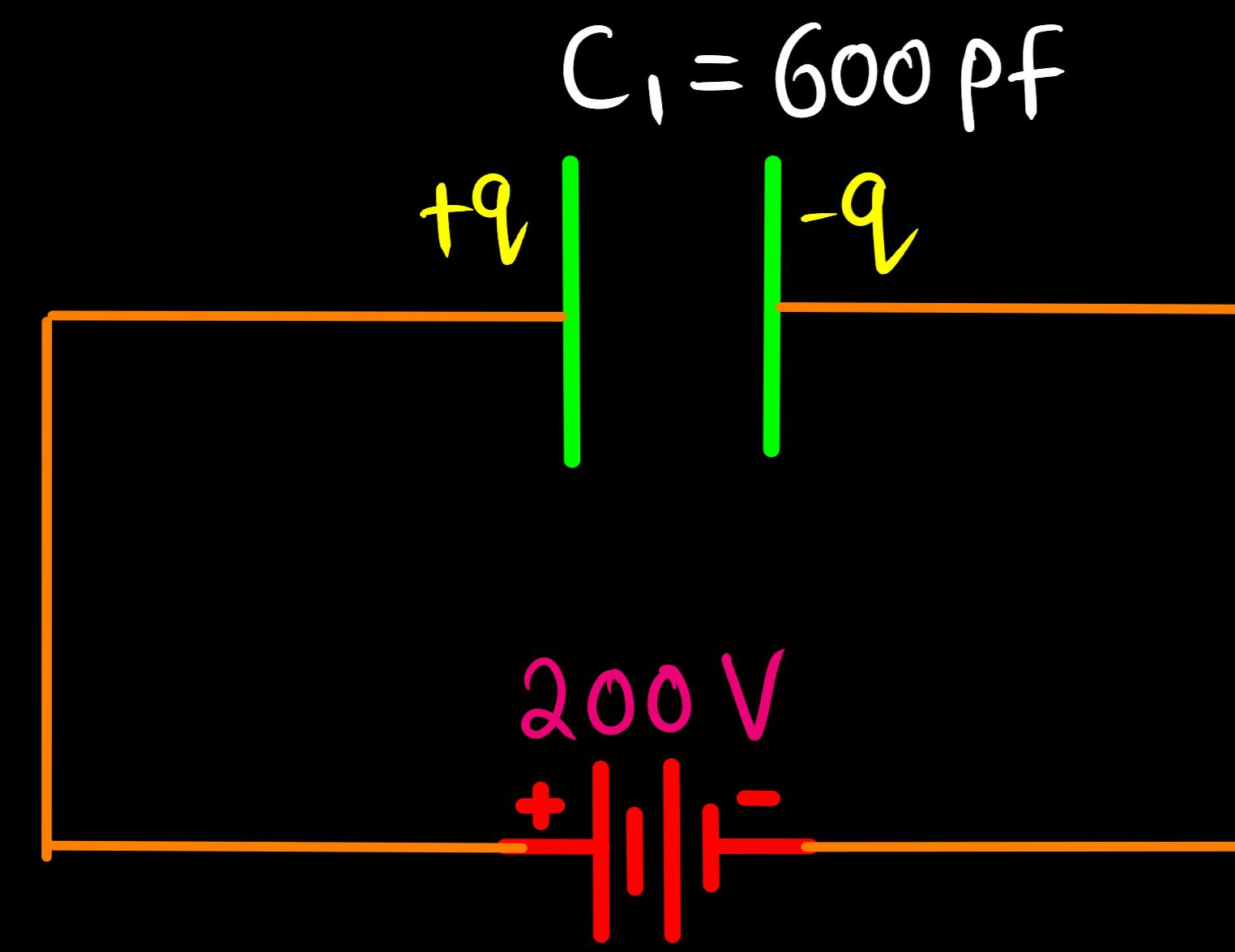2.11 A 600pF capacitor is charged by a 200V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. How much electrostatic energy is lost in the process?



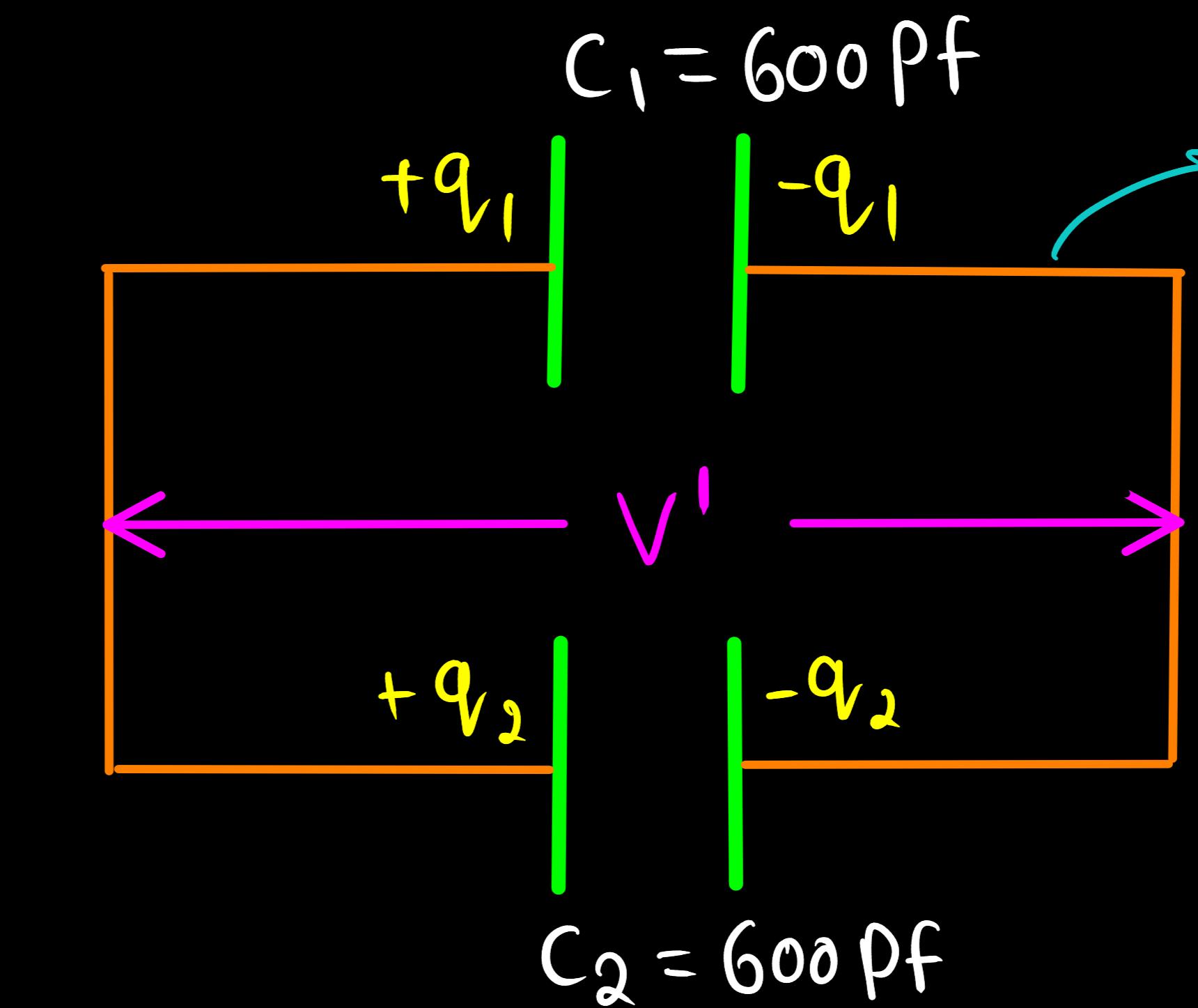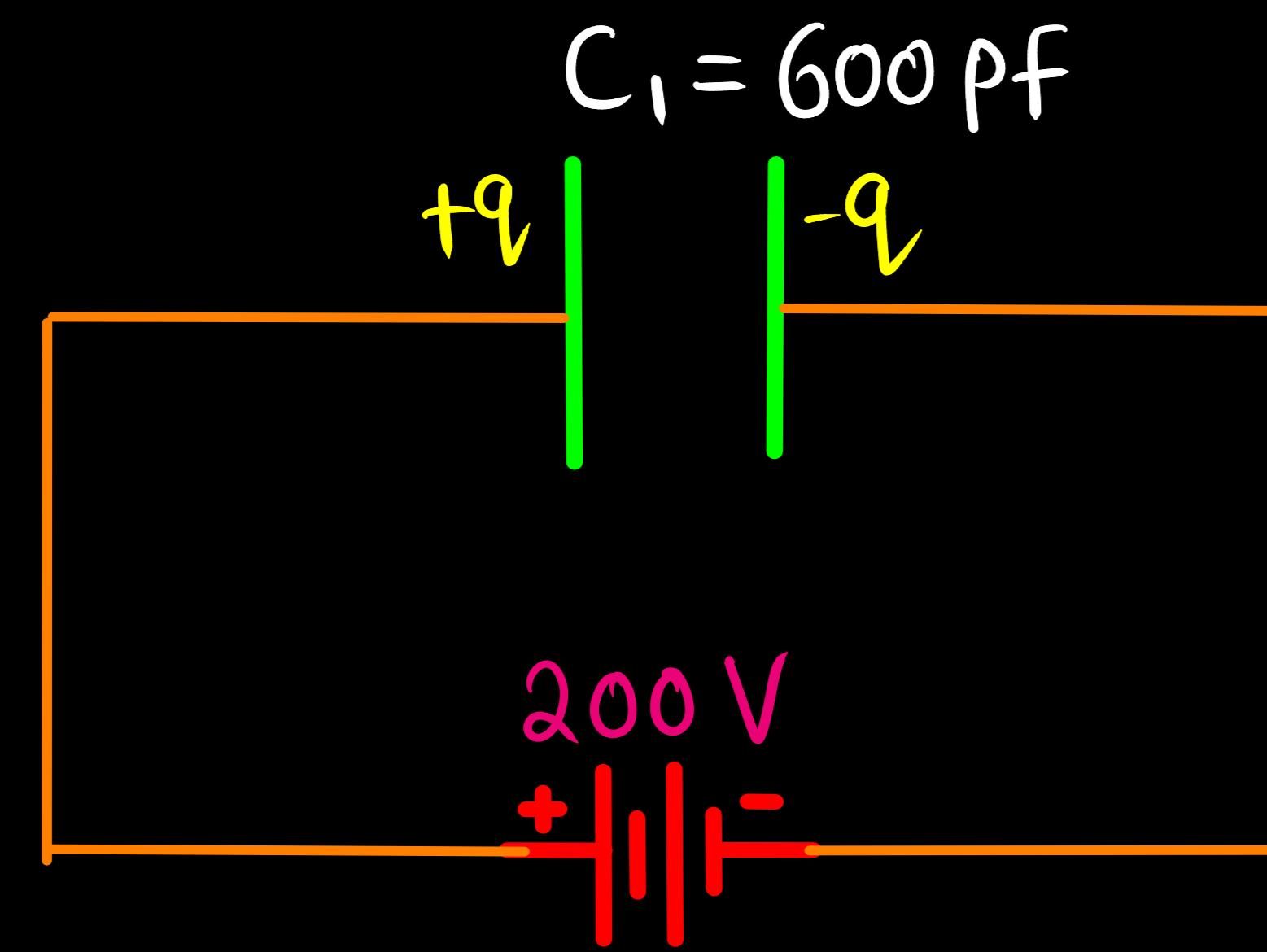2.11 A 600pF capacitor is charged by a 200V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. How much electrostatic energy is lost in the process?




Charge will flow
from C_1 to C_2
until both capacitor
have common potential.

$$q_1 + q_2 = q$$

↳ Conservation of
charge.

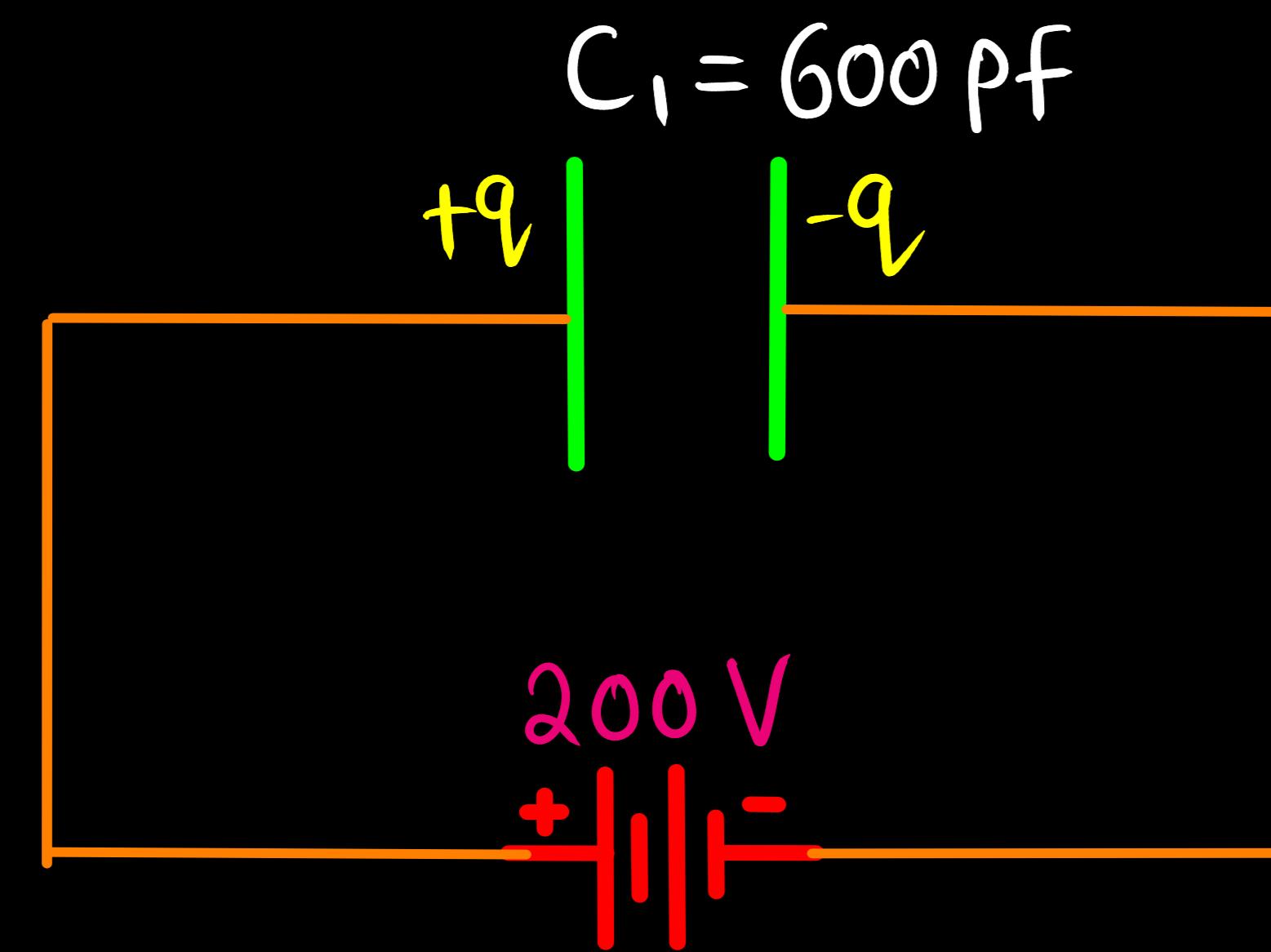
2.11 A 600pF capacitor is charged by a 200V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. How much electrostatic energy is lost in the process?



* Initial potential energy

$$U_i = \frac{1}{2} C_1 V^2$$
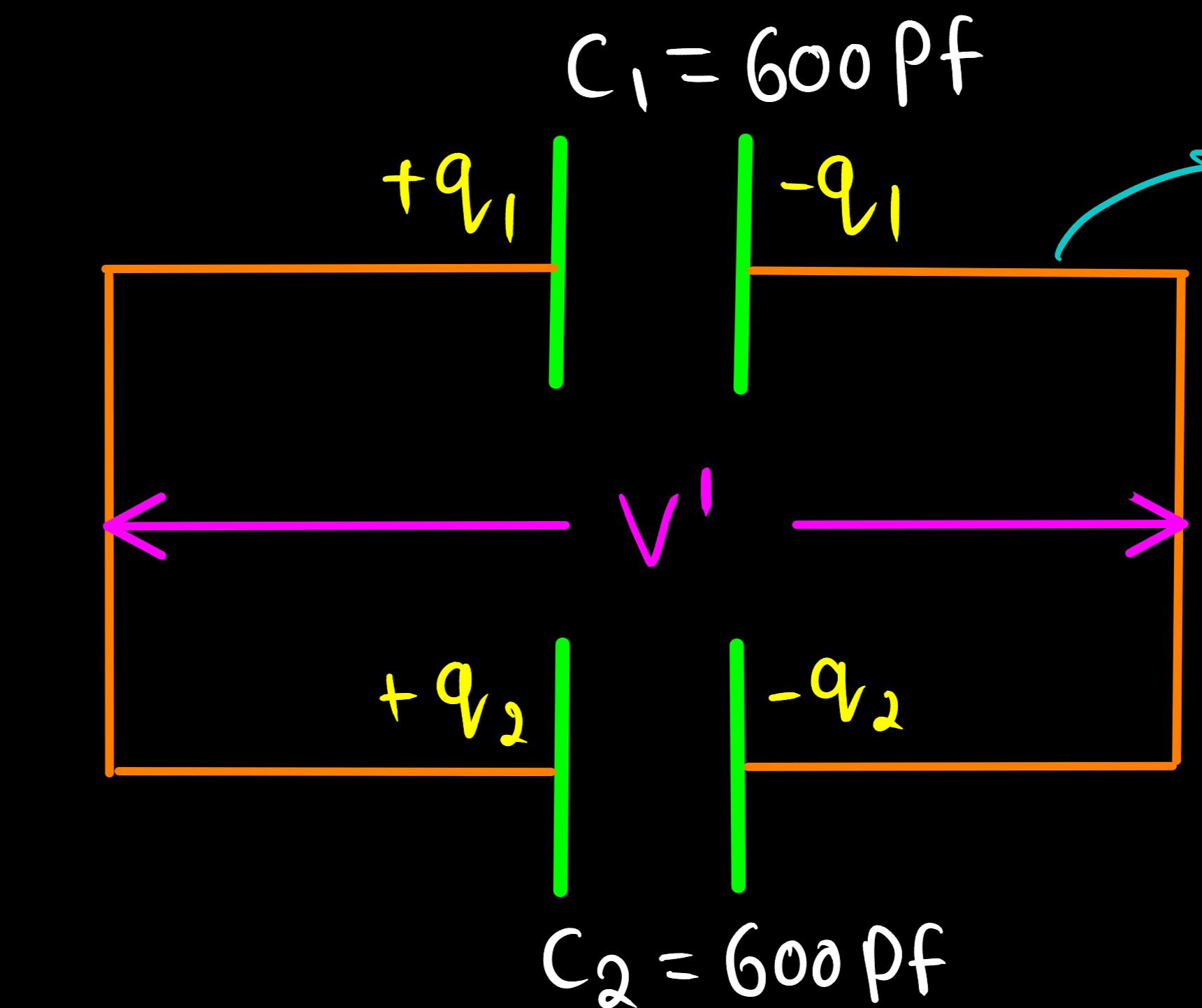
$$U_i = \frac{1}{2} \times 600 \times 10^{-12} \times 4 \times 10^4$$




Charge will flow from C₁ to C₂ until both capacitor have common potential.

$$q_1 + q_2 = q$$

↳ Conservation of Charge.

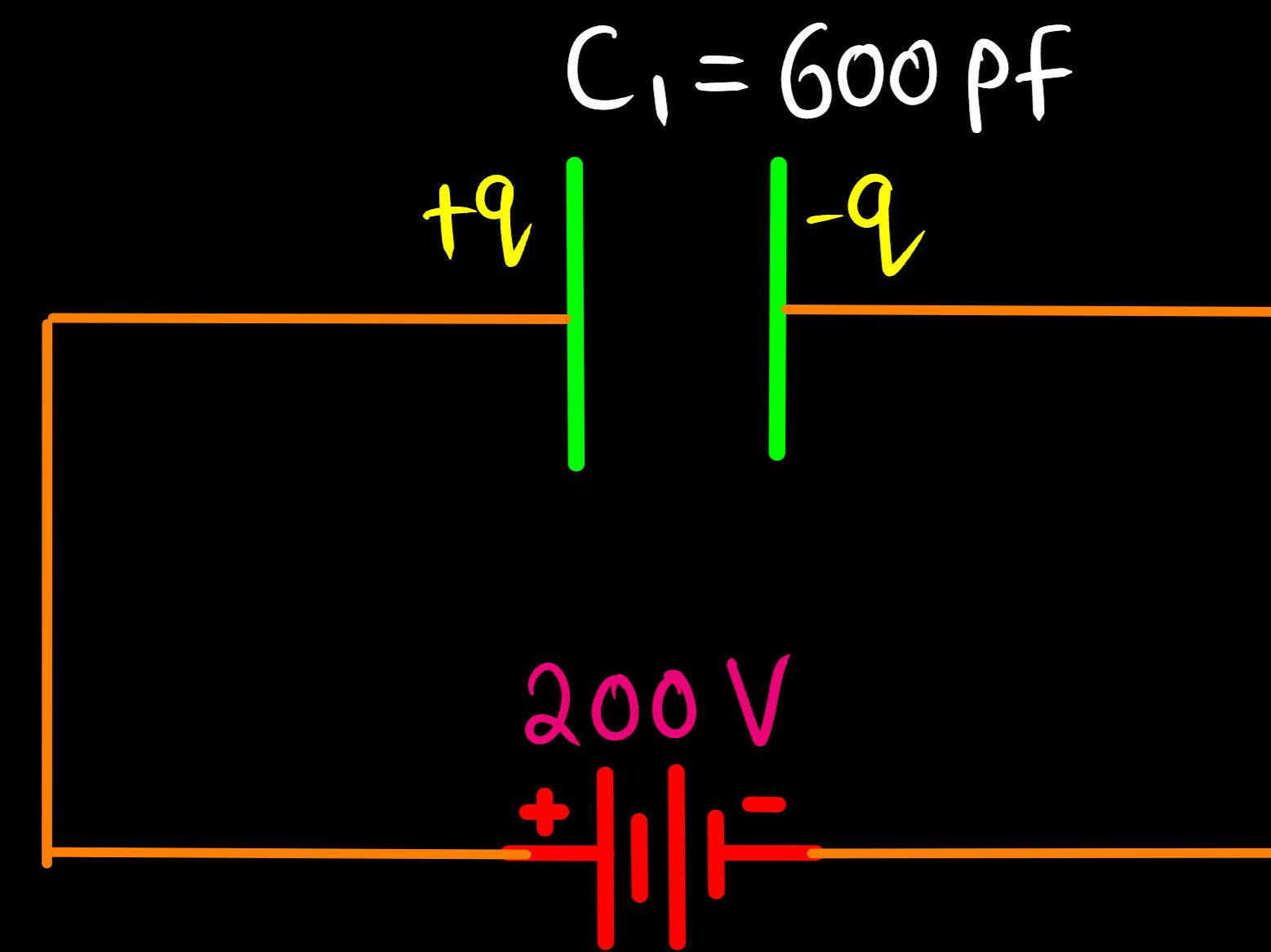2.11 A 600pF capacitor is charged by a 200V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. How much electrostatic energy is lost in the process?




* Initial potential energy

$$U_i = \frac{1}{2} C_1 V^2$$

$$U_i = \frac{1}{2} \times 600 \times 10^{-12} \times 200^2 \times 10^{-4}$$

$$U_i = 12 \times 10^{-6} \text{ J}$$

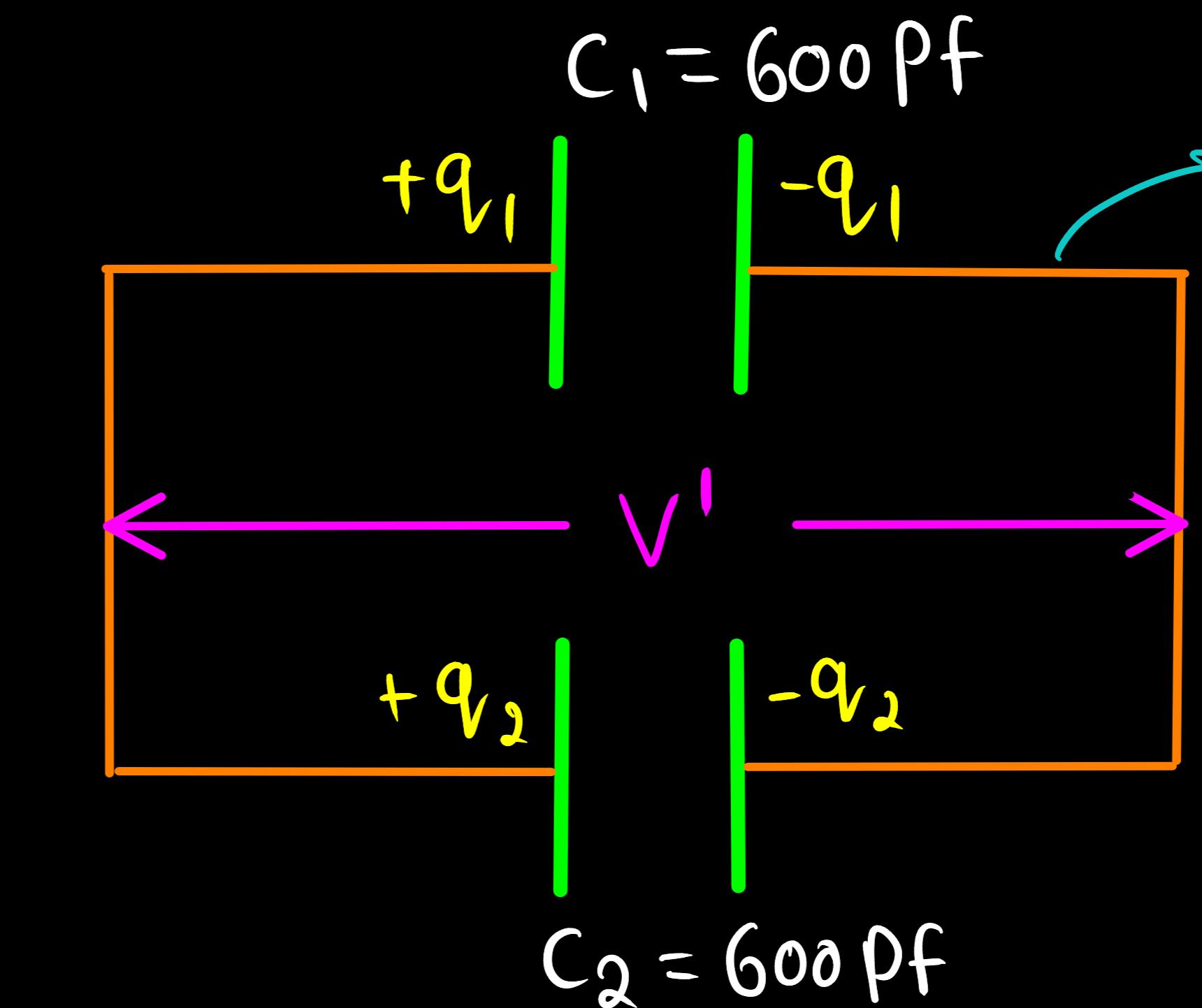


Charge will flow from C_1 to C_2 until both capacitor have common potential.

$$q_1 + q_2 = q$$

↳ Conservation of Charge.

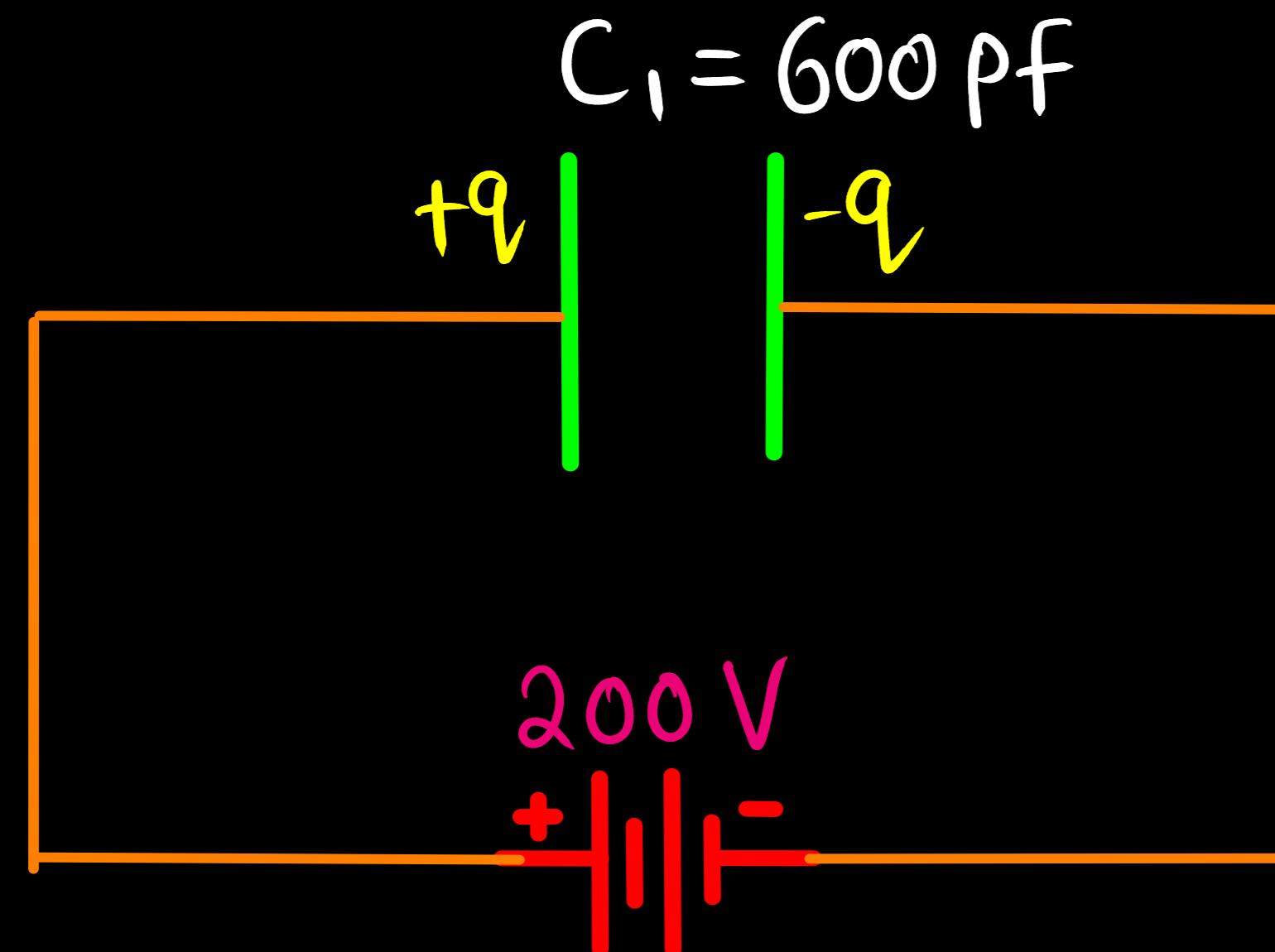2.11 A 600pF capacitor is charged by a 200V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. How much electrostatic energy is lost in the process?



* Initial potential energy


$$U_i = \frac{1}{2} C_1 V^2$$

$$U_i = \frac{1}{2} \times 600 \times 10^{-12} \times 200^2 \times 10^{-4}$$

$$U_i = 12 \times 10^{-6} \text{ J}$$

$$* q_1 + q_2 = q$$

$$\frac{C_1}{V'} + \frac{C_2}{V'} = q$$

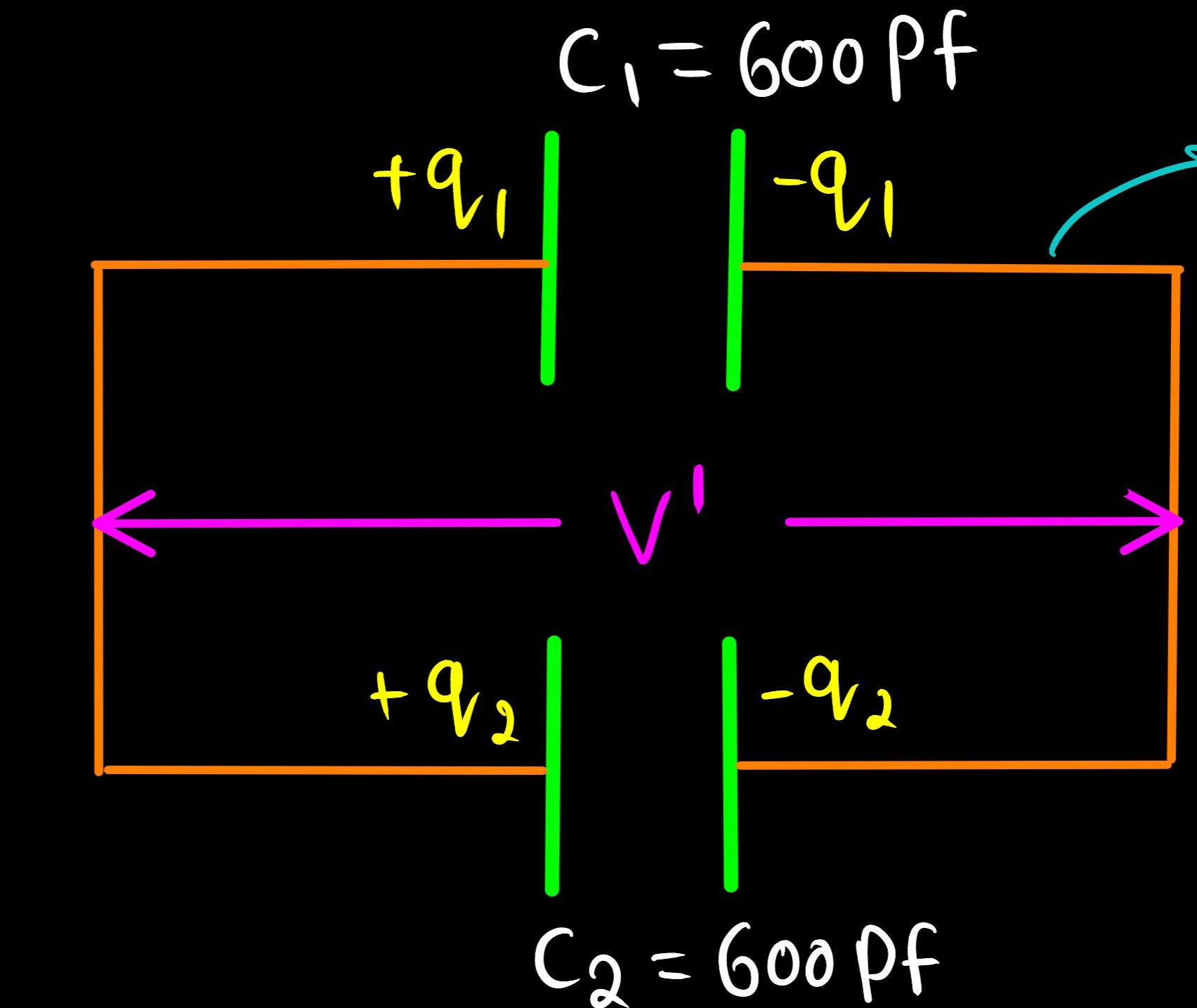


Charge will flow from C_1 to C_2 until both capacitor have common potential.

$$q_1 + q_2 = q$$

↳ Conservation of Charge.

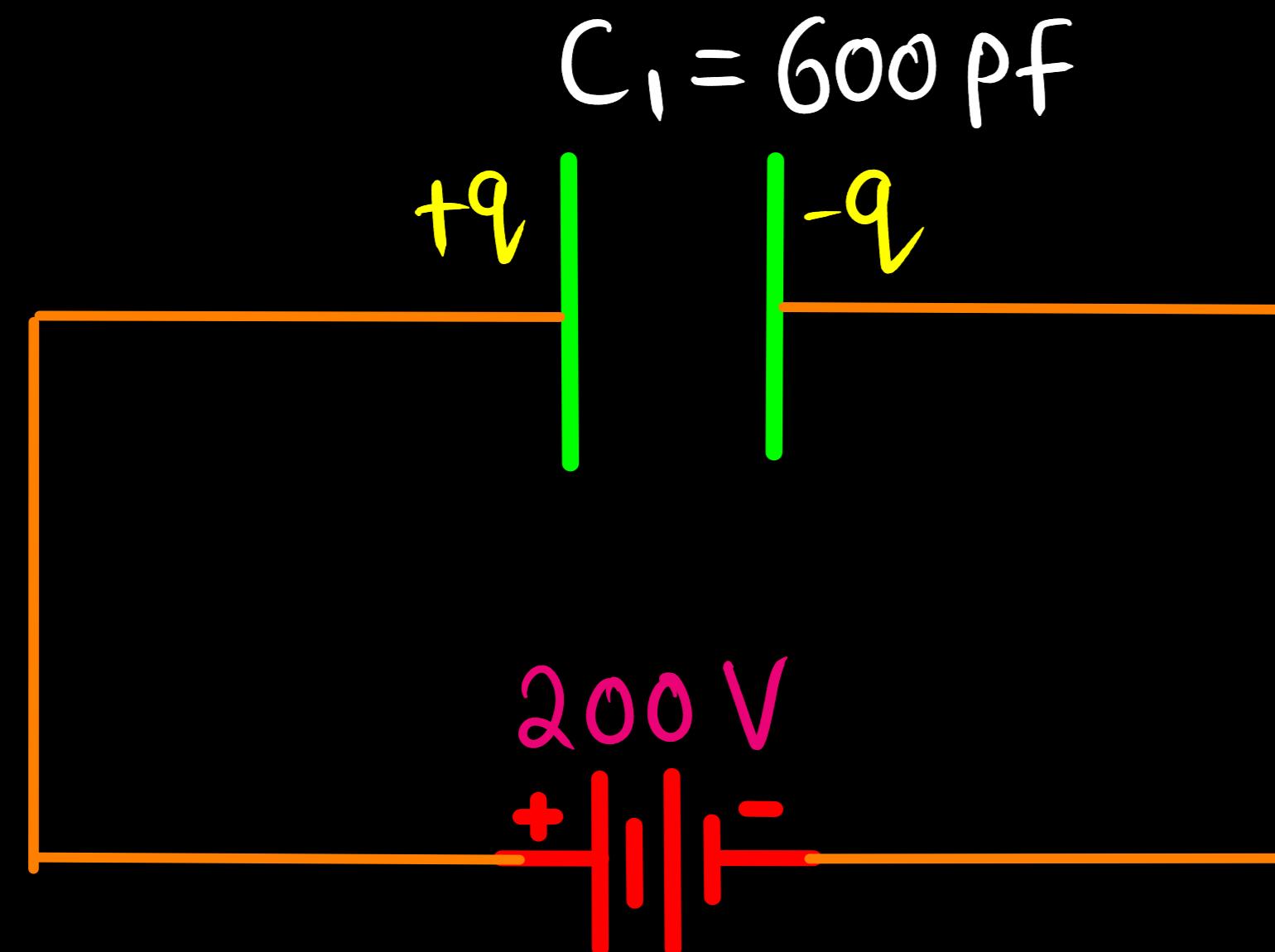2.11 A 600pF capacitor is charged by a 200V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. How much electrostatic energy is lost in the process?




* Initial potential energy

$$U_i = \frac{1}{2} C_1 V^2$$

$$U_i = \frac{1}{2} \times 600 \times 10^{-12} \times 200^2 \times 10^{-4}$$

$$U_i = 12 \times 10^{-6} \text{ J}$$

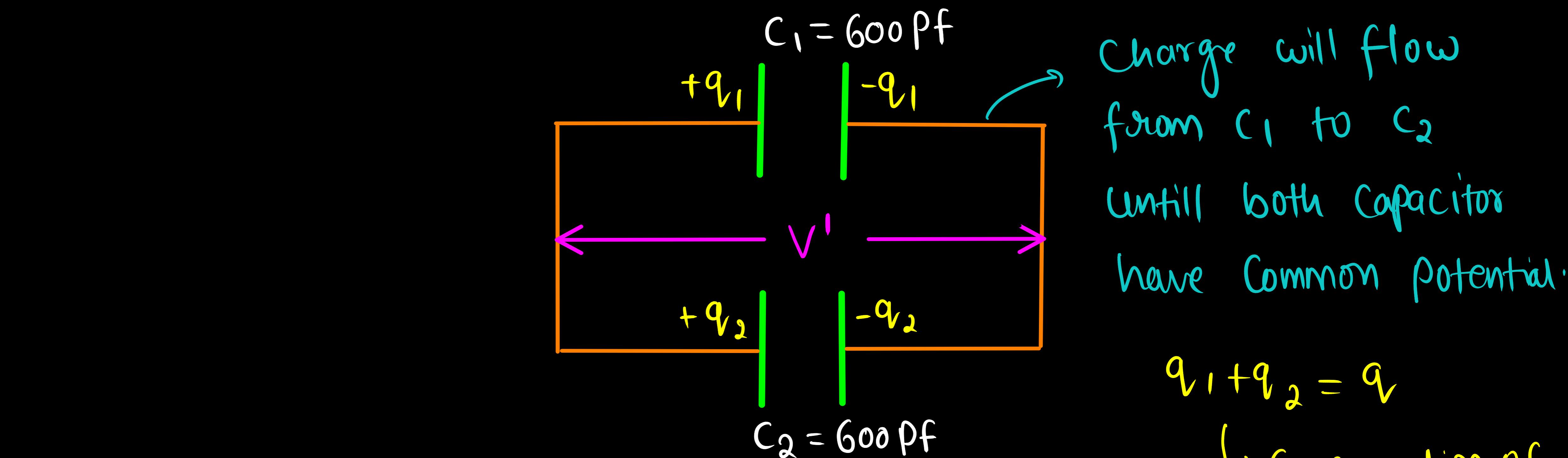

$$* q_1 + q_2 = q$$

$$\frac{C}{V'} + \frac{C}{V'} = q$$

$$\frac{2C}{V'} = q$$


$$V' = \frac{q}{2C}$$

Charge will flow from C_1 to C_2 until both capacitor have common potential.

$$q_1 + q_2 = q$$

↳ Conservation of Charge.

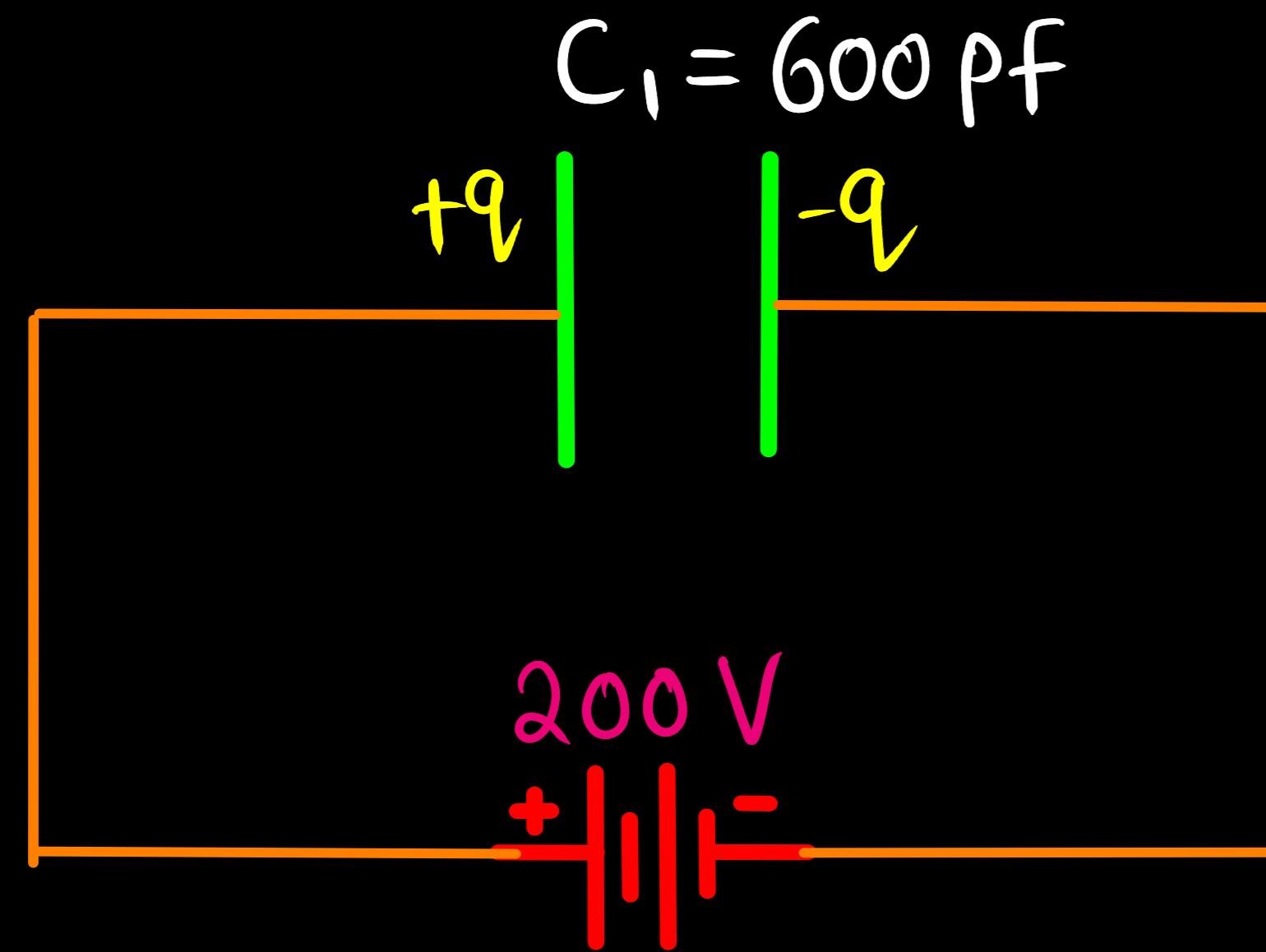2.11 A 600pF capacitor is charged by a 200V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. How much electrostatic energy is lost in the process?




* Initial potential energy

$$U_i = \frac{1}{2} C_1 V^2$$

$$U_i = \frac{1}{2} \times 600 \times 10^{-12} \times 200^2 \times 10^{-4}$$

$$U_i = 12 \times 10^{-6} \text{ J}$$

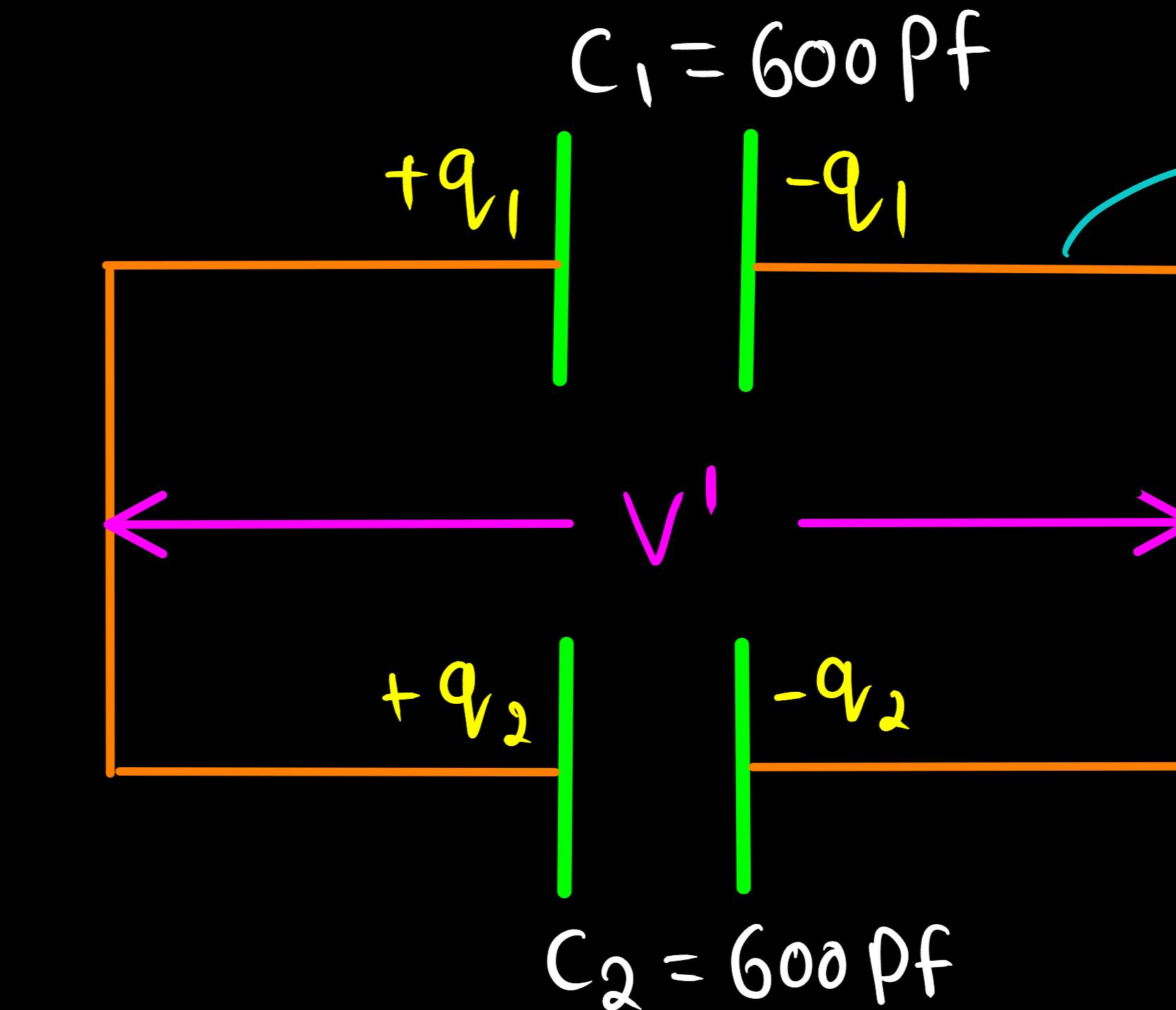

$$* q_1 + q_2 = q$$

$$\frac{C}{V'} + \frac{C}{V'} = q$$

$$\frac{2C}{V'} = q$$


$$V' = \frac{q}{2C} = \frac{V}{2}$$

Charge will flow from C_1 to C_2 until both capacitor have common potential.

$$q_1 + q_2 = q$$

↳ Conservation of Charge.

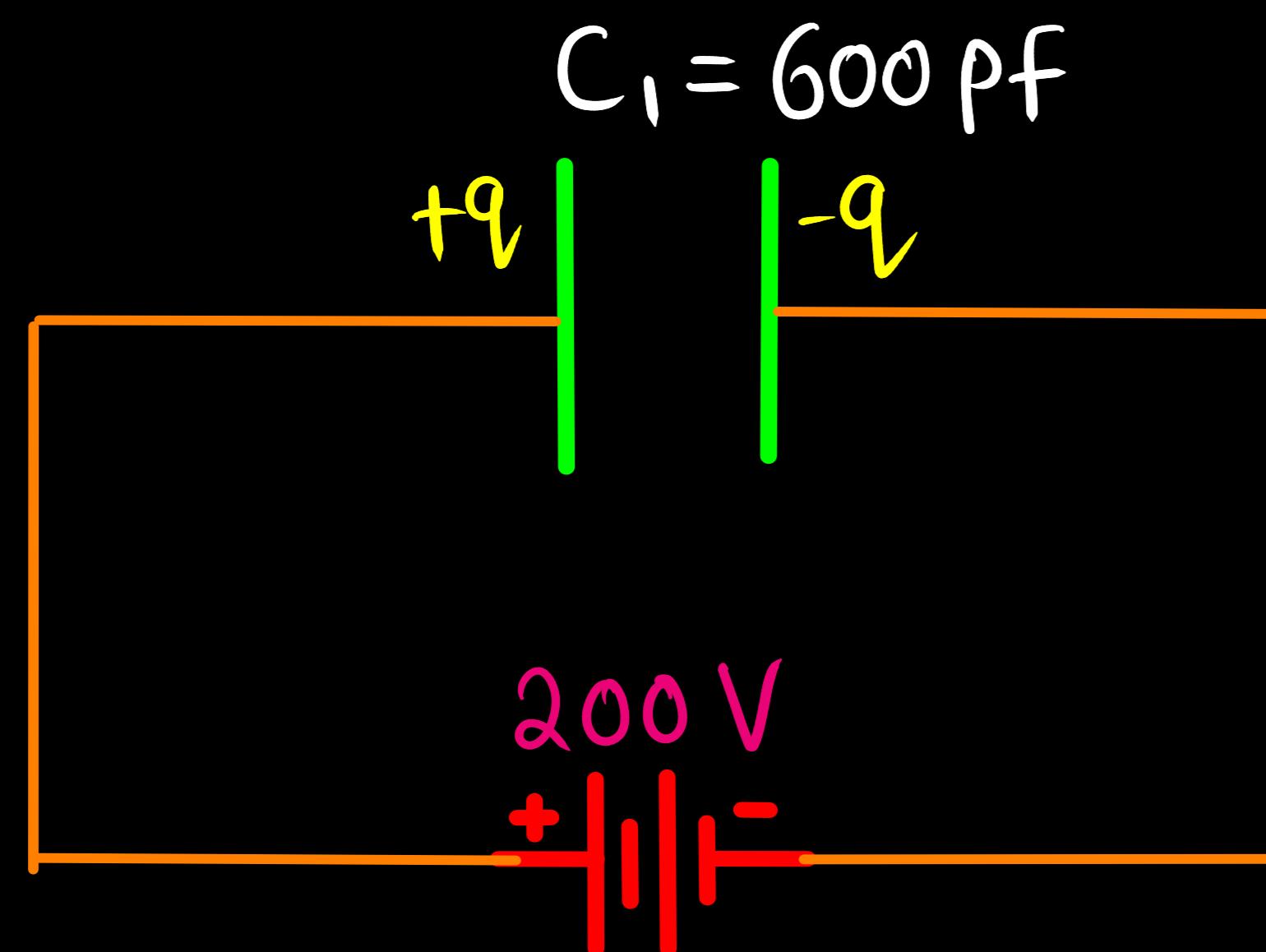2.11 A 600pF capacitor is charged by a 200V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. How much electrostatic energy is lost in the process?




* Initial potential energy

$$U_i = \frac{1}{2} C_1 V^2$$

$$U_i = \frac{1}{2} \times 600 \times 10^{-12} \times 200^2 \times 10^{-4}$$

$$U_i = 12 \times 10^{-6} \text{ J}$$

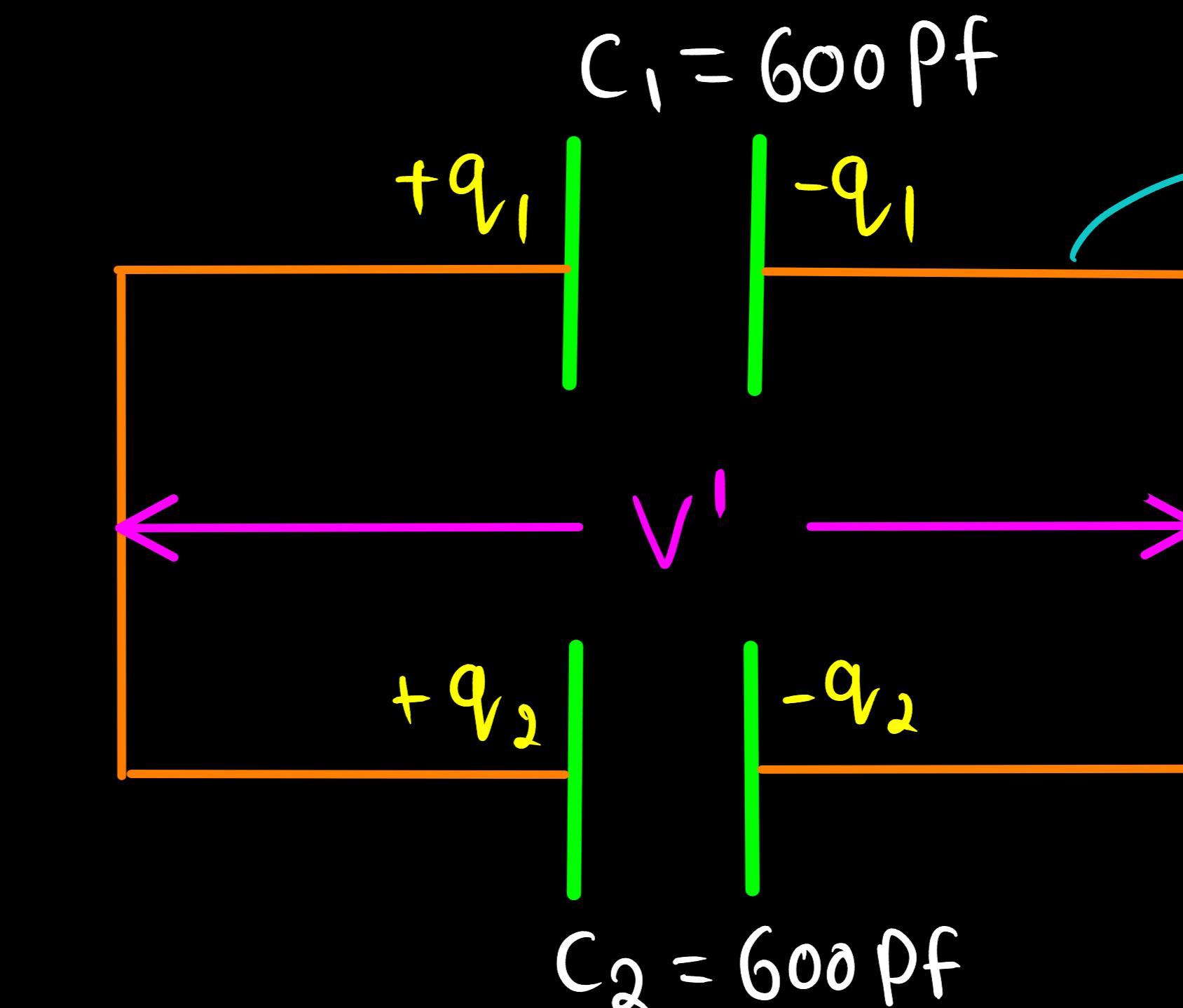

Charge will flow from C_1 to C_2 until both capacitor have common potential.

$$q_1 + q_2 = q$$

↳ Conservation of Charge.


$$* \quad q_1 + q_2 = q$$

$$\frac{C}{V'} + \frac{C}{V'} = q$$

$$\frac{2C}{V'} = q$$

$$V' = \frac{q}{2C} = \frac{V}{2} = \frac{200}{2} = 100 \text{ V}$$

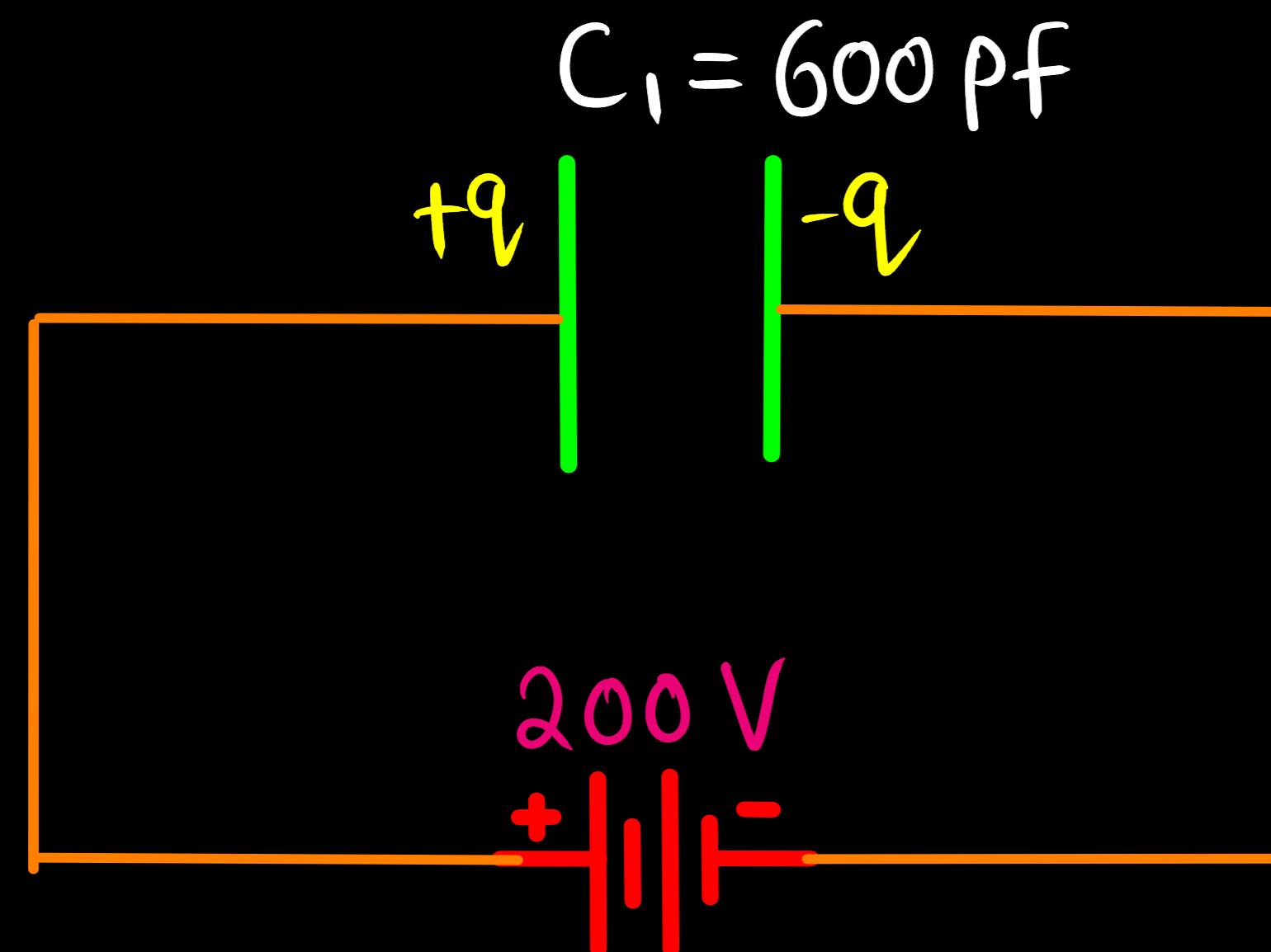2.11 A 600pF capacitor is charged by a 200V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. How much electrostatic energy is lost in the process?




* Initial potential energy

$$U_i = \frac{1}{2} C_1 V^2$$

$$U_i = \frac{1}{2} \times 600 \times 10^{-12} \times 200^2 \times 10^{-4}$$

$$U_i = 12 \times 10^{-6} \text{ J}$$

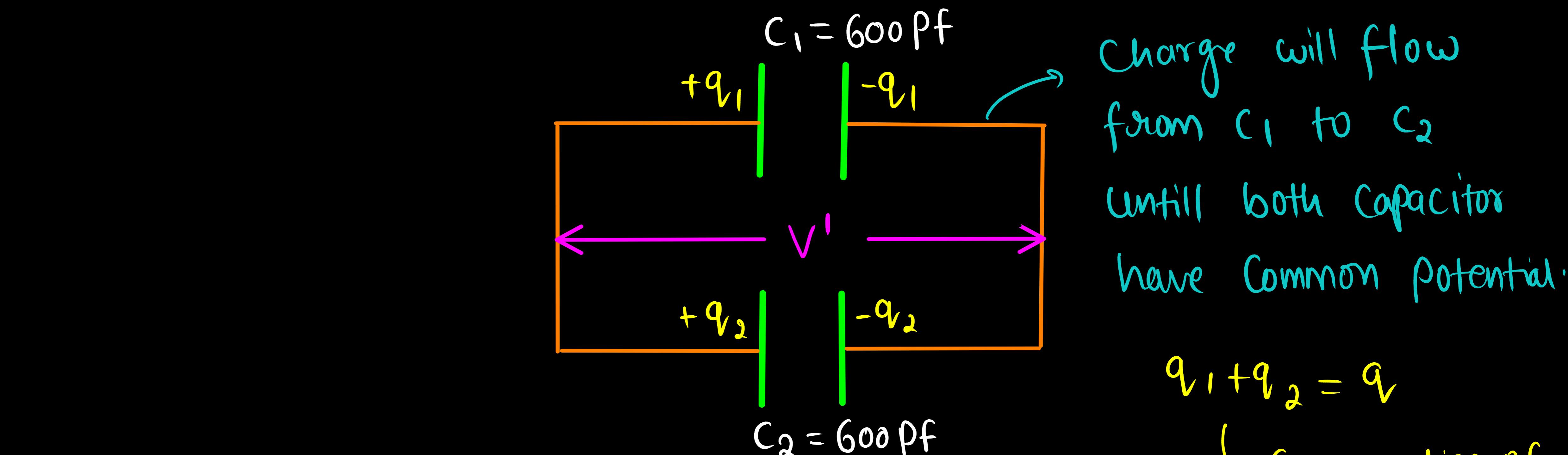

$$* q_{11} + q_{22} = q$$

$$\frac{C_1}{V'} + \frac{C_2}{V'} = q$$


$$\frac{2C}{V'} = q$$

$$V' = \frac{q}{2C} = \frac{V}{2} = \frac{200}{2} = 100 \text{ V}$$

$$C' = C_1 + C_2 = 1200 \text{ pF}$$

↳ Conservation of Charge.

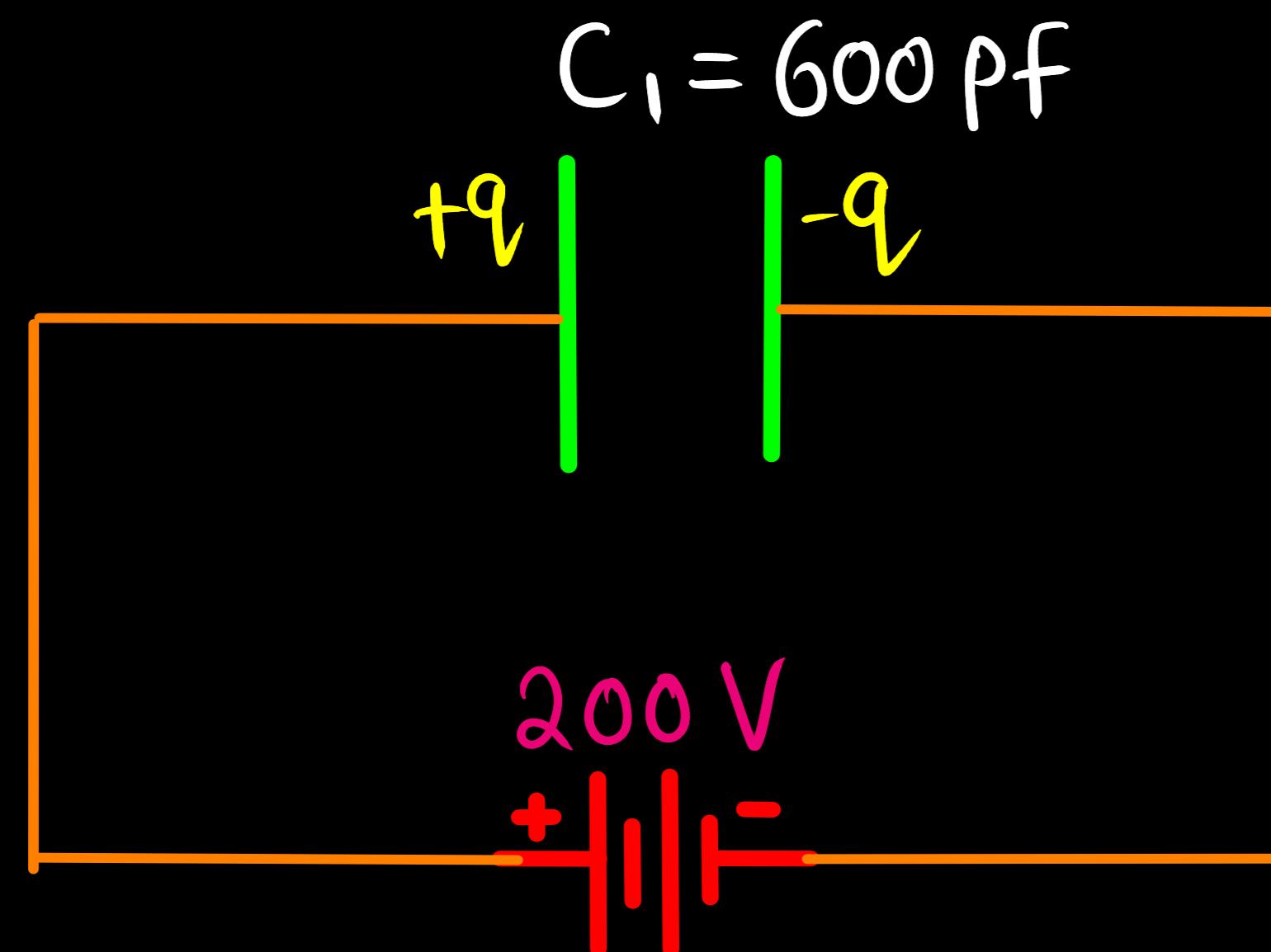2.11 A 600pF capacitor is charged by a 200V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. How much electrostatic energy is lost in the process?



* Initial potential energy

$$U_i = \frac{1}{2} C_1 V^2$$

$$U_i = \frac{1}{2} \times 600 \times 10^{-12} \times 200^2 \times 10^{-4}$$


$$U_i = 12 \times 10^{-6} \text{ J}$$

$$* q_1 + q_2 = q$$

$$\frac{C}{V'} + \frac{C}{V'} = q$$

$$\frac{2C}{V'} = q$$
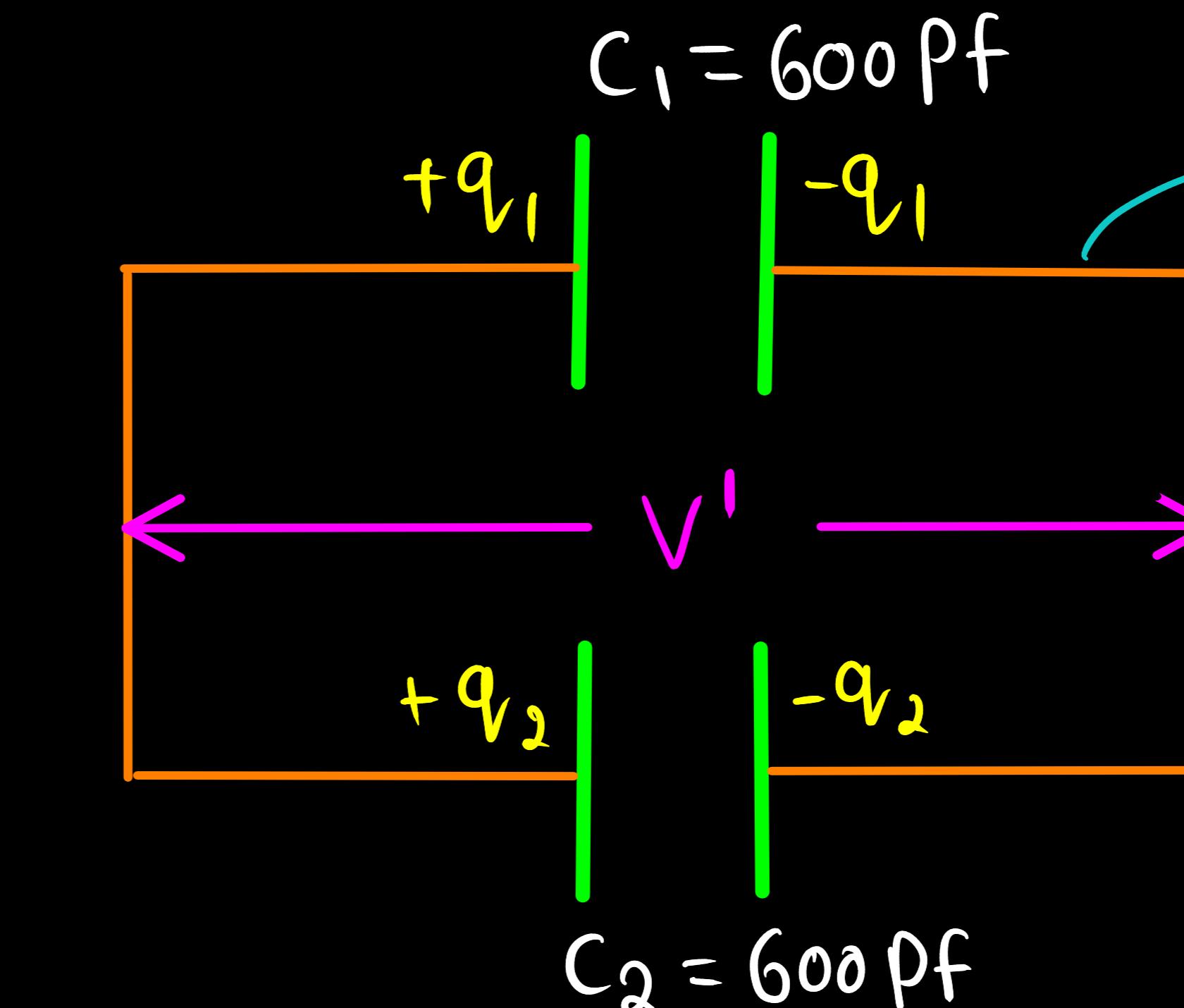
$$V' = \frac{q}{2C} = \frac{V}{2} = \frac{200}{2} = 100 \text{ V}$$



Charge will flow from C_1 to C_2 until both capacitor have common potential.

$$q_1 + q_2 = q$$


↳ Conservation of Charge.

$$C' = C_1 + C_2 = 1200 \text{ pF}$$

final Potential Energy -

$$U_f = \frac{1}{2} C' V'^2$$

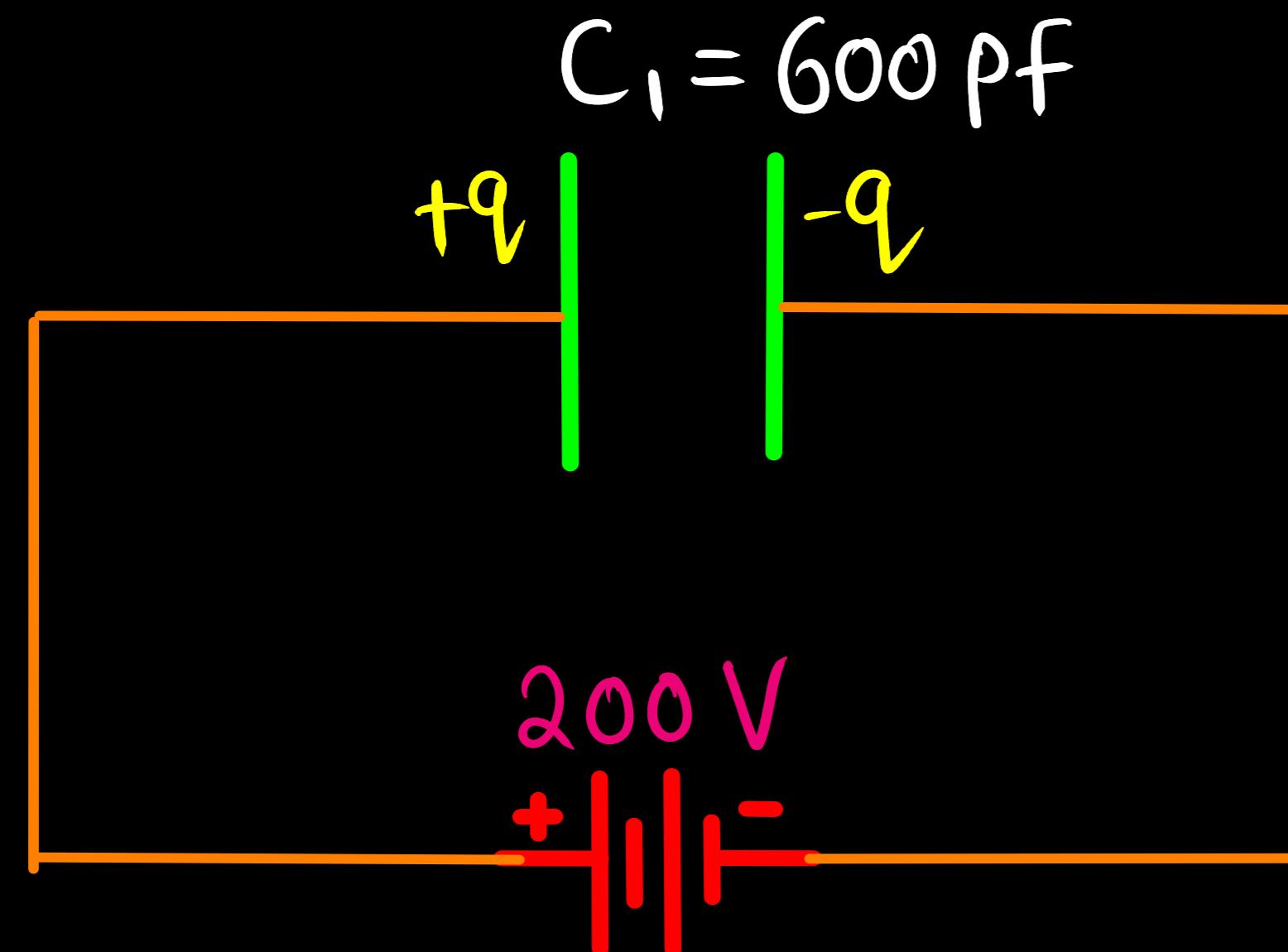2.11 A 600pF capacitor is charged by a 200V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. How much electrostatic energy is lost in the process?




* Initial potential energy

$$U_i = \frac{1}{2} C_1 V^2$$

$$U_i = \frac{1}{2} \times 600 \times 10^{-12} \times 200^2 \times 10^{-4}$$

$$U_i = 12 \times 10^{-6} \text{ J}$$

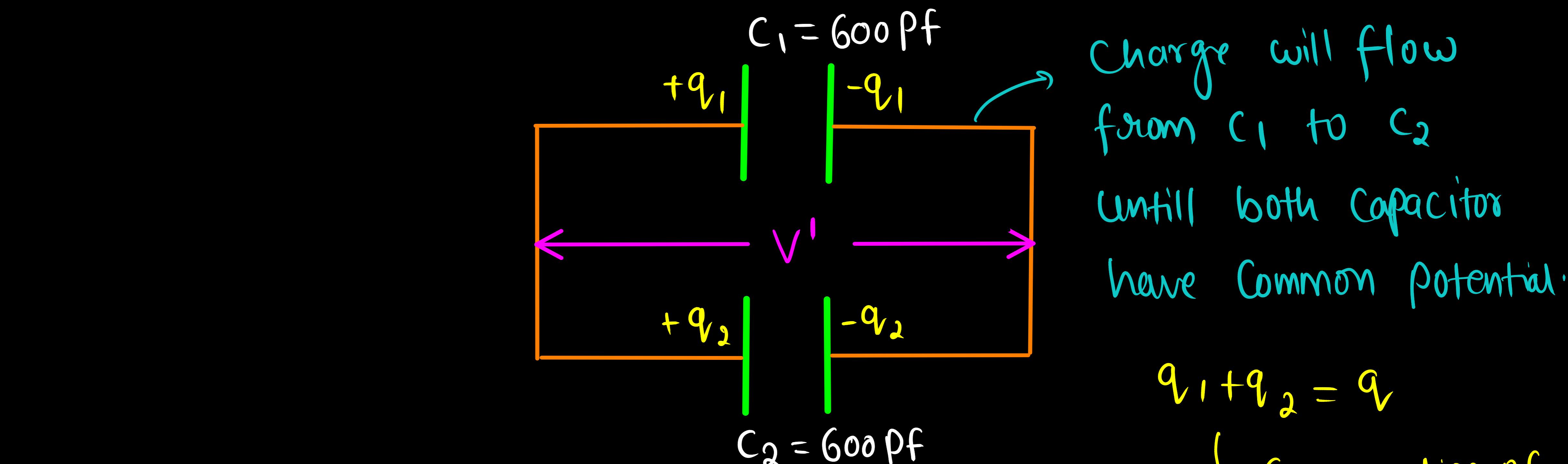

$$* q_1 + q_2 = q$$

$$\frac{C}{V'} + \frac{C}{V'} = q$$

$$\frac{2C}{V'} = q$$

$$V' = \frac{q}{2C} = \frac{V}{2} = \frac{200}{2} = 100 \text{ V}$$


$$C' = C_1 + C_2 = 1200 \text{ pF}$$

final Potential Energy -

$$U_f = \frac{1}{2} C' V'^2$$

$$U_f = \frac{1}{2} \times 1200 \times 10^{-12} \times 100 \times 100$$

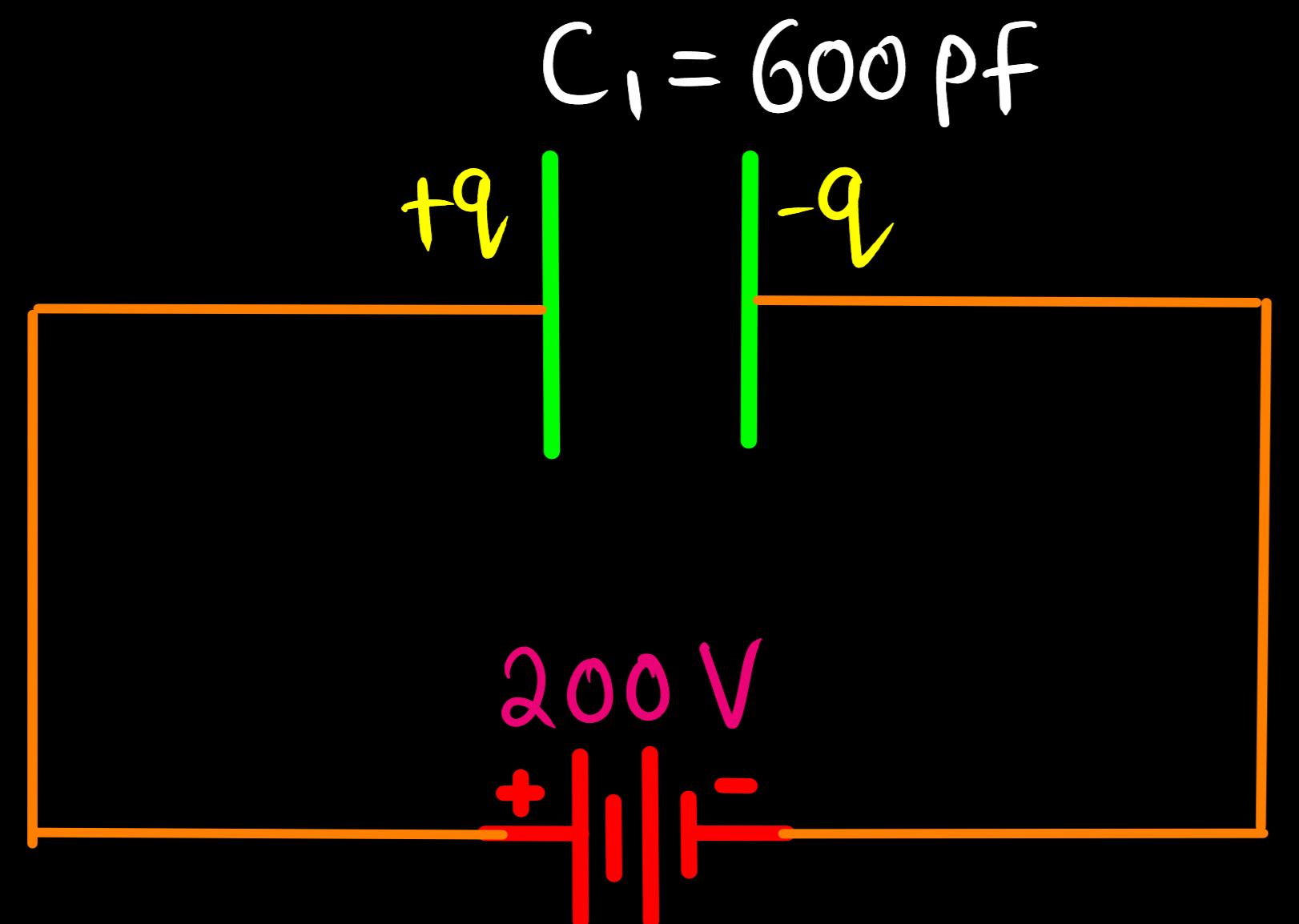2.11 A 600pF capacitor is charged by a 200V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. How much electrostatic energy is lost in the process?



* Initial potential energy

$$U_i = \frac{1}{2} C_1 V^2$$

$$U_i = \frac{1}{2} \times 600 \times 10^{-12} \times 200^2 \times 10^{-4}$$


$$U_i = 12 \times 10^{-6} \text{ J}$$

$$* q_1 + q_2 = q$$

$$\frac{C_1}{V'} + \frac{C_2}{V'} = q$$

$$\frac{2C}{V'} = q$$
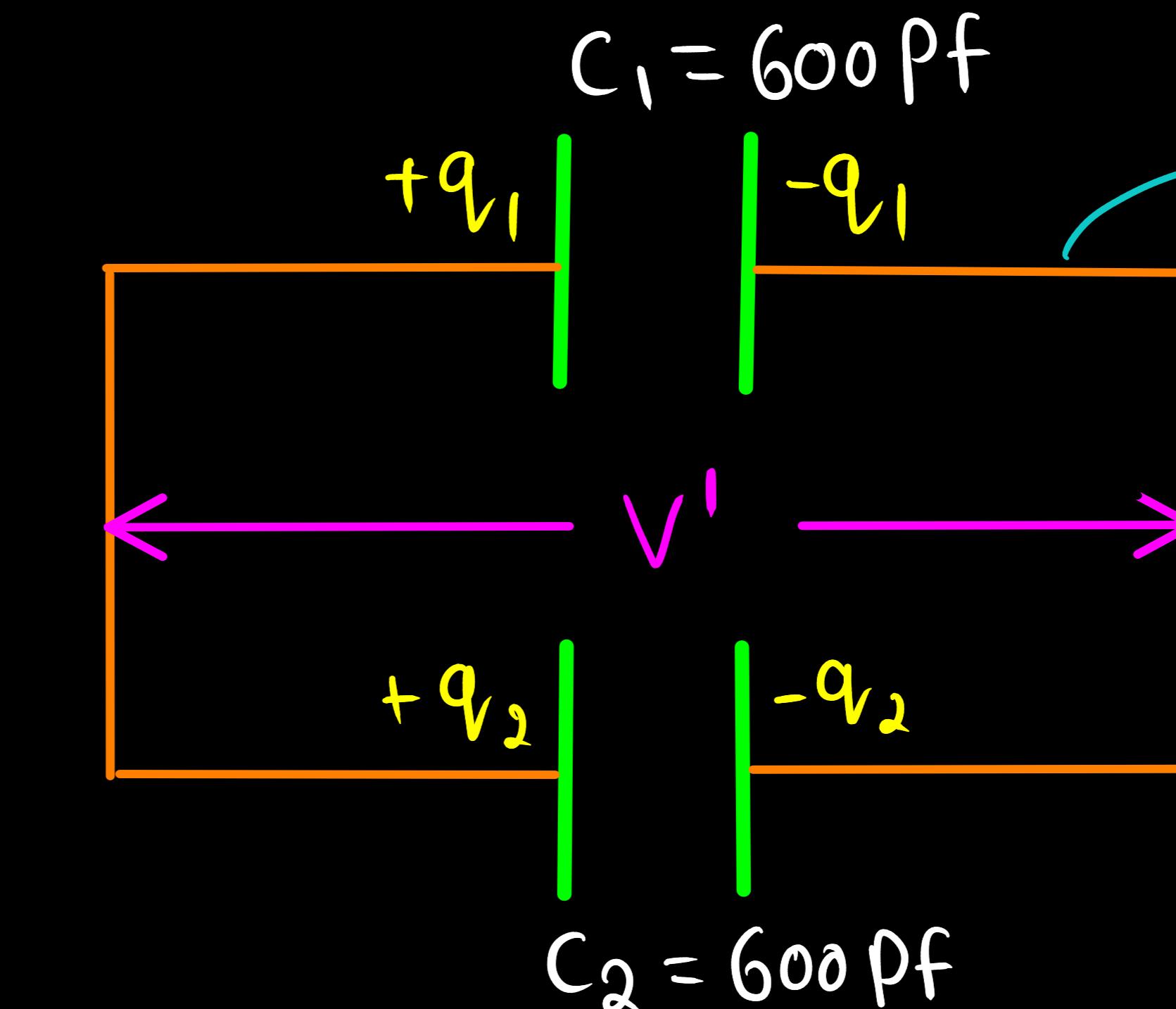
$$V' = \frac{q}{2C} = \frac{V}{2} = \frac{200}{2} = 100 \text{ V}$$



Charge will flow from C_1 to C_2 until both capacitor have common potential.

$$q_1 + q_2 = q$$

↳ Conservation of Charge.

$$C' = C_1 + C_2 = 1200 \text{ pF}$$


final Potential Energy -

$$U_f = \frac{1}{2} C' V'^2$$

$$U_f = \frac{1}{2} \times 1200 \times 10^{-12} \times 100 \times 100$$

$$U_f = 6 \times 10^{-6} \text{ J}$$

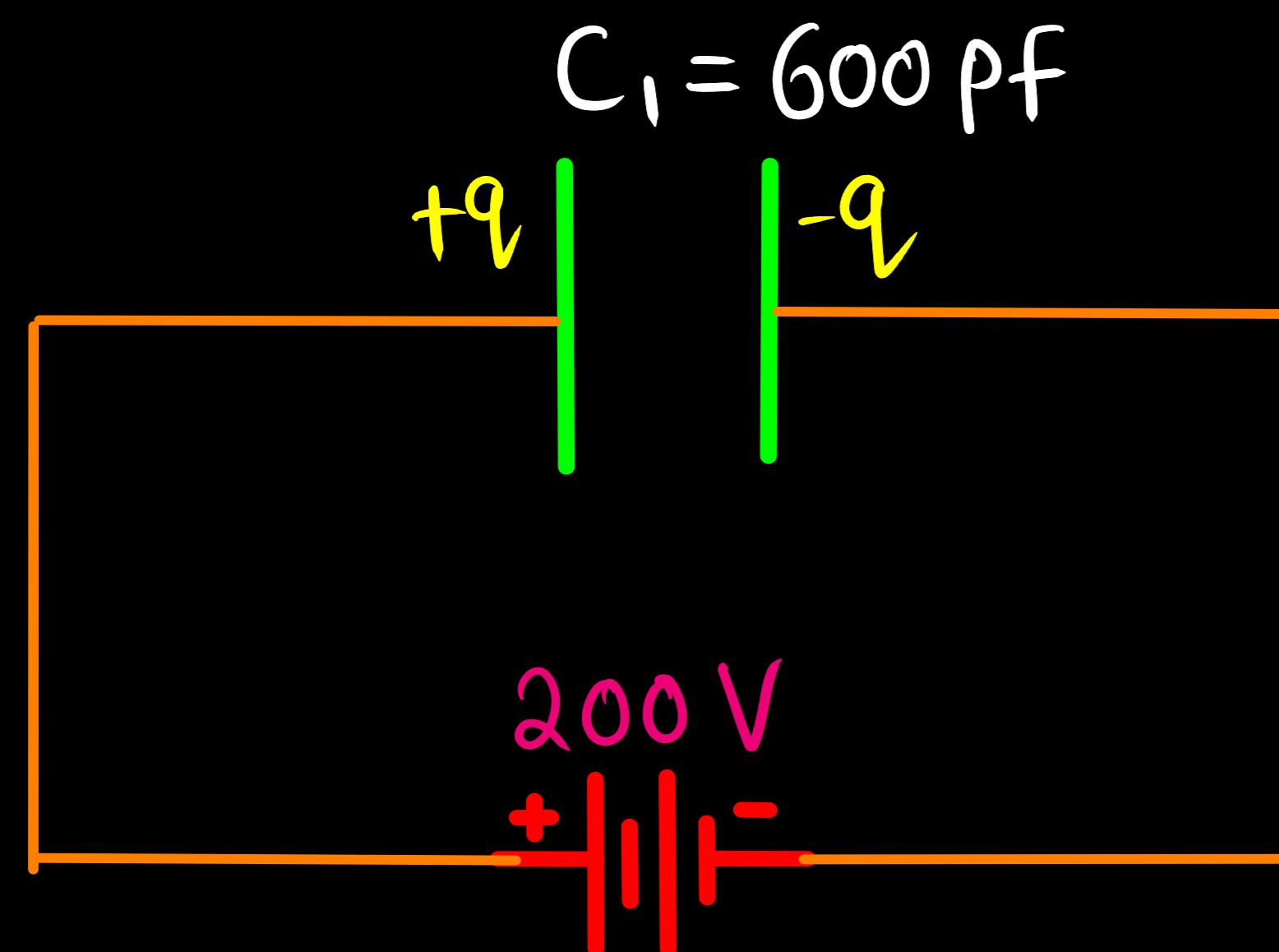2.11 A 600pF capacitor is charged by a 200V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. How much electrostatic energy is lost in the process?




* Initial potential energy

$$U_i = \frac{1}{2} C_1 V^2$$

$$U_i = \frac{1}{2} \times 600 \times 10^{-12} \times 200^2 \times 10^{-4}$$

$$U_i = 12 \times 10^{-6} \text{ J}$$

$$\text{Energy lost} = U_i - U_f$$

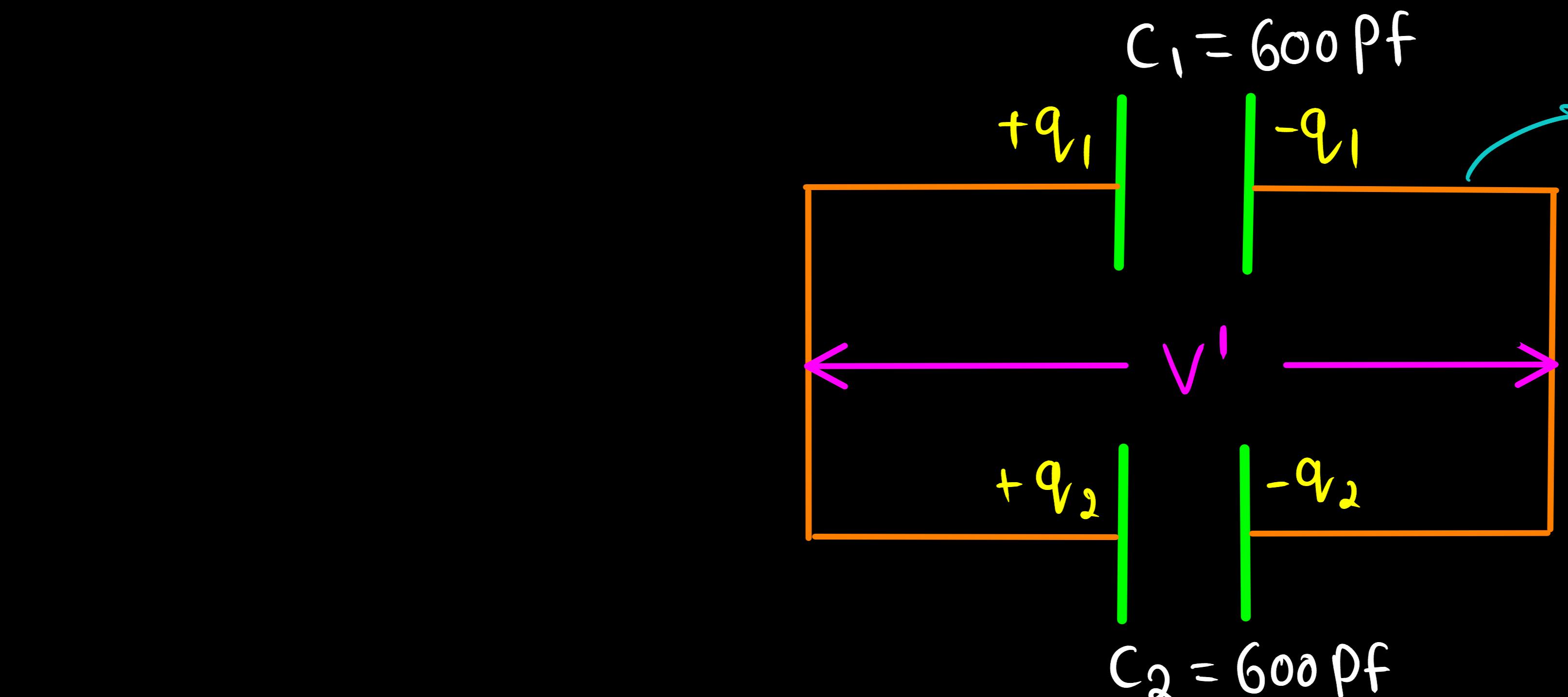

$$* q_1 + q_2 = q$$

$$\frac{C}{V'} + \frac{C}{V'} = q$$

$$\frac{2C}{V'} = q$$

$$V' = \frac{q}{2C} = \frac{V}{2} = \frac{200}{2} = 100 \text{ V}$$

Charge will flow from C_1 to C_2 until both capacitor have common potential.

$$q_1 + q_2 = q$$

↳ Conservation of Charge.

$$C' = C_1 + C_2 = 1200 \text{ pF}$$


final Potential Energy -

$$U_f = \frac{1}{2} C' V'^2$$

$$U_f = \frac{1}{2} \times 1200 \times 10^{-12} \times 100 \times 100$$

$$U_f = 6 \times 10^{-6} \text{ J}$$

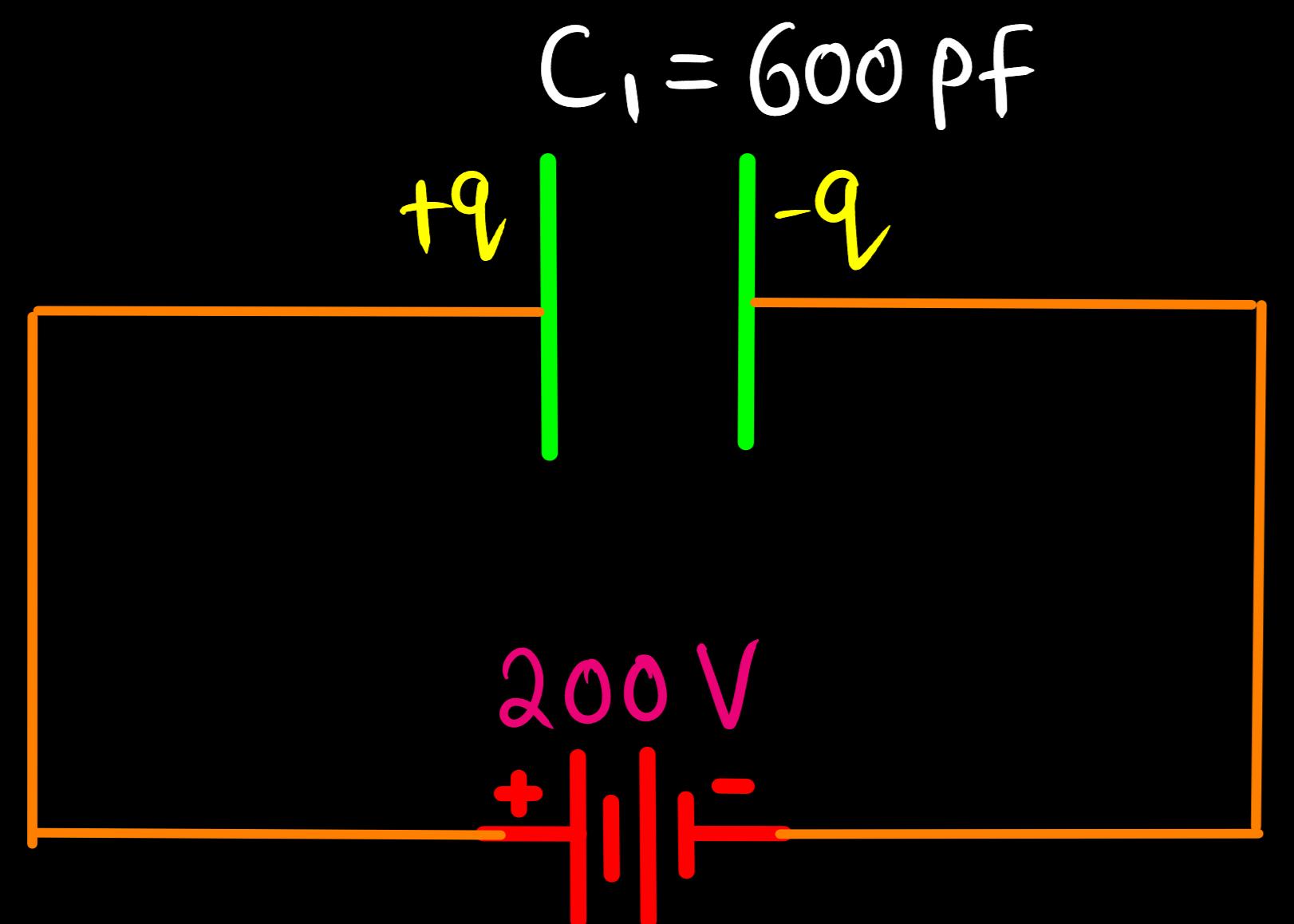2.11 A 600pF capacitor is charged by a 200V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. How much electrostatic energy is lost in the process?



* Initial potential energy

$$U_i = \frac{1}{2} C_1 V^2$$

$$U_i = \frac{1}{2} \times 600 \times 10^{-12} \times 200^2 \times 10^{-4}$$

$$U_i = 12 \times 10^{-6} \text{ J}$$


$$\text{Energy lost} = U_i - U_f = 12 \times 10^{-6} \text{ J} - 6 \times 10^{-6} \text{ J}$$

$$* q_1 + q_2 = q$$

$$\frac{C}{V'} + \frac{C}{V'} = q$$

$$\frac{2C}{V'} = q$$
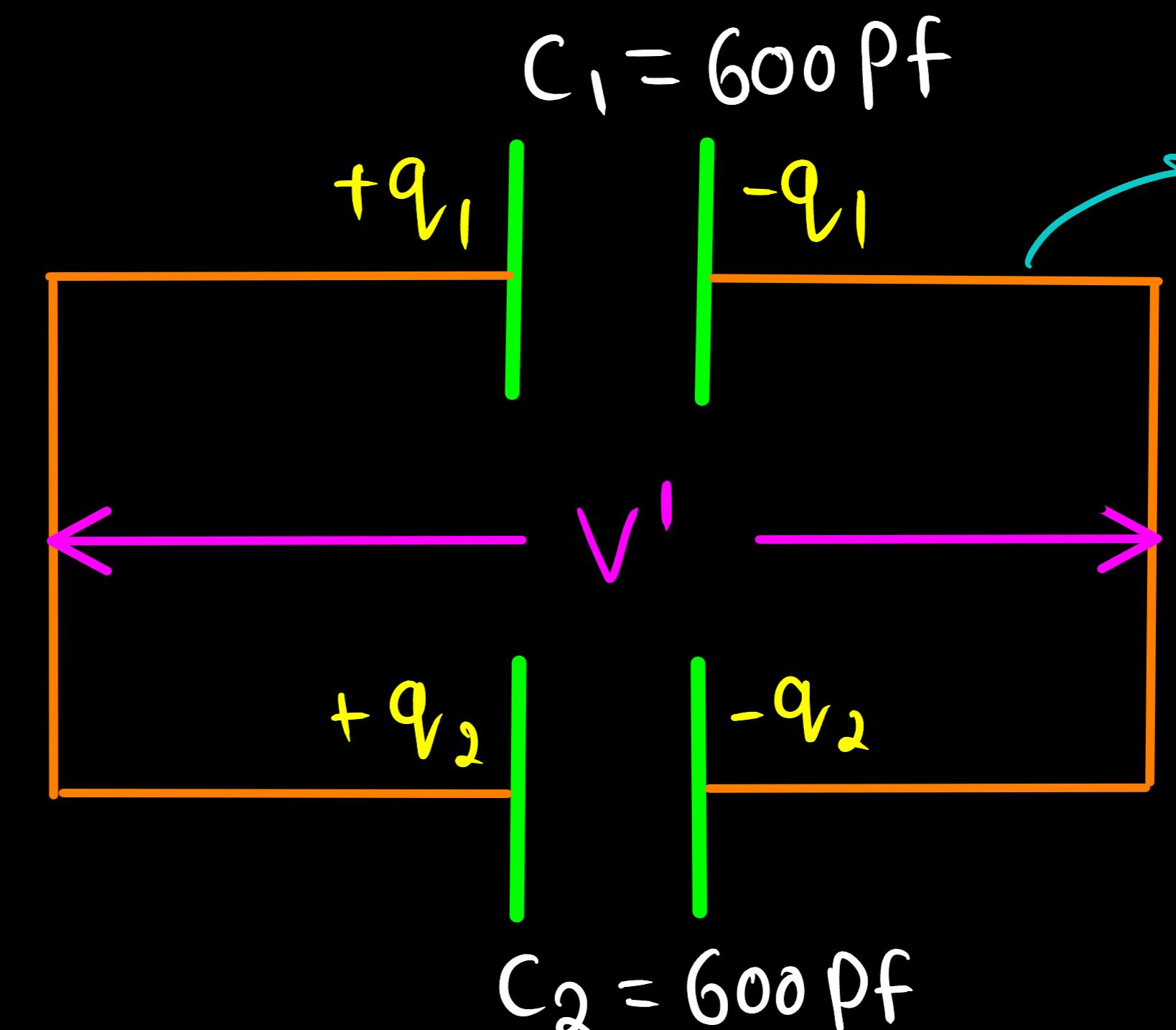
$$V' = \frac{q}{2C} = \frac{V}{2} = \frac{200}{2} = 100 \text{ V}$$



charge will flow from C_1 to C_2 until both capacitor have common potential.

$$q_1 + q_2 = q$$

↳ Conservation of Charge.

$$C' = C_1 + C_2 = 1200 \text{ pF}$$


final Potential Energy -

$$U_f = \frac{1}{2} C' V'^2$$

$$U_f = \frac{1}{2} \times 1200 \times 10^{-12} \times 100 \times 100$$

$$U_f = 6 \times 10^{-6} \text{ J}$$

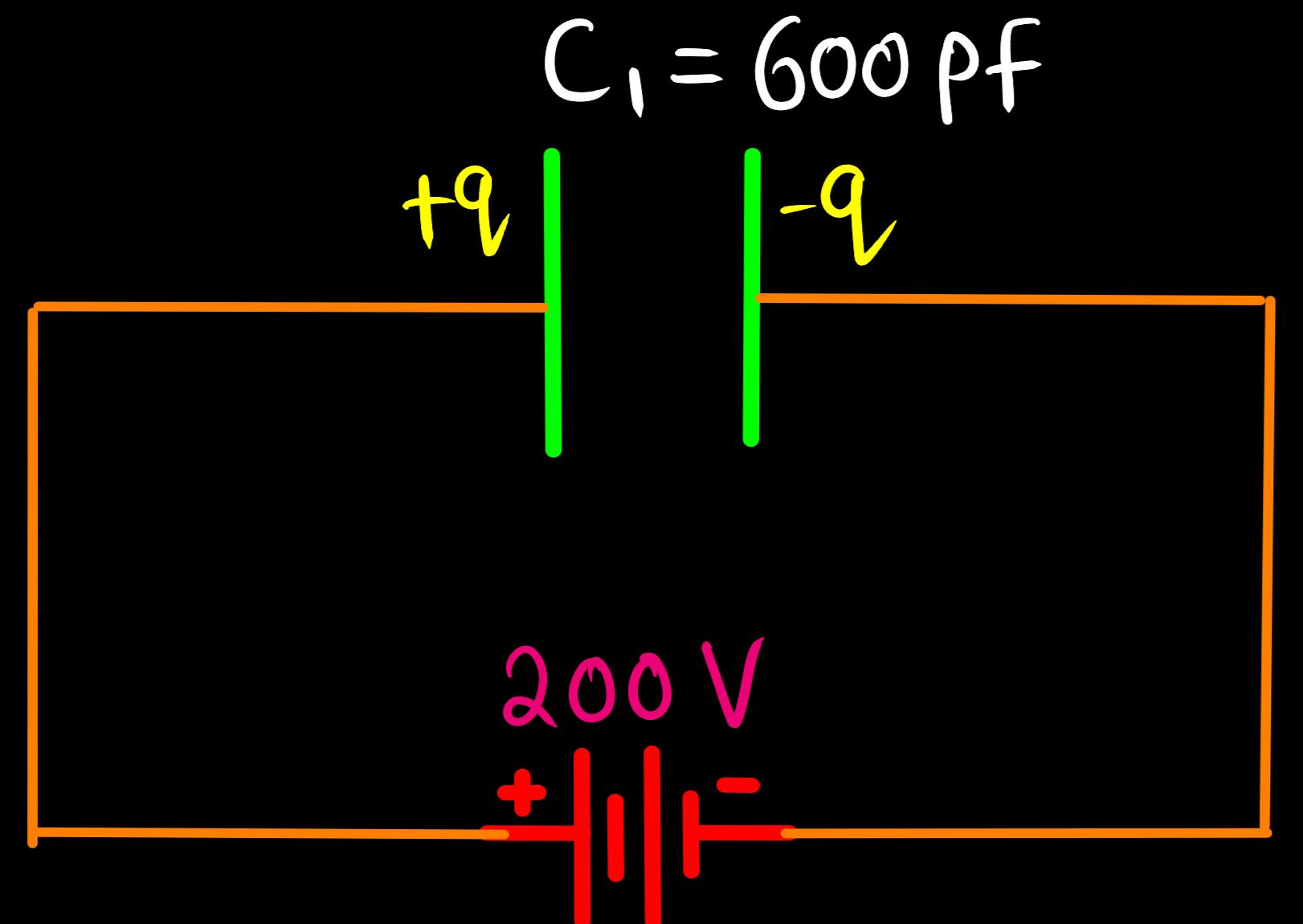2.11 A 600pF capacitor is charged by a 200V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. How much electrostatic energy is lost in the process?



* Initial potential energy


$$U_i = \frac{1}{2} C_1 V^2$$

$$U_i = \frac{1}{2} \times 600 \times 10^{-12} \times 200^2 \times 10^{-4}$$

$$U_i = 12 \times 10^{-6} \text{ J}$$

$$\text{Energy lost} = U_i - U_f = 12 \times 10^{-6} \text{ J} - 6 \times 10^{-6} \text{ J}$$
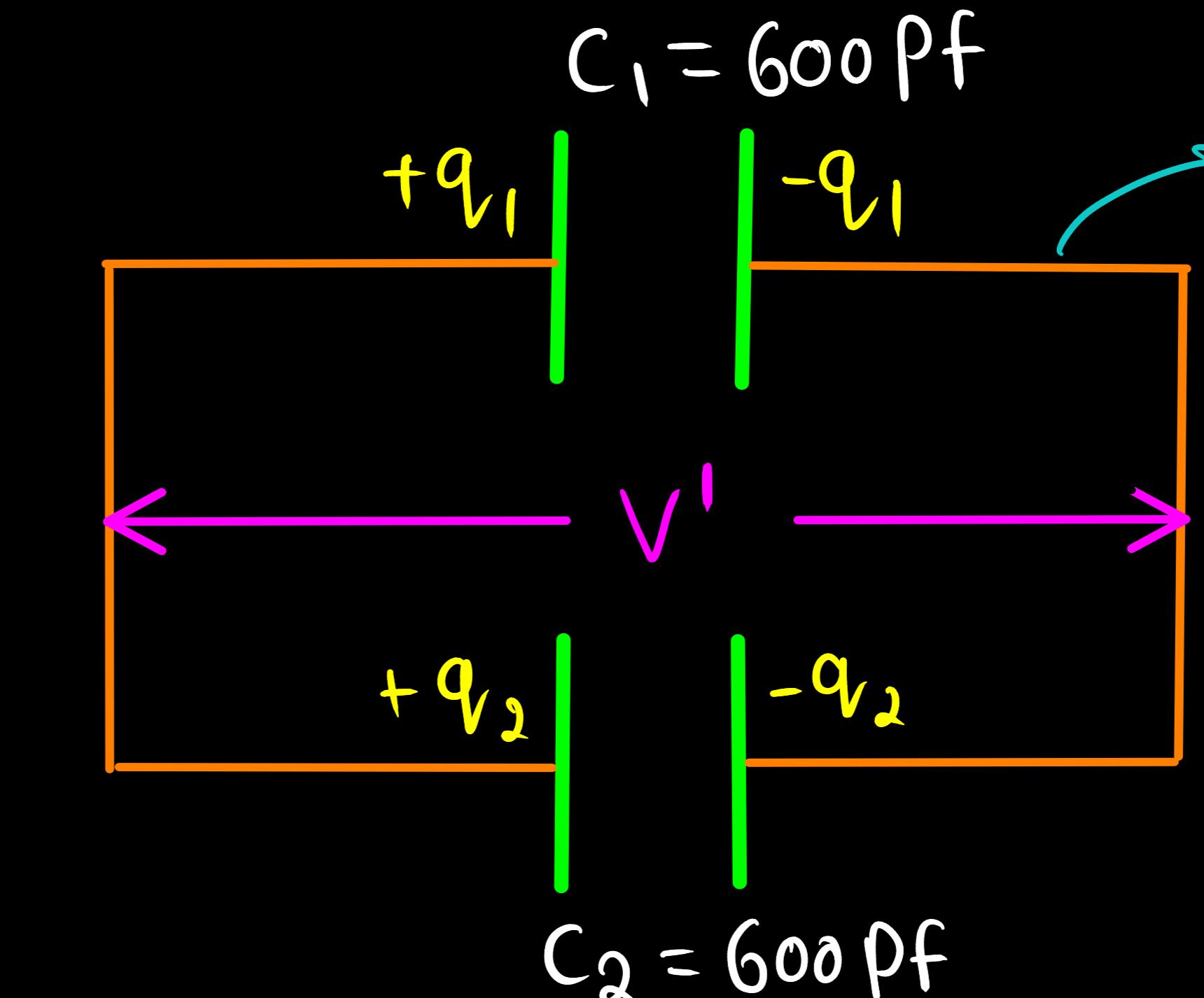
$$\boxed{\text{Energy lost} = 6 \times 10^{-6} \text{ J}}$$



Charge will flow from C_1 to C_2 until both capacitor have common potential.

$$q_1 + q_2 = q$$

↳ Conservation of Charge.

$$C' = C_1 + C_2 = 1200 \text{ pF}$$

final Potential Energy -

$$U_f = \frac{1}{2} C' V'^2$$

$$U_f = \frac{1}{2} \times 1200 \times 10^{-12} \times 100 \times 100$$

$$\boxed{U_f = 6 \times 10^{-6} \text{ J}}$$

$$* q_1 + q_2 = q$$

$$\frac{C}{V'} + \frac{C}{V'} = q$$

$$\frac{2C}{V'} = q$$

$$V' = \frac{q}{2C} = \frac{V}{2} = \frac{200}{2} = 100 \text{ V}$$