

Capacitance of a parallel plate capacitor, partly filled with dielectric

- * Consider a parallel plate capacitor having plates surface charge density $\pm\sigma$, Area A and plate separation d .
- * Suppose that a dielectric slab of thickness t and dielectric constant K is placed between the plates of the capacitor.
- * Electric field in the empty space between the plates -

$$E_1 = \frac{\sigma}{\epsilon_0}$$


- * Electric field inside the dielectric slab -

$$E_2 = \frac{\sigma}{K\epsilon_0}$$

- * The potential difference between the plates -

$$V = E_1(d-t) + E_2 t \quad (\because V = -\int E \cdot dx)$$
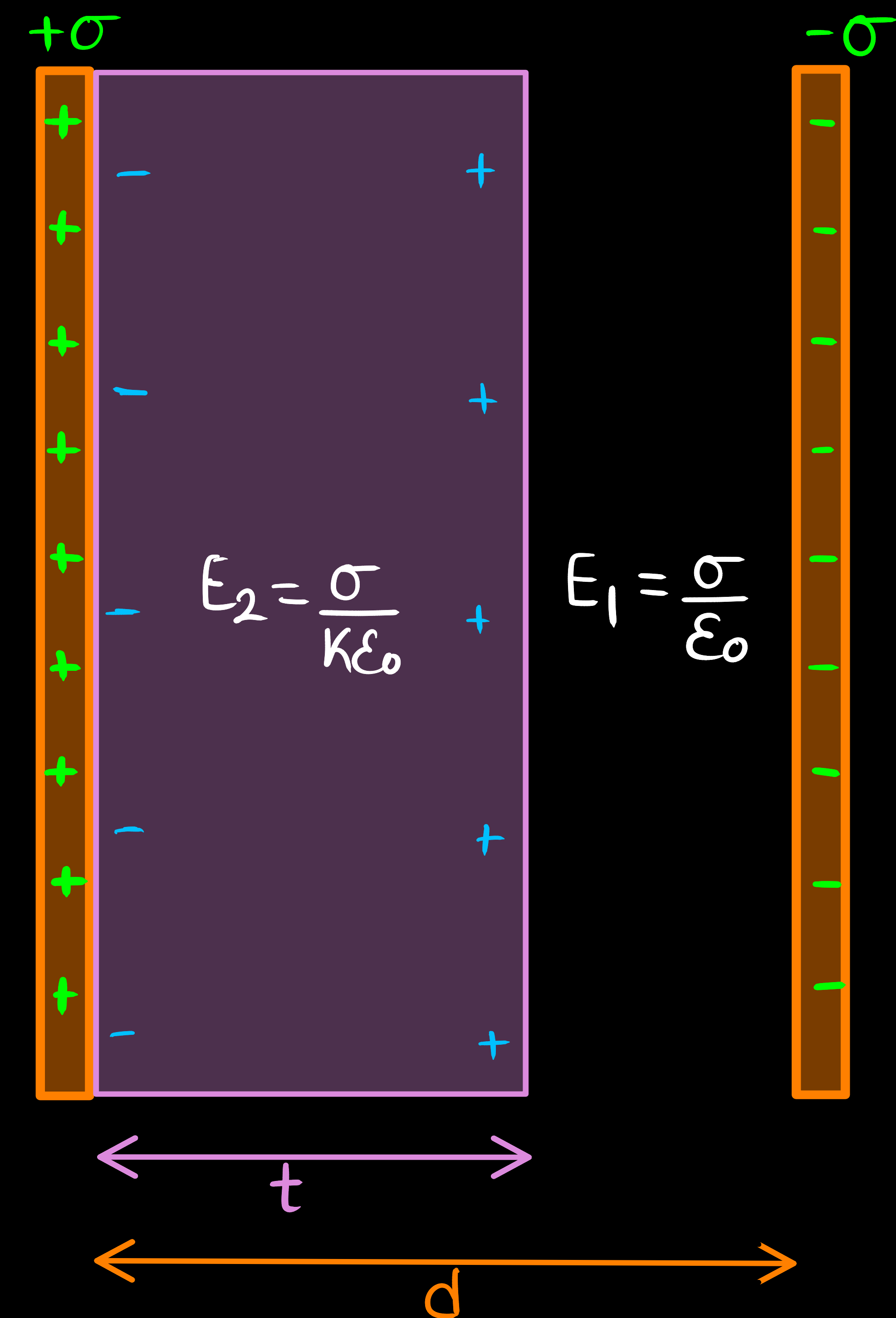
$$V = \frac{\sigma}{\epsilon_0}(d-t) + \frac{\sigma}{K\epsilon_0} t$$



$$V = \frac{\sigma}{\epsilon_0} \left(d - t + \frac{t}{K} \right)$$

Now capacitance -

$$C = \frac{Q}{V} = \frac{\sigma A}{V}$$

$$C = \frac{\cancel{\sigma} A}{\cancel{\frac{\sigma}{\epsilon_0}} \left(d - t + \frac{t}{K} \right)}$$

$$C = \frac{\epsilon_0 A}{\left(d - t + \frac{t}{K} \right)}$$



Combination of capacitors

i) Capacitors in series -

- * Consider three capacitors of capacitance C_1 , C_2 , and C_3 , connected in series to a battery of potential difference (V).
- * In series combination charges on the two plates are same on each capacitor.
- * The total potential drop (V) across the combination is the sum of the potential drop V_1 , V_2 , and V_3 across C_1 , C_2 and C_3 respectively

$$V = V_1 + V_2 + V_3$$
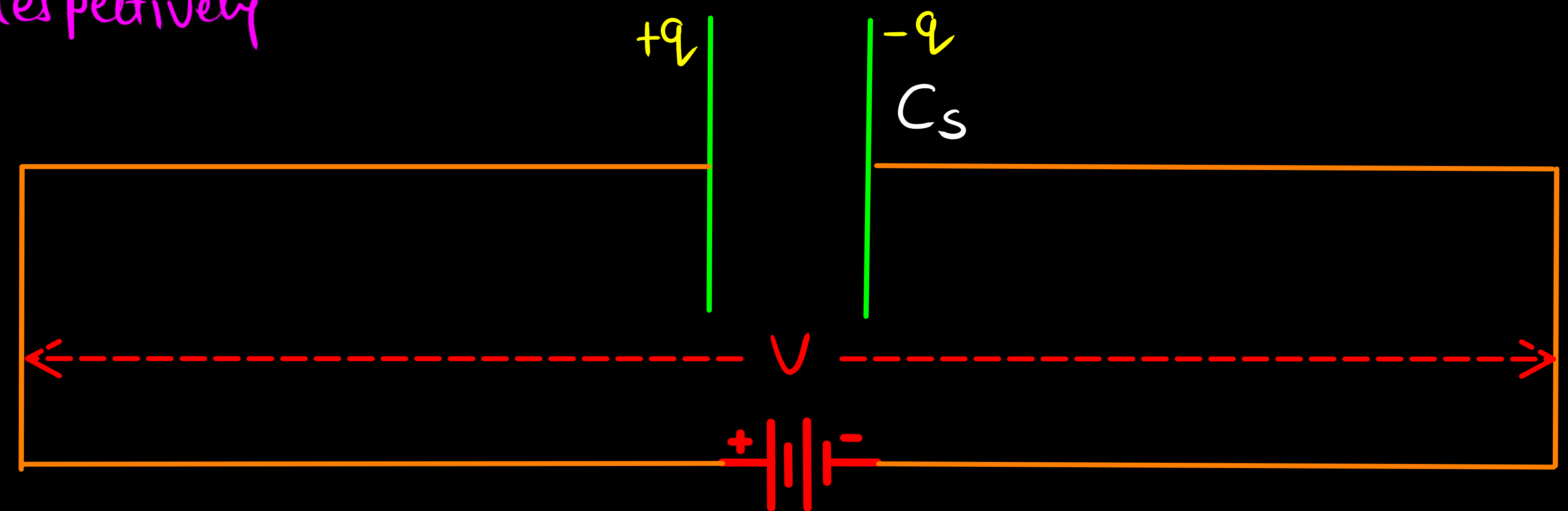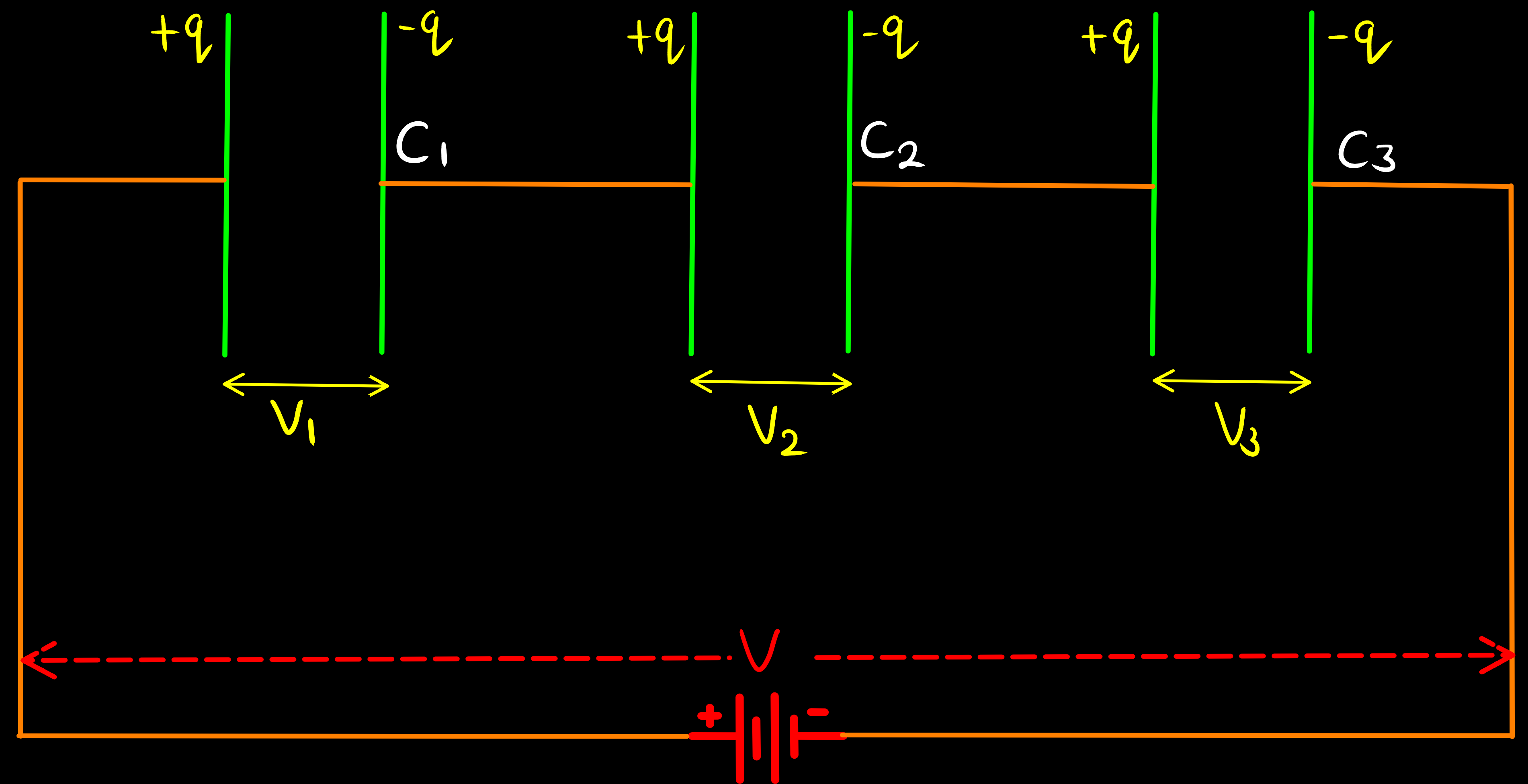
$$V = \frac{q}{C_1} + \frac{q}{C_2} + \frac{q}{C_3} \quad \text{--- (1)}$$



Combination of capacitors


* The effective capacitance of the combination -

$$V = \frac{q}{C_s} \quad \text{--- (2)}$$

* from eqⁿ (1) & (2)

$$\frac{q}{C_s} = \frac{q}{C_1} + \frac{q}{C_2} + \frac{q}{C_3}$$
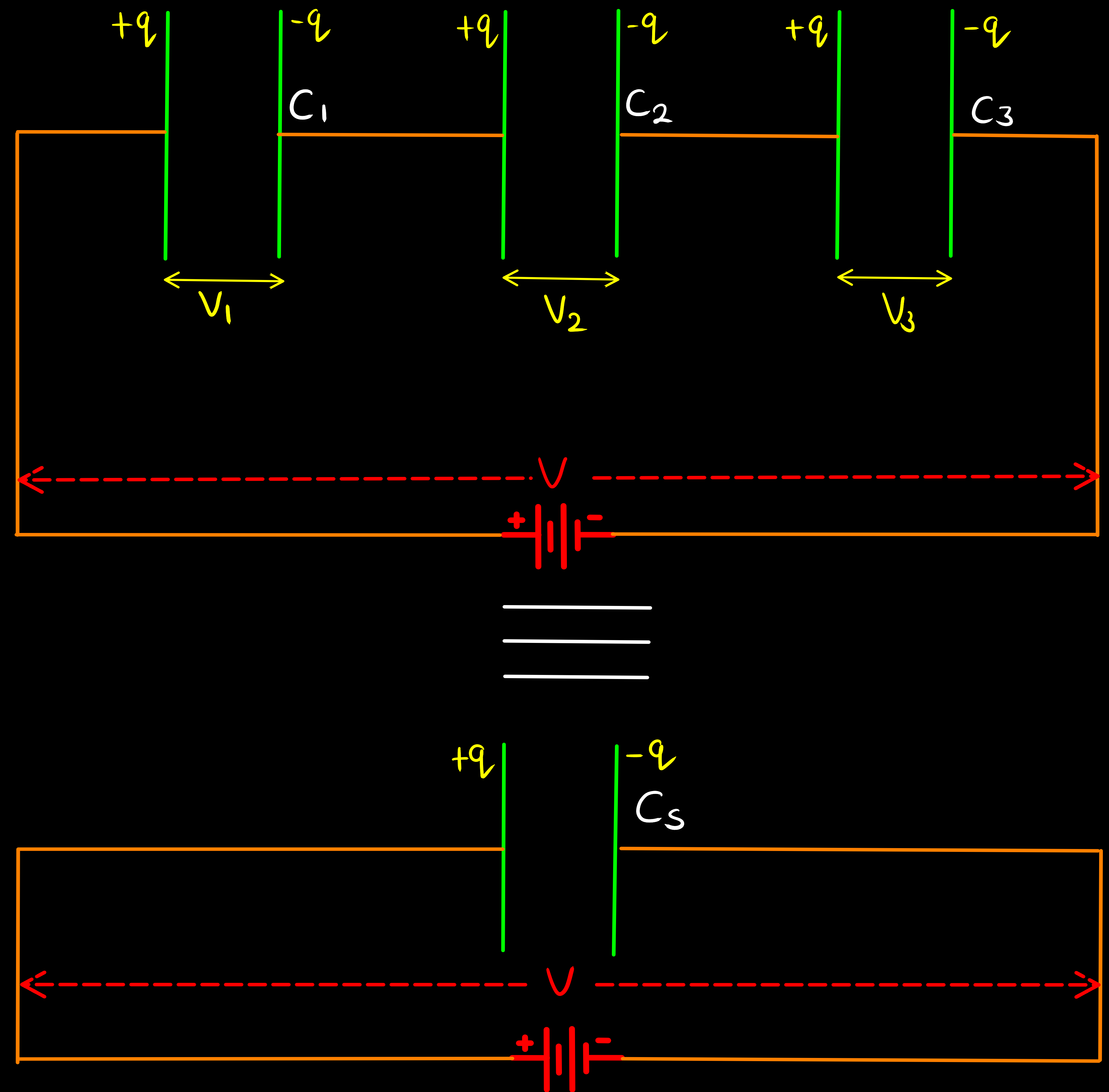
$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$



ii) Capacitors in parallel-

* Consider three capacitors of capacitance C_1 , C_2 and C_3 , connected in parallel with a battery of potential difference (V)

* In parallel combination potential difference is same across each capacitor.

* The charge stored in each capacitor -
 $q_1 = C_1 V$, $q_2 = C_2 V$, $q_3 = C_3 V$

* Total charge supplied by the battery -

$$q = q_1 + q_2 + q_3$$


$$q = C_1 V + C_2 V + C_3 V$$

$$q = V [C_1 + C_2 + C_3] \quad \text{--- (1)}$$



* Also, $q = C_p V$ --- (2)

* from eqn (1) & (2) $\rightarrow C_p V = V [C_1 + C_2 + C_3]$

$$C_p = C_1 + C_2 + C_3$$

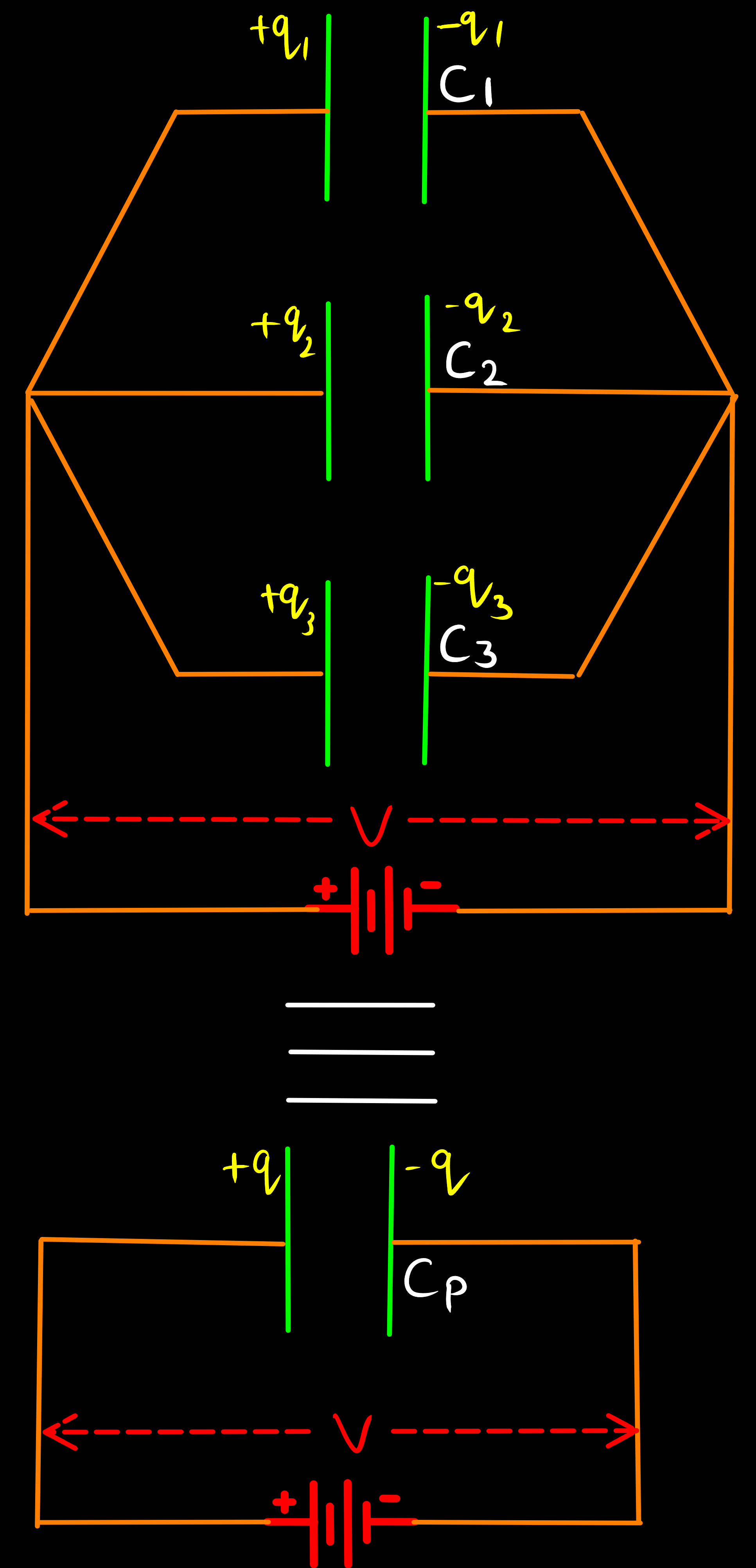

* Some important Concepts-

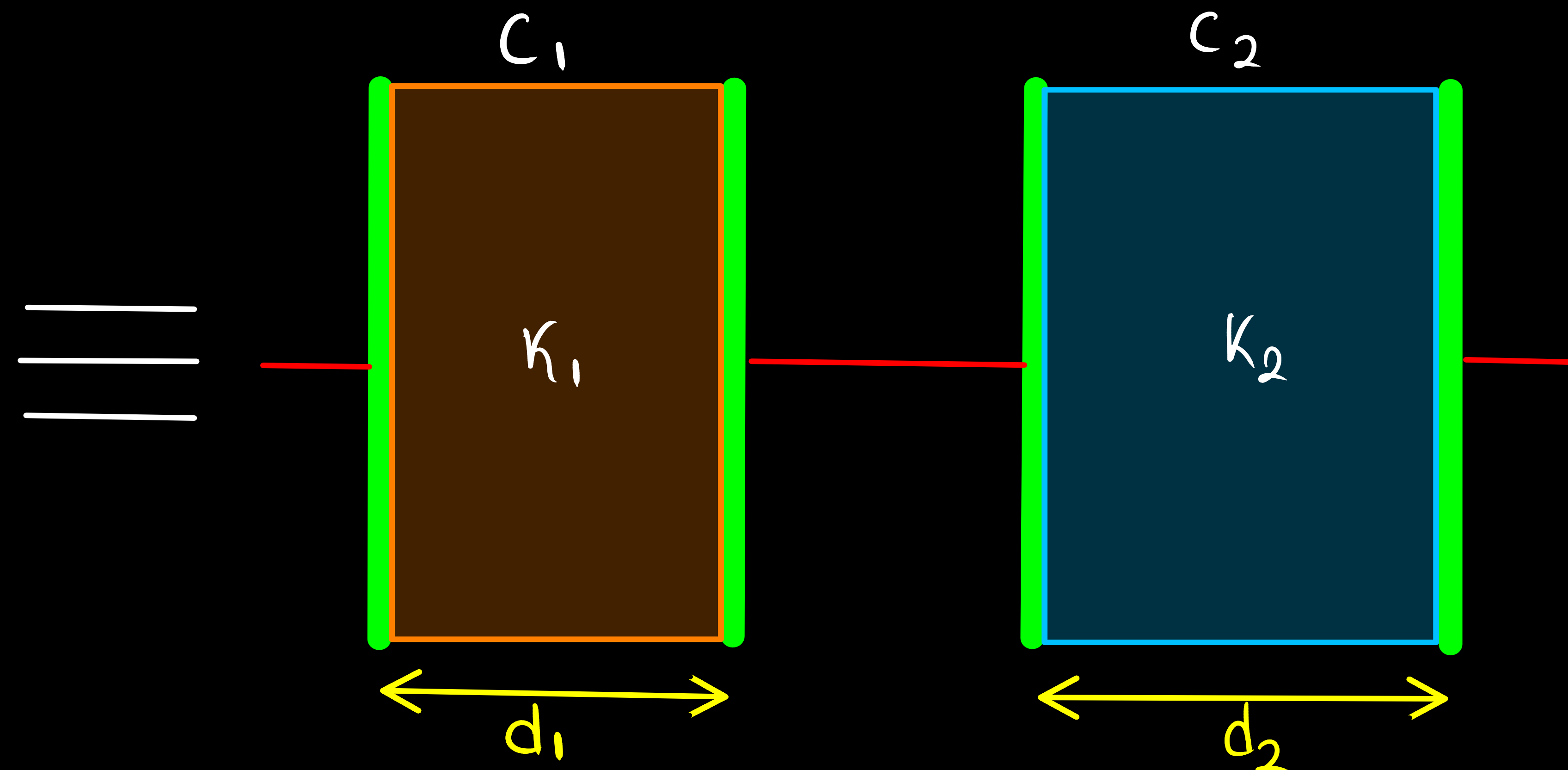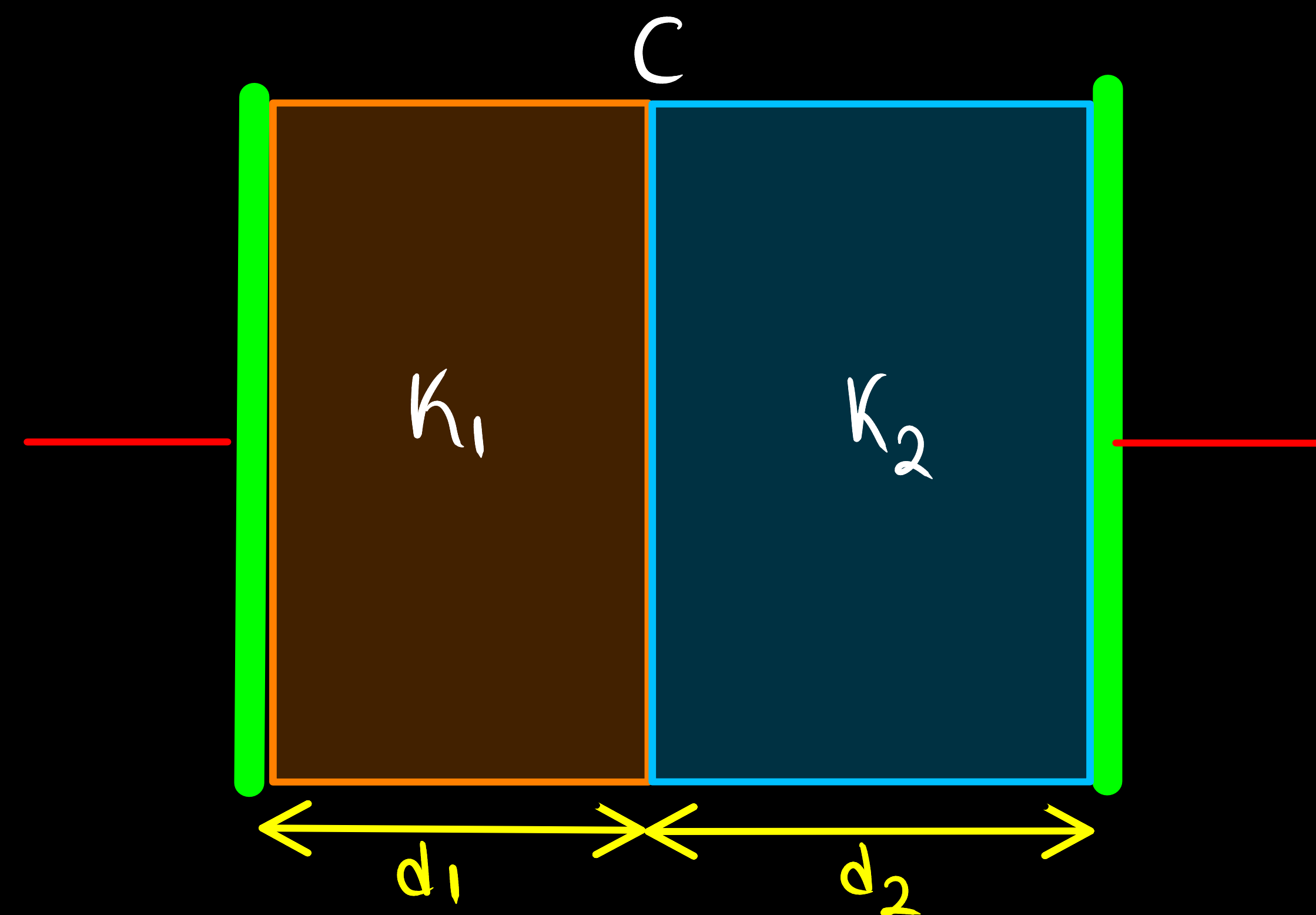



$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C} = \frac{1}{\frac{K_1 \epsilon_0 A}{d_1}} + \frac{1}{\frac{K_2 \epsilon_0 A}{d_2}}$$

$$\frac{1}{C} = \frac{d_1}{K_1 \epsilon_0 A} + \frac{d_2}{K_2 \epsilon_0 A}$$

$$\frac{1}{C} = \frac{1}{\epsilon_0 A} \left[\frac{d_1}{K_1} + \frac{d_2}{K_2} \right]$$
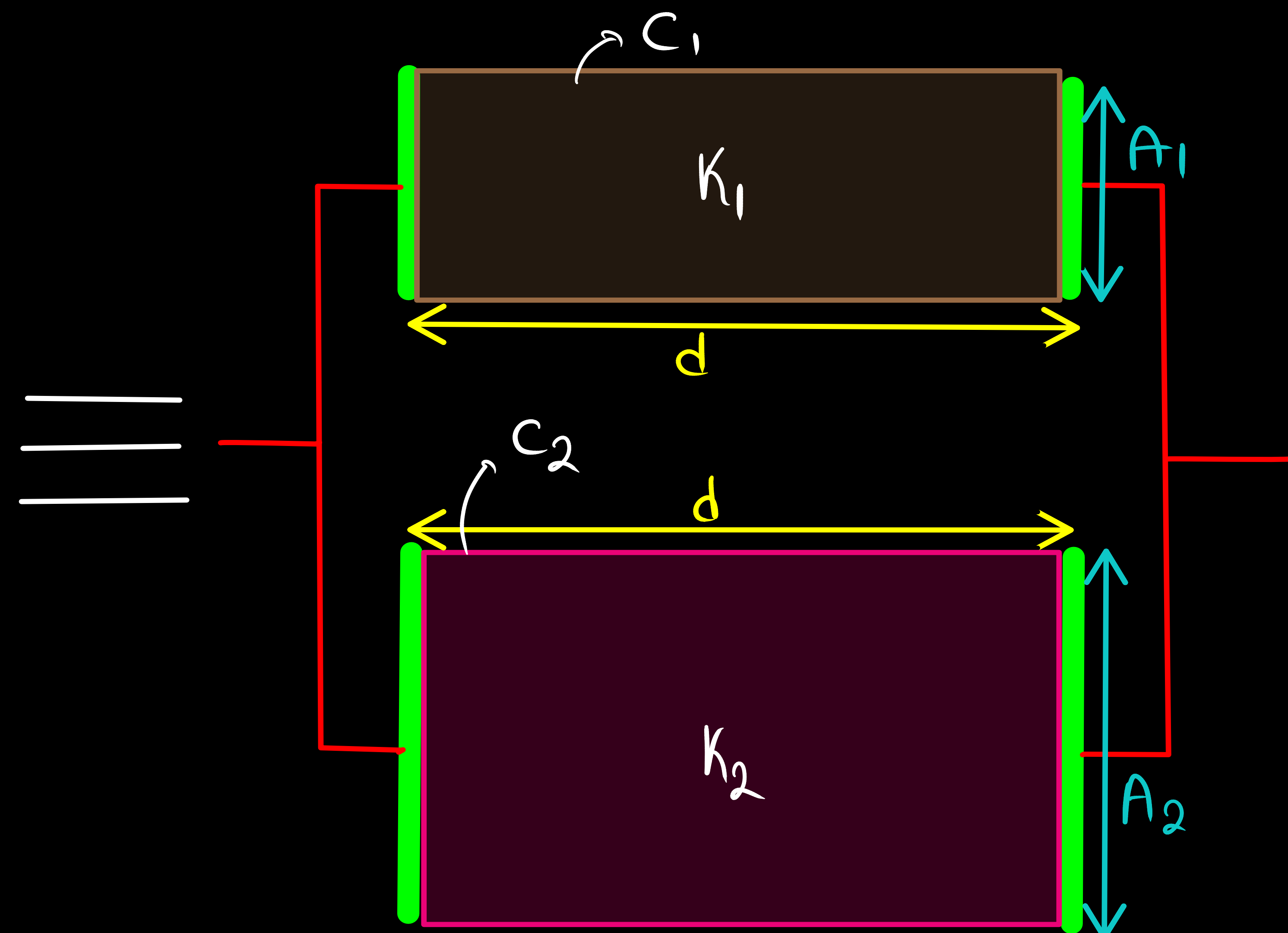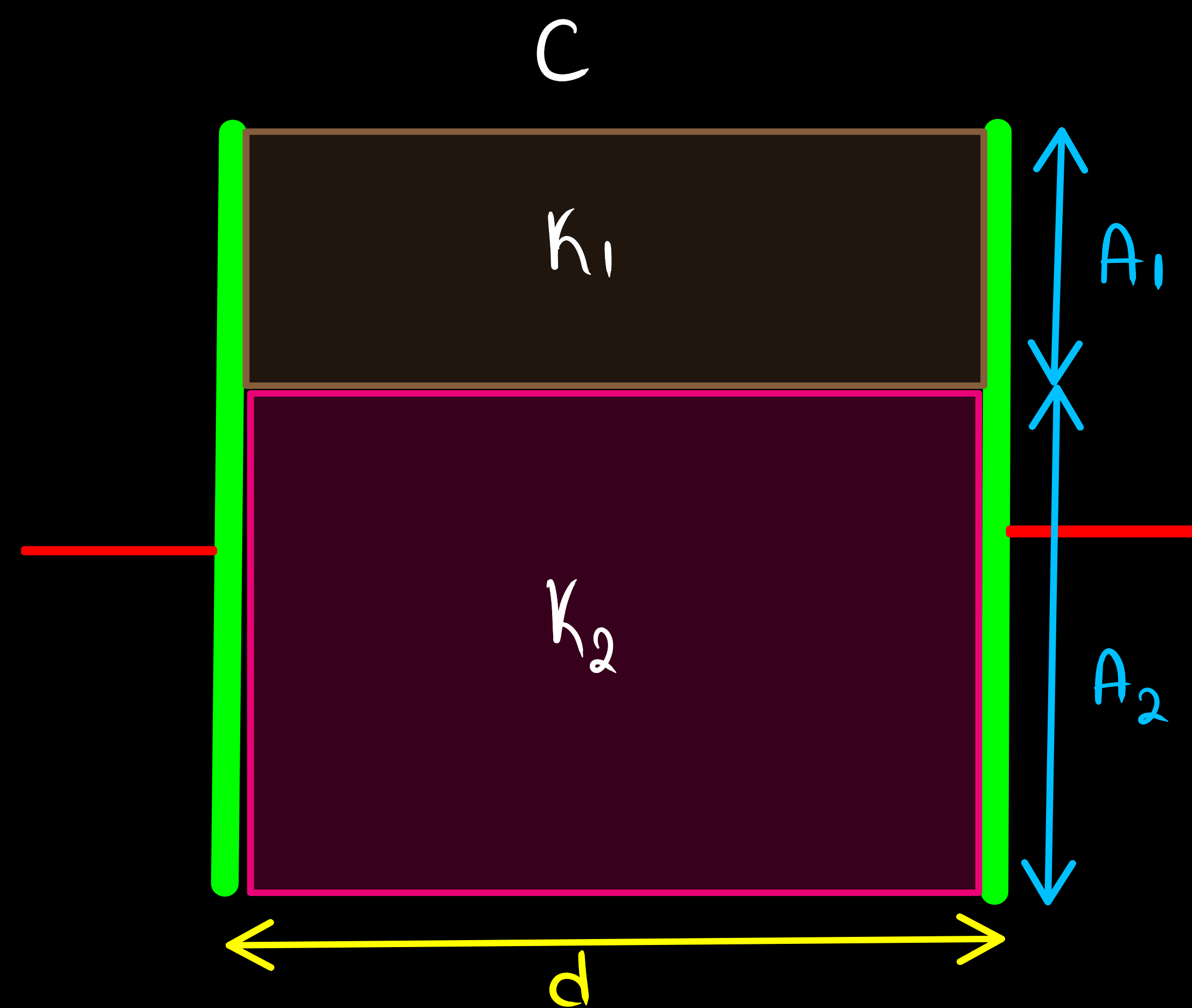
$$C = \frac{\epsilon_0 A}{\left[\frac{d_1}{K_1} + \frac{d_2}{K_2} \right]}$$



$$C = C_1 + C_2$$

$$C = \frac{K_1 \epsilon_0 A_1}{d} + \frac{K_2 \epsilon_0 A_2}{d}$$

$$C = \frac{\epsilon_0}{d} (K_1 A_1 + K_2 A_2)$$

Energy Stored in a Capacitor

- * Let q and V be the charge and potential respectively at an intermediate stage during charging process. Then

$$V = \frac{q}{C}$$

- * At this stage the work required to add a very small amount of charge dq is


$$dW = V dq = \frac{q}{C} dq$$

- * So, Total work needed to increase the charge q from 0 to final charge Q .

$$W = \int_0^Q \frac{q}{C} dq$$

$$W = \frac{1}{C} \int_0^Q q dq = \frac{1}{C} \frac{q^2}{2} \Big|_0^Q$$

$$W = \frac{1}{2} \frac{Q^2}{C}$$

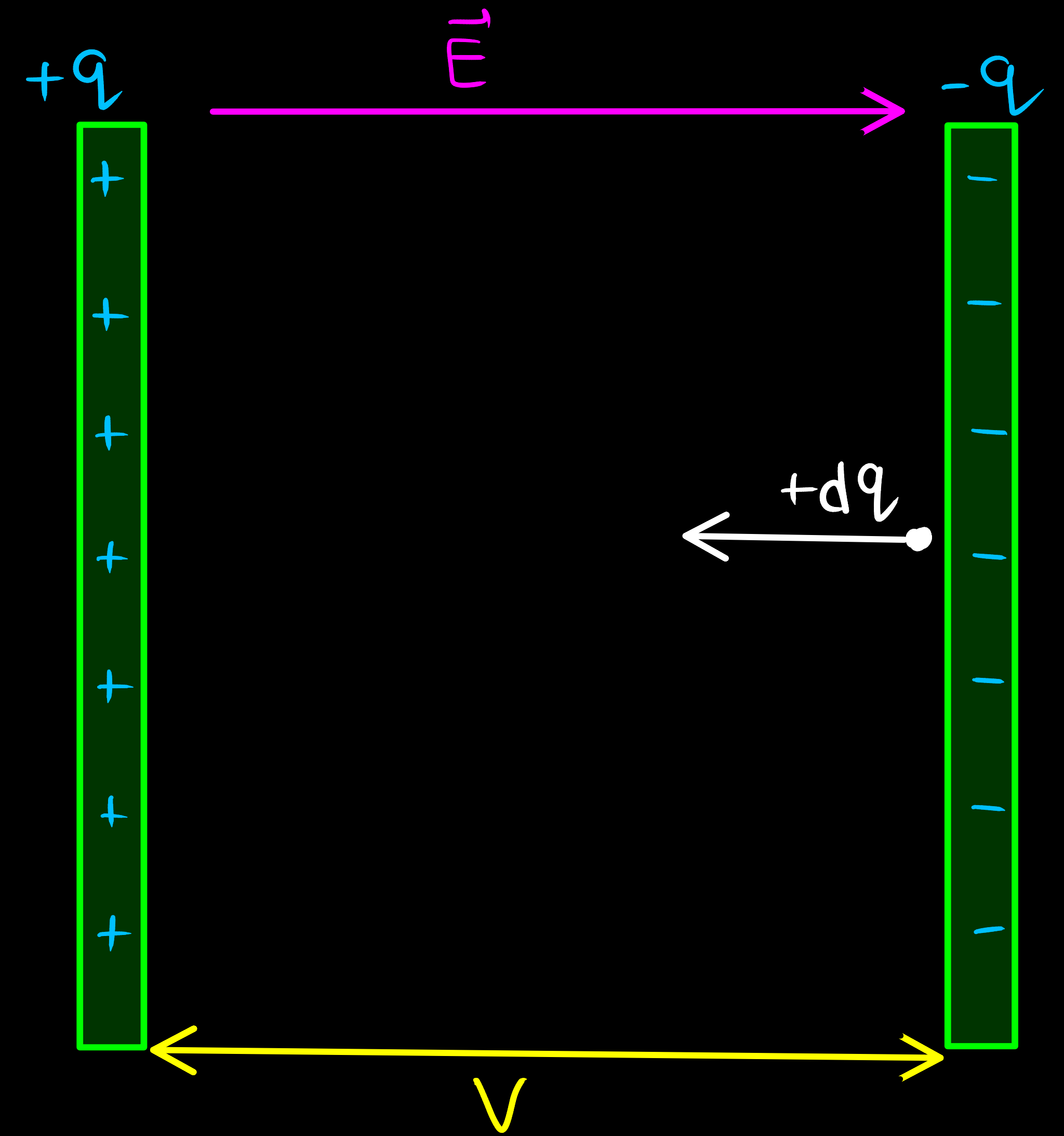

- * This work done by external agency (battery) is stored as Potential Energy of the capacitor.

$$U = \frac{1}{2} \frac{Q^2}{C}$$

Also, $Q = CV$

$$U = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} CV^2 = \frac{1}{2} QV$$

* Energy Density (u) - It is defined as energy stored per unit volume of the space between the plates of the capacitor.

$$u = \frac{U}{\text{Volume}}$$

$$u = \frac{1}{2} \frac{CV^2}{Ad}$$

for parallel plate capacitor $\rightarrow C = \frac{\epsilon_0 A}{d}$

$$u = \frac{1}{2} \frac{\epsilon_0 A V^2}{d A d}$$


$$u = \frac{1}{2} \epsilon_0 \times \left(\frac{V}{d}\right)$$

$$u = \frac{1}{2} \epsilon_0 E^2$$


$$\left(\because E = \frac{V}{d} \right)$$

* It is possible to view the potential energy of the capacitor as 'Stored' in the electric field between the plates.

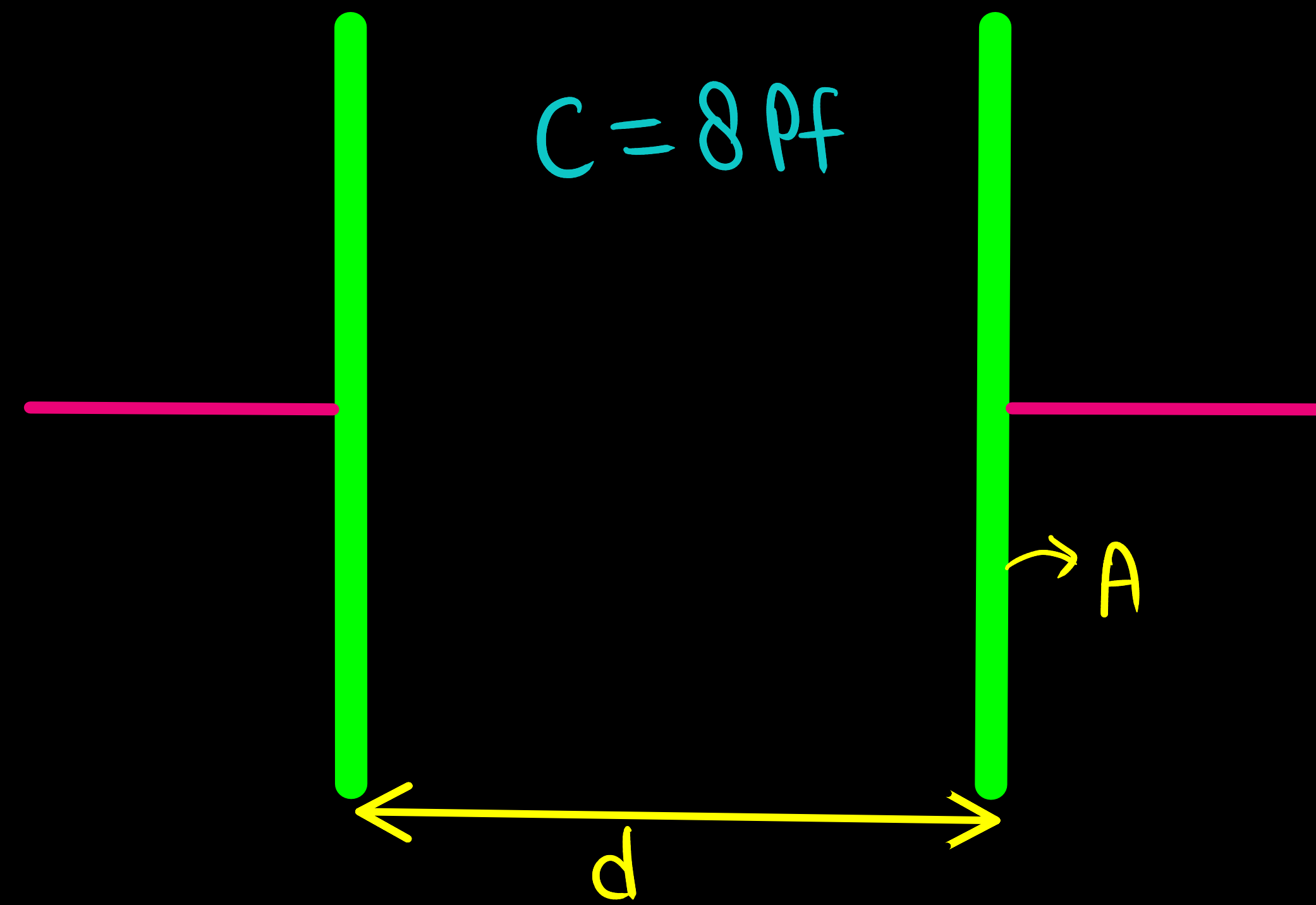2.5 A parallel plate capacitor with air between the plates has a capacitance of 8 pF ($1\text{pF} = 10^{-12}\text{ F}$). What will be the capacitance if the distance between the plates is reduced by half, and the space between them is filled with a substance of dielectric constant 6?


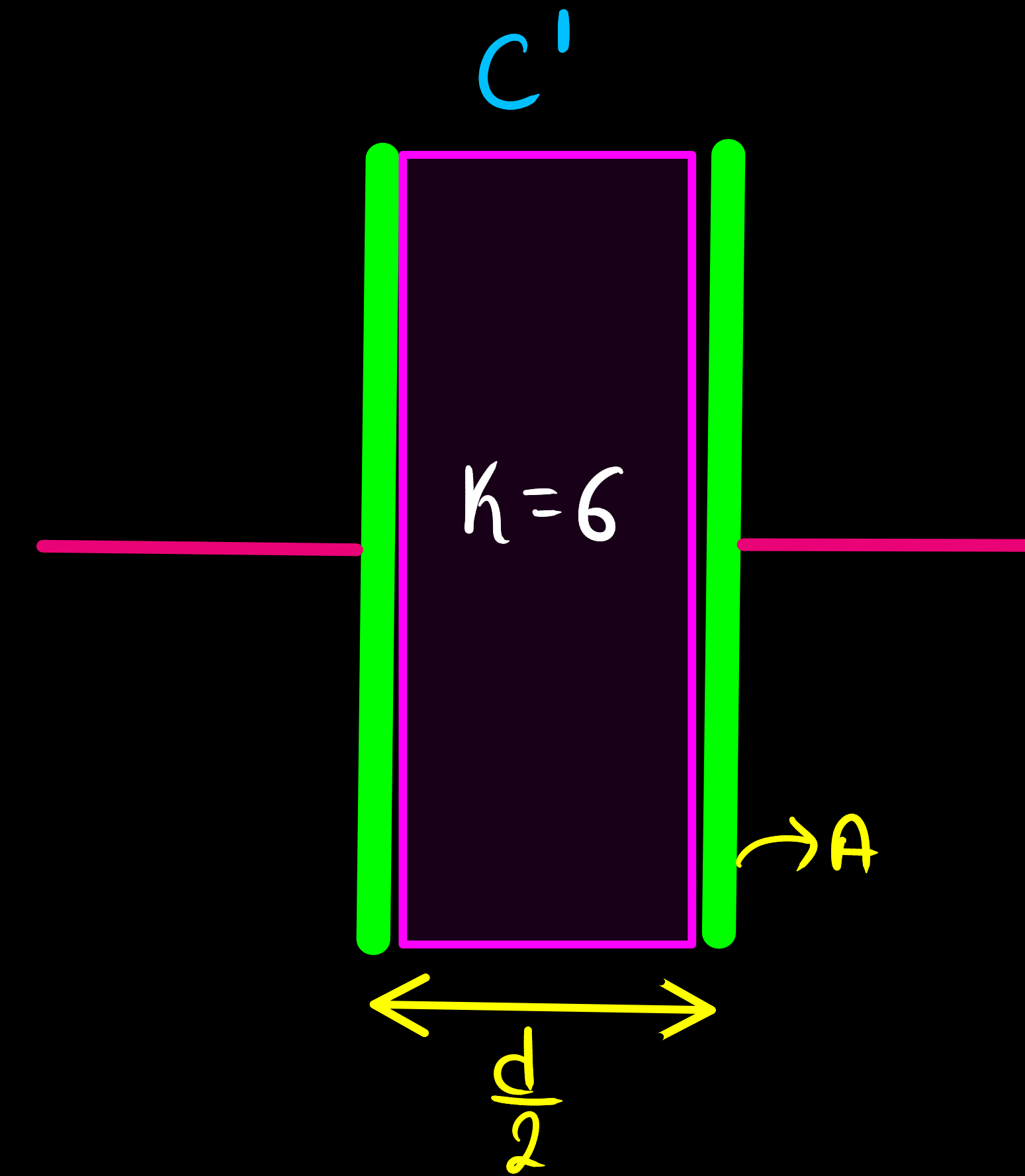
$$C = \frac{\epsilon_0 A}{d} = 8\text{ pF}$$



$$C' = \frac{k \epsilon_0 A}{\frac{d}{2}}$$

$$C' = 2k \frac{\epsilon_0 A}{d}$$

$$C' = 2 \times 6 \times 8\text{ pF} = 96\text{ pF}$$

2.8 In a parallel plate capacitor with air between the plates, each plate has an area of $6 \times 10^{-3} \text{ m}^2$ and the distance between the plates is 3 mm. Calculate the capacitance of the capacitor. If this capacitor is connected to a 100 V supply, what is the charge on each plate of the capacitor?

i)


$$C = \frac{\epsilon_0 A}{d}$$
$$C = \frac{8.854 \times 10^{-12} \times 6 \times 10^{-3}}{3 \times 10^{-3}}$$

$$C = 17.708 \times 10^{-12} \text{ F}$$

ii)

$$Q = CV$$
$$Q = 17.708 \times 10^{-12} \times 100 \text{ C}$$


$$Q = 1.7708 \times 10^{-9} \text{ C}$$

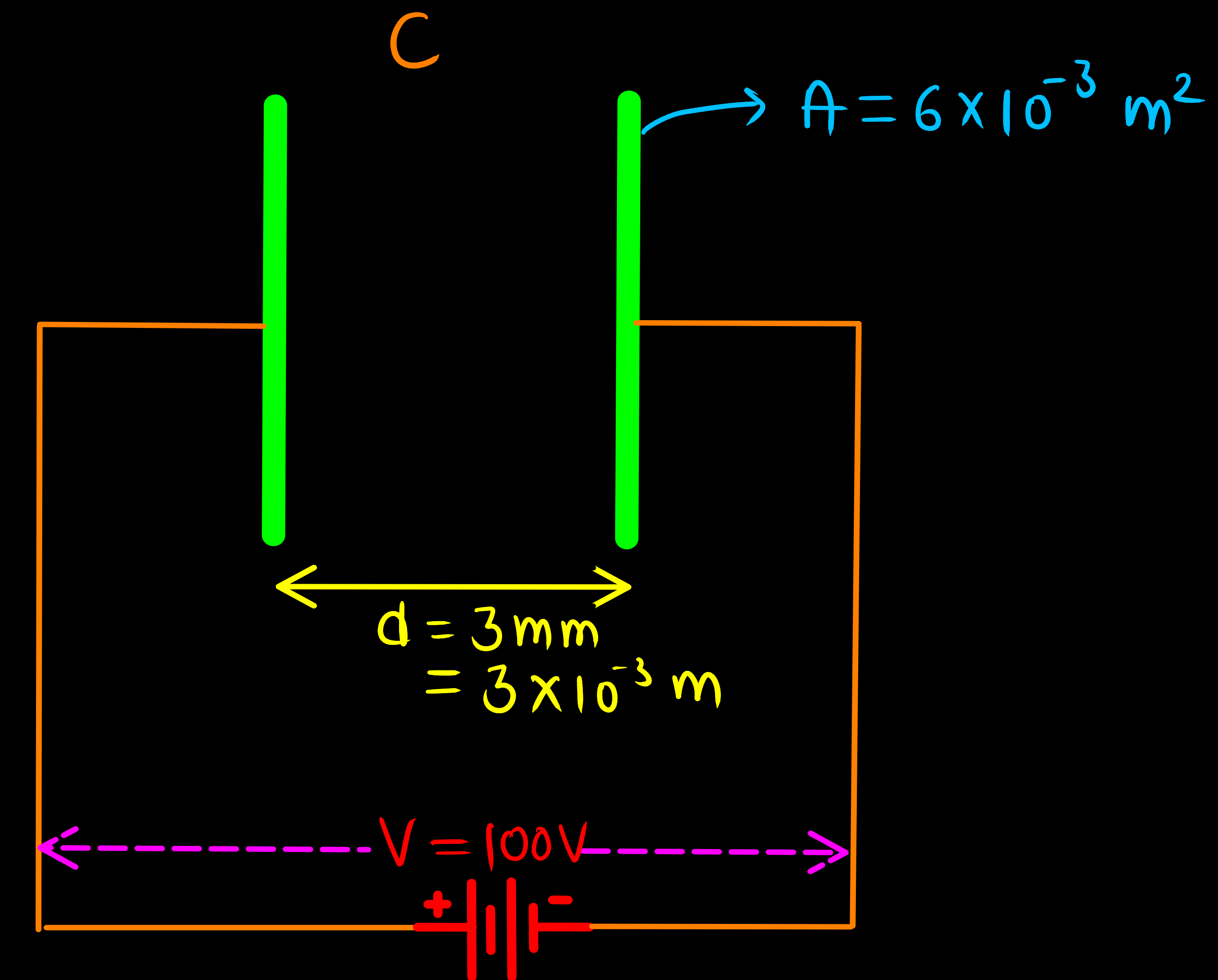

2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,

- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.

a)

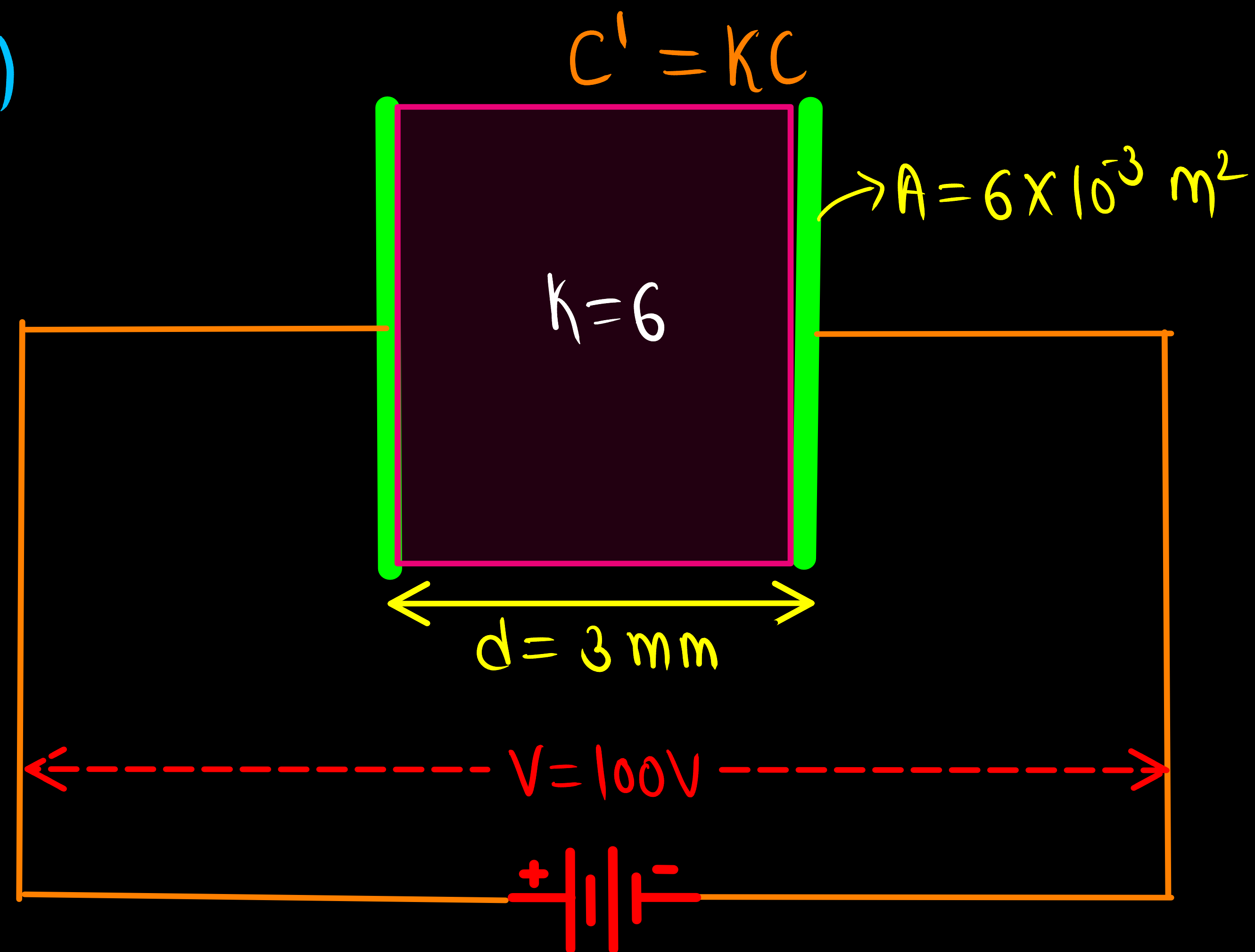

* when voltage supply remained connected & dielectric is inserted.

$V' = V$ remains constant

$C' = KC$ Capacitance increases

$$Q' = C'V$$

$$Q' = KCV$$

$Q' = KQ \rightarrow$ Capacitance increases

from previous question $Q = 17.708 \times 10^{-10} C$


$$Q' = 6 \times 17.708 \times 10^{-10} C$$

$$Q' = 106.248 \times 10^{-10} C$$

2.9 Explain what would happen if in the capacitor given in Exercise 2.8, a 3 mm thick mica sheet (of dielectric constant = 6) were inserted between the plates,

- (a) while the voltage supply remained connected.
- (b) after the supply was disconnected.

b)

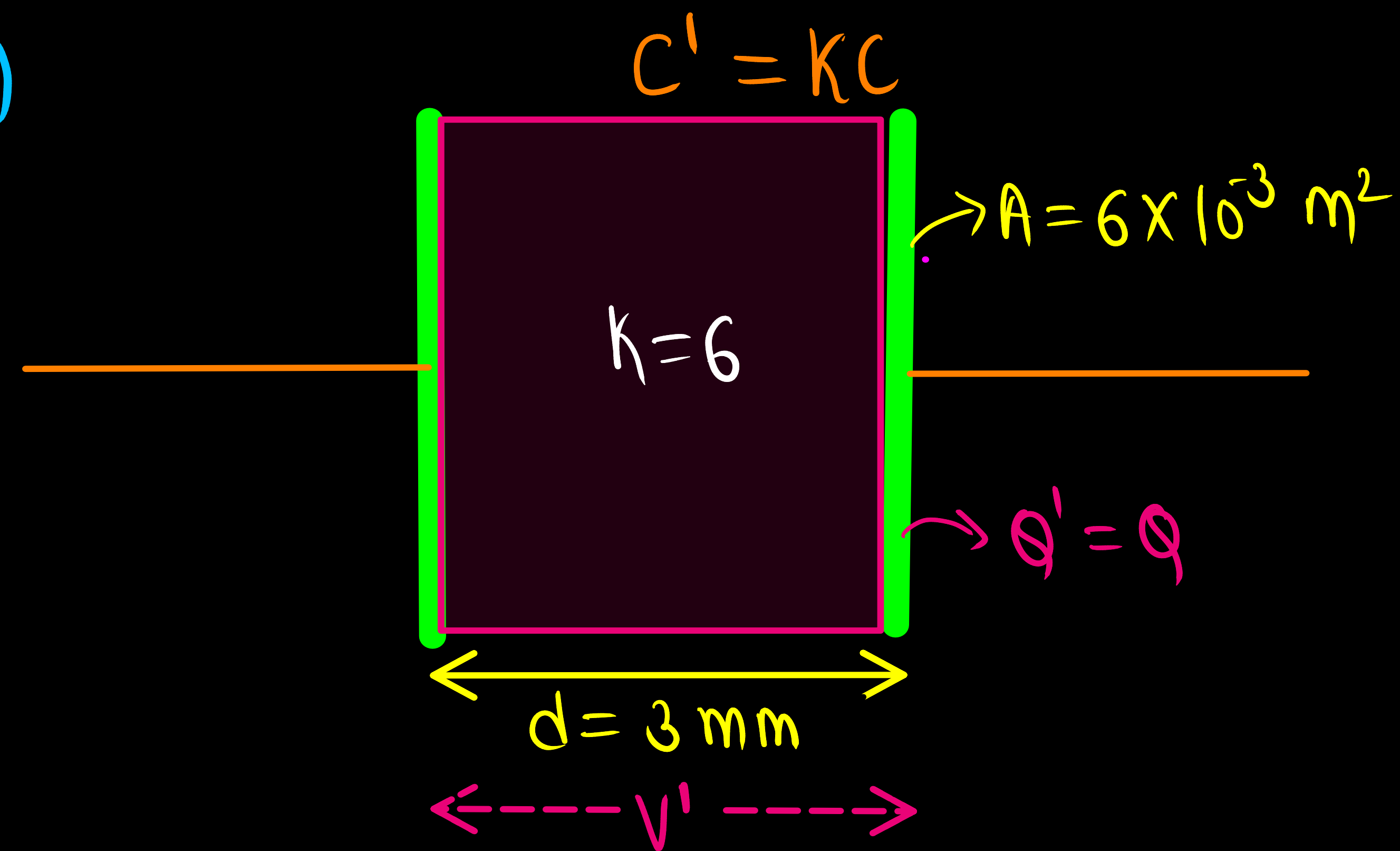

* When dielectric is inserted after the supply was disconnected.

$$Q' = Q \rightarrow \text{Charge on Capacitor Plate remains constant}$$

$$C' = KC \rightarrow \text{Capacitance increases}$$


$$V' = \frac{Q'}{C'}$$

$$V' = \frac{Q}{Kc}$$


$$V' = \frac{V}{K} \quad \left(\because \frac{Q}{C} = V \right)$$

\rightarrow Voltage decreases $\frac{1}{K}$ times.

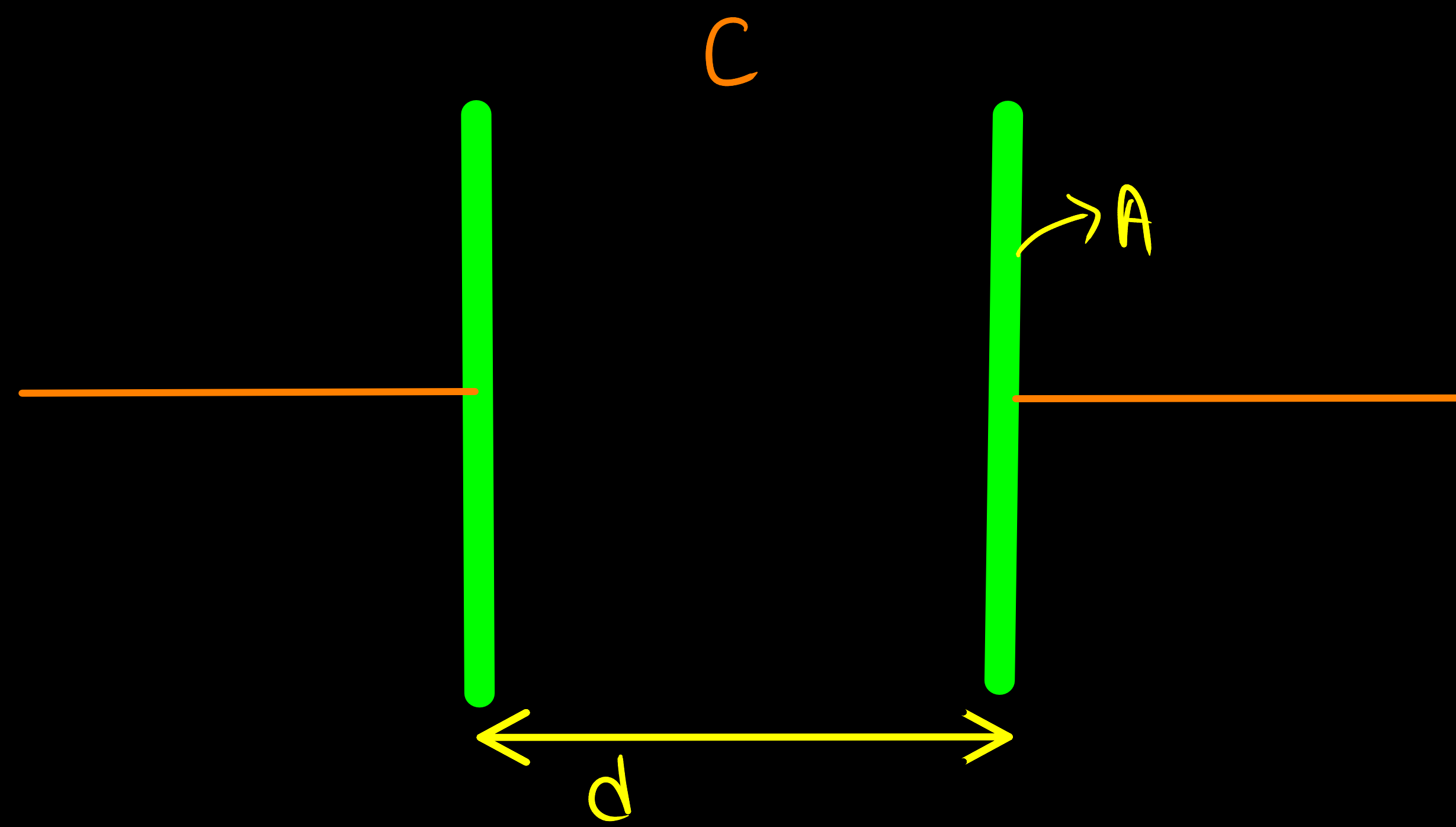Example 2.8 A slab of material of dielectric constant K has the same area as the plates of a parallel-plate capacitor but has a thickness $(3/4)d$, where d is the separation of the plates. How is the capacitance changed when the slab is inserted between the plates?



$$C = \frac{\epsilon_0 A}{d}$$

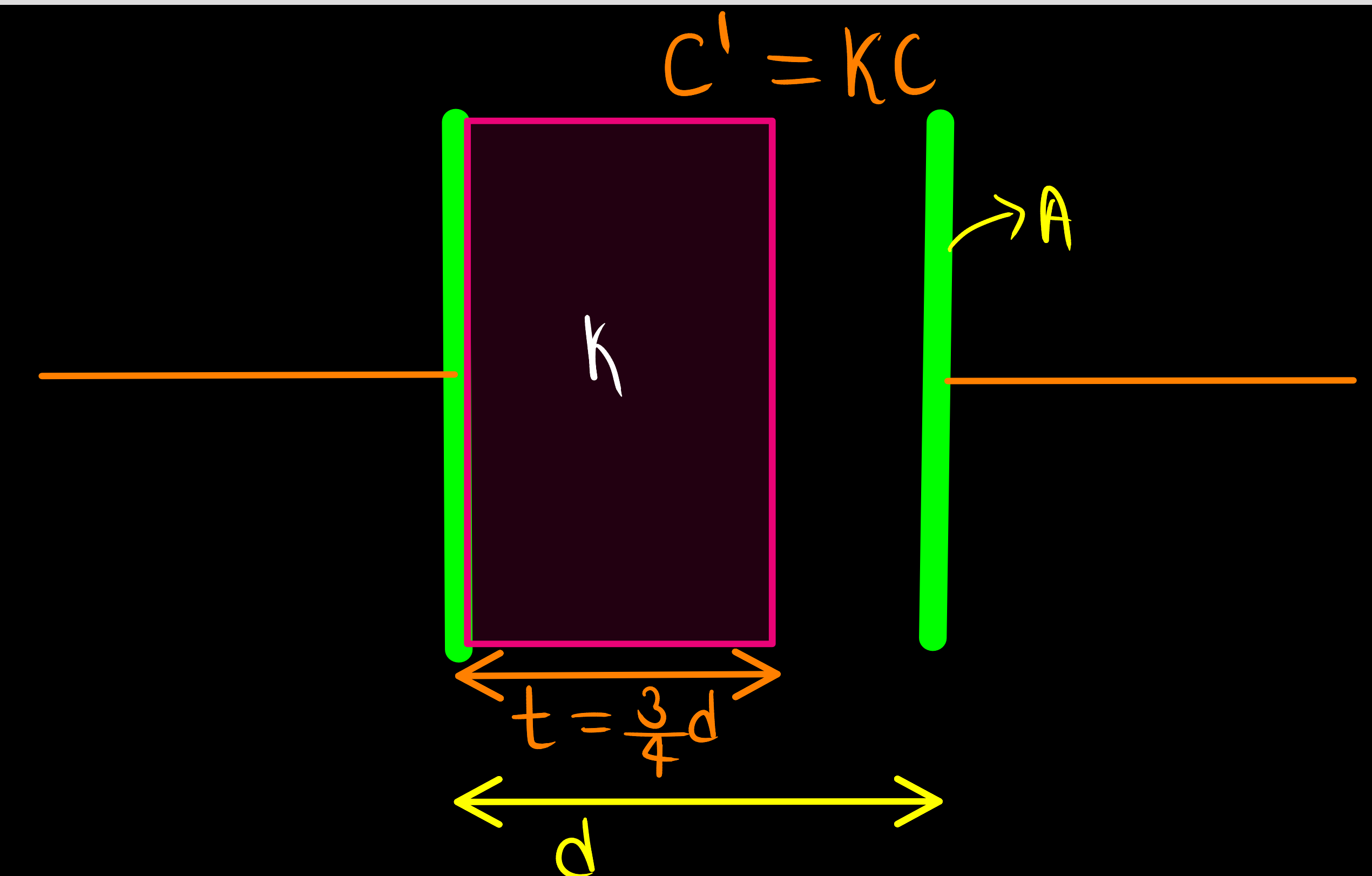

$$C' = \frac{\epsilon_0 A}{\left(d - t + \frac{t}{K}\right)}$$

$$C' = \frac{\epsilon_0 A}{\left(d - \frac{3d}{4} + \frac{3d}{4K}\right)} = \frac{\epsilon_0 A}{\left(\frac{d}{4} + \frac{3d}{4K}\right)}$$

$$C' = \frac{4\epsilon_0 A}{d\left(1 + \frac{3}{K}\right)} = \frac{4K}{(K+3)} C$$

2.6 Three capacitors each of capacitance 9 pF are connected in series.

- (a) What is the total capacitance of the combination?
- (b) What is the potential difference across each capacitor if the combination is connected to a 120 V supply?

* (a)

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C} = \frac{1}{9} + \frac{1}{9} + \frac{1}{9}$$

$$\frac{1}{C} = \frac{3}{9} = \frac{1}{3}$$

$$C = 3 \text{ pF}$$


* b)

Charge stored by all capacitors -

$$q_1 = q_2 = q_3 = q \rightarrow (\text{In series } q \rightarrow \text{same})$$

$$q = CV = 3 \times 10^{-12} \times 120$$

$$q = 360 \times 10^{-12} \text{ C}$$

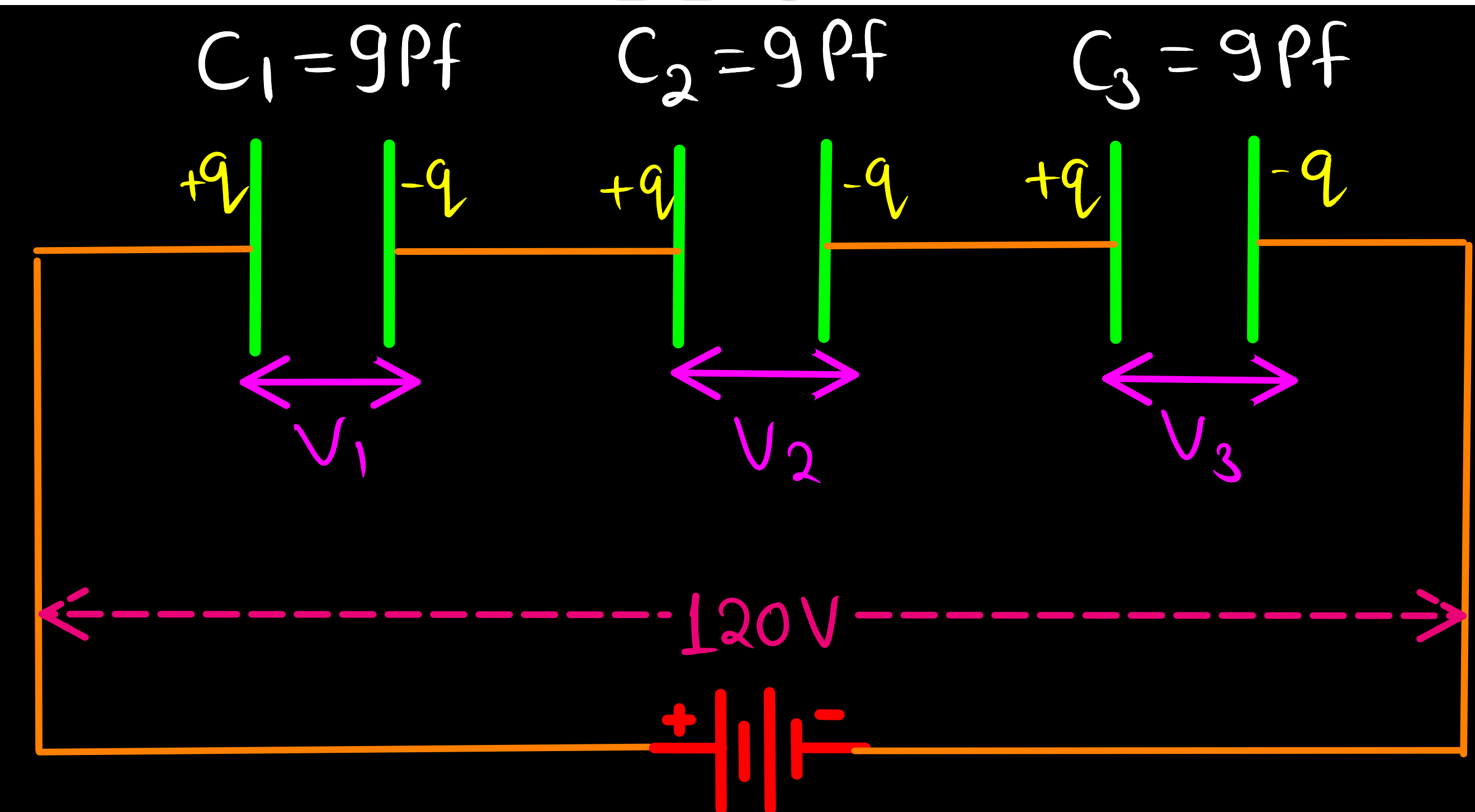

$$V_1 = \frac{q_1}{C_1} = \frac{q}{C_1}$$

$$V_1 = \frac{360 \times 10^{-12}}{9 \times 10^{-12}}$$

$$V_1 = 40 \text{ V}$$

$$V_2 = V_3 = V_1 = \underline{\underline{40 \text{ V}}}$$

2.7 Three capacitors of capacitances 2 pF, 3 pF and 4 pF are connected in parallel.

- (a) What is the total capacitance of the combination?
- (b) Determine the charge on each capacitor if the combination is connected to a 100 V supply.

a)


$$C = C_1 + C_2 + C_3$$
$$C = 2 \text{ pF} + 3 \text{ pF} + 4 \text{ pF}$$
$$C = 9 \text{ pF}$$

b)

$$q_1 = C_1 V$$
$$q_1 = 2 \times 10^{-12} \times 100$$
$$q_1 = 2 \times 10^{-10} \text{ C}$$

$$q_2 = C_2 V$$
$$q_2 = 3 \times 10^{-12} \times 100 = 3 \times 10^{-10} \text{ C}$$
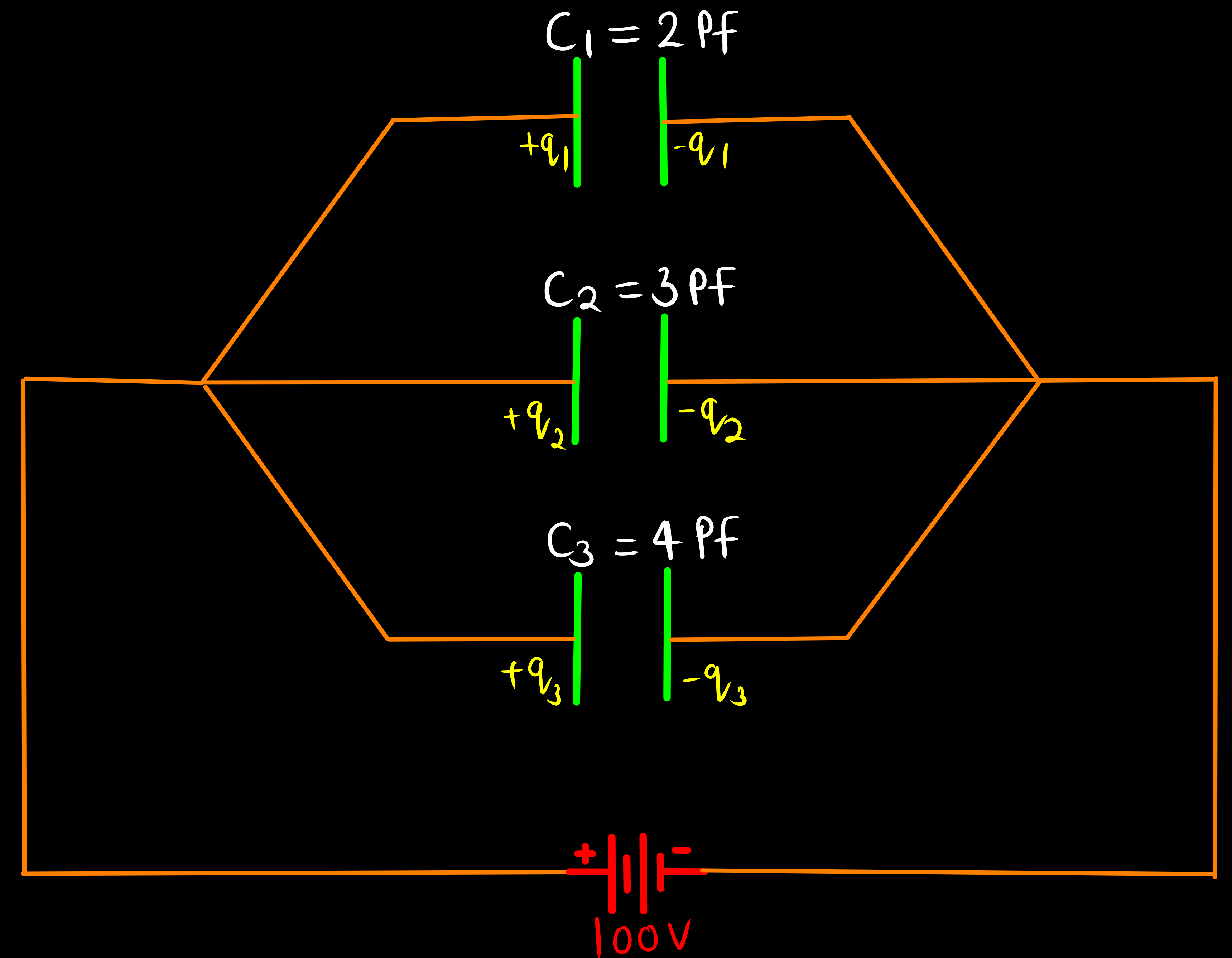
$$q_3 = C_3 V$$
$$q_3 = 4 \times 10^{-12} \times 100 = 4 \times 10^{-10} \text{ C}$$



a) C_1, C_2 , and C_3 are in series-

$$\frac{1}{C'} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C'} = \frac{1}{10} + \frac{1}{10} + \frac{1}{10} = \frac{3}{10}$$

$$C' = \frac{10}{3} \mu\text{F}$$

Now, C' and C_4 are in parallel

$$C = C' + C_4$$

$$C = \left(\frac{10}{3} + 10\right) \mu\text{F}$$

$$C = \frac{40}{3} \mu\text{F}$$

b) $q_4 = C_4 V$


$$q_4 = 10 \times 10^{-6} \times 500$$

$$q_4 = 5 \times 10^{-3} \text{ C}$$

$$V_1 + V_2 + V_3 = V$$

$$\frac{q}{C} + \frac{q}{C} + \frac{q}{C} = 500$$

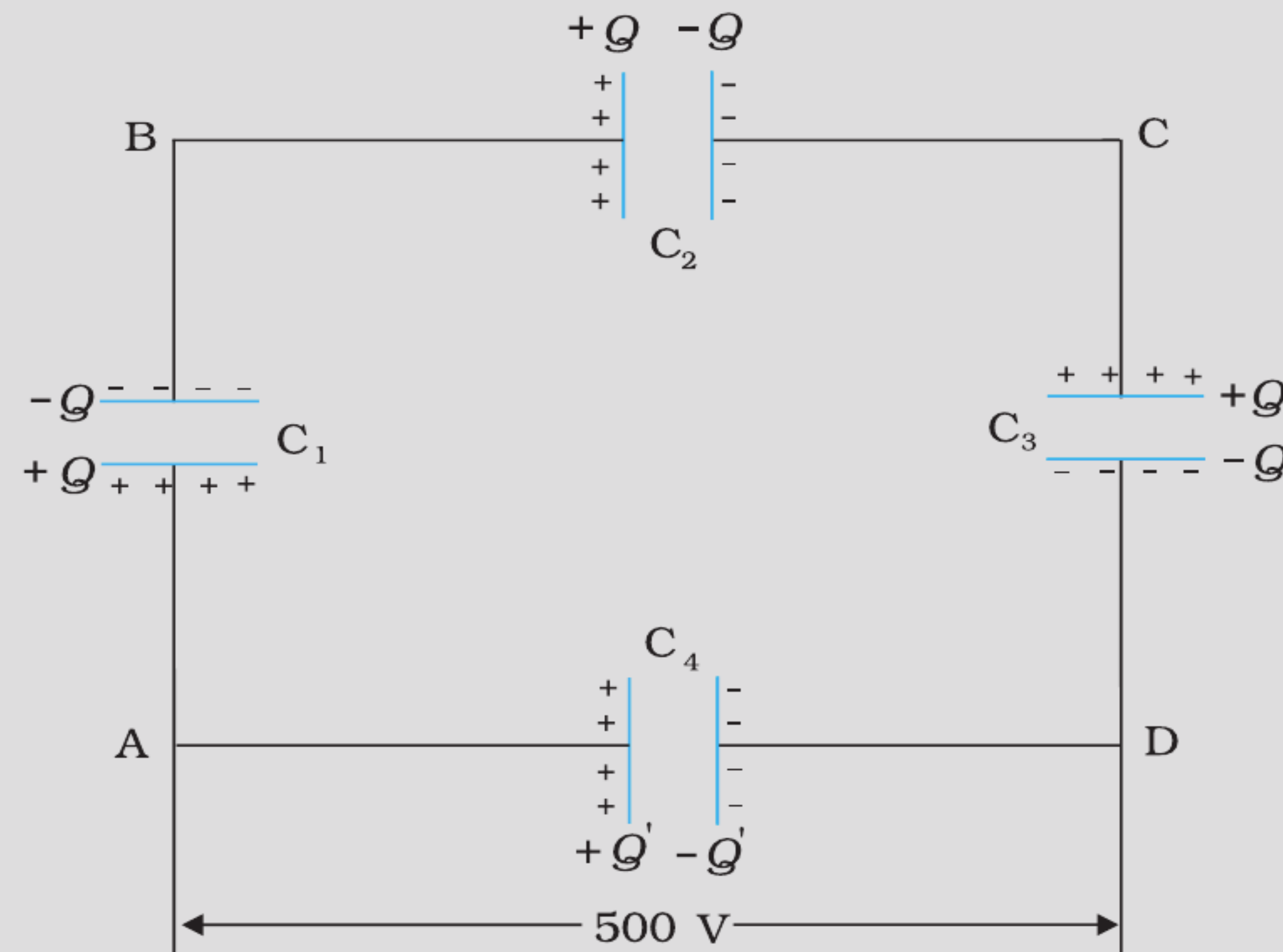Example 2.9 A network of four $10 \mu\text{F}$ capacitors is connected to a 500 V supply, as shown in Fig. 2.29. Determine (a) the equivalent capacitance of the network and (b) the charge on each capacitor. (Note, the *charge on a capacitor* is the charge on the plate with higher potential, equal and opposite to the charge on the plate with lower potential.)



$$\frac{3q}{C} = 500$$

$$q = \frac{500 \times C}{3} = \frac{500 \times 10 \times 10^{-6}}{3}$$

$$q = \frac{5}{3} \times 10^{-3} \text{ C}$$

$$q_1 = q_2 = q_3 = \frac{5}{3} \times 10^{-3} \text{ C}$$

2.10 A 12pF capacitor is connected to a 50V battery. How much electrostatic energy is stored in the capacitor?


$$C = 120 \text{ pF} , \quad V = 50 \text{ V}$$

$$U = \frac{1}{2} C V^2 \rightarrow \text{Energy stored in the capacitor}$$

$$U = \frac{1}{2} \times 120 \times 10^{-6} \times 50$$

$$U = 3 \times 10^{-3} \text{ J}$$

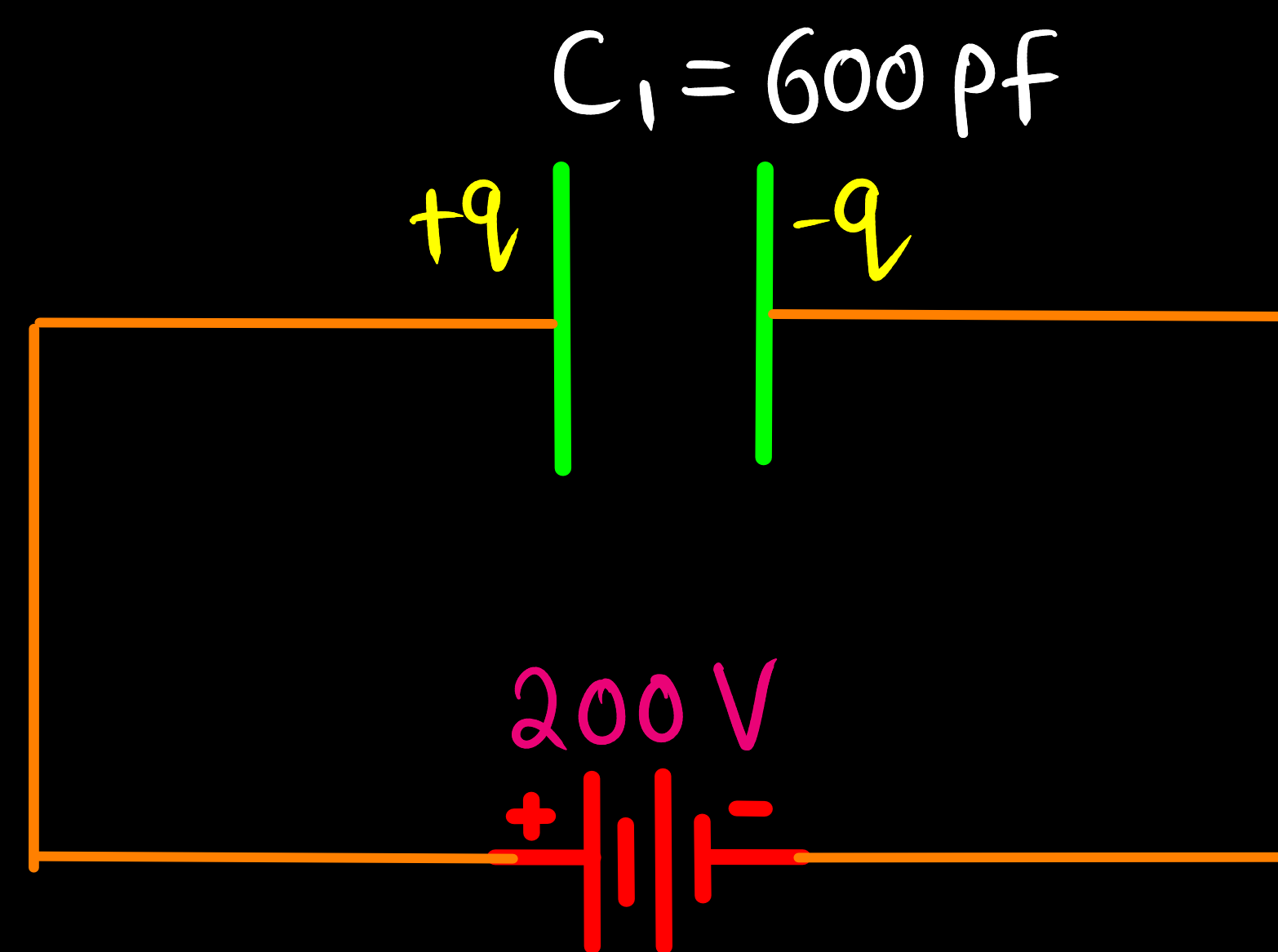2.11 A 600pF capacitor is charged by a 200V supply. It is then disconnected from the supply and is connected to another uncharged 600 pF capacitor. How much electrostatic energy is lost in the process?



* Initial potential energy


$$U_i = \frac{1}{2} C_1 V^2$$

$$U_i = \frac{1}{2} \times 600 \times 10^{-12} \times 200^2$$

$$U_i = 12 \times 10^{-6} \text{ J}$$

$$\text{Energy lost} = U_i - U_f = 12 \times 10^{-6} \text{ J} - 6 \times 10^{-6} \text{ J}$$
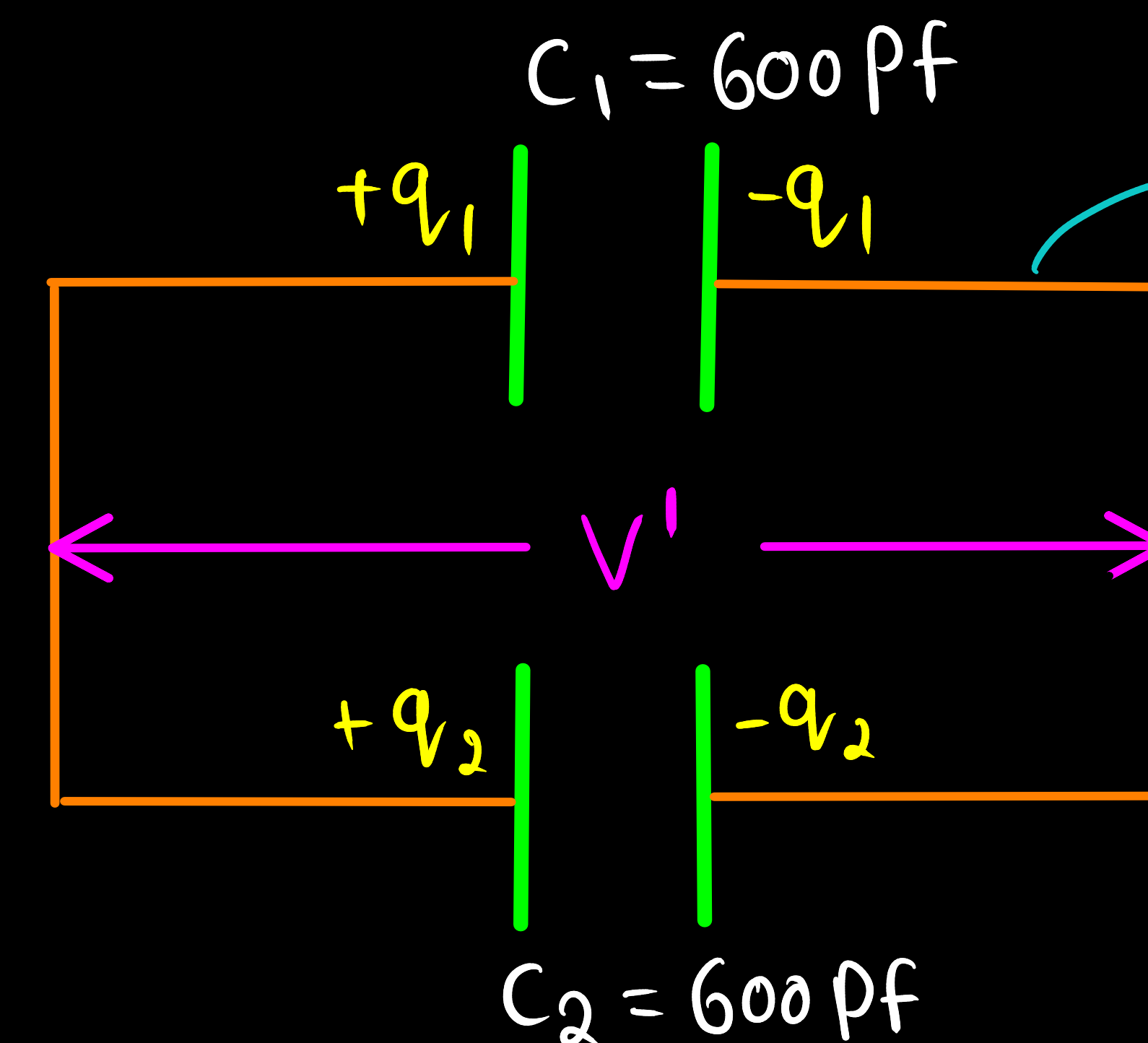
$$\text{Energy lost} = 6 \times 10^{-6} \text{ J}$$



Charge will flow from C_1 to C_2 until both capacitors have common potential.

$$q_1 + q_2 = q$$

↳ Conservation of Charge.

$$* \quad q_1 + q_2 = q$$

$$\frac{C}{V'} + \frac{C}{V'} = q$$

$$\frac{2C}{V'} = q$$

$$V' = \frac{q}{2C} = \frac{V}{2} = \frac{200}{2} = 100 \text{ V}$$

$$C' = C_1 + C_2 = 1200 \text{ pF}$$

Final Potential Energy -

$$U_f = \frac{1}{2} C' V'^2$$

$$U_f = \frac{1}{2} \times 1200 \times 10^{-12} \times 100 \times 100$$

$$U_f = 6 \times 10^{-6} \text{ J}$$