

CELLS, EMF, INTERNAL RESISTANCE


Chapter [3] - Current Electricity
Class - XII

Manish Joshi

D.A.V. Lohaghat

August 17, 2024


CELLS, EMF, INTERNAL RESISTANCE

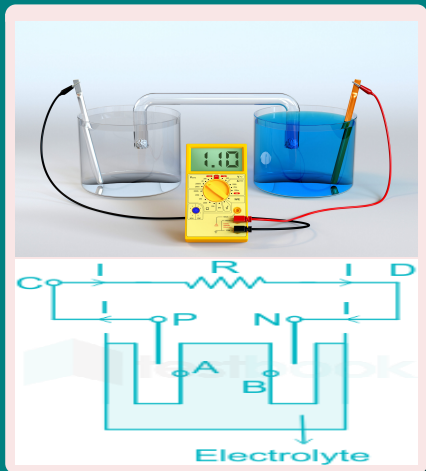

Electric Cell

- **Electric Cell** is a **device** that can **generate** electrical energy from **chemical** processes.


CELLS, EMF, INTERNAL RESISTANCE

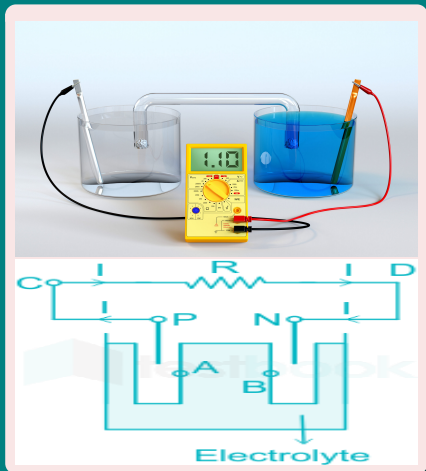

Electric Cell

- **Electric Cell** is a **device** that can **generate electrical energy from chemical processes**.
- Basically a **cell has two electrodes**, called the **positive (P)** and the **negative (N)**, They are immersed in an **electrolytic solution**.


CELLS, EMF, INTERNAL RESISTANCE

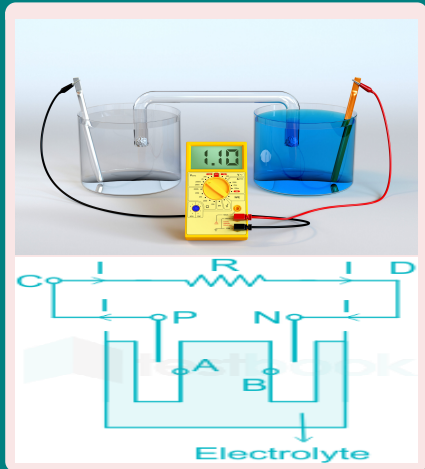

EMF

- When there is **no current (open circuit)**, the potential difference between the positive and negative electrode is called the **electromotive force (emf)** of the cell (ϵ).


CELLS, EMF, INTERNAL RESISTANCE

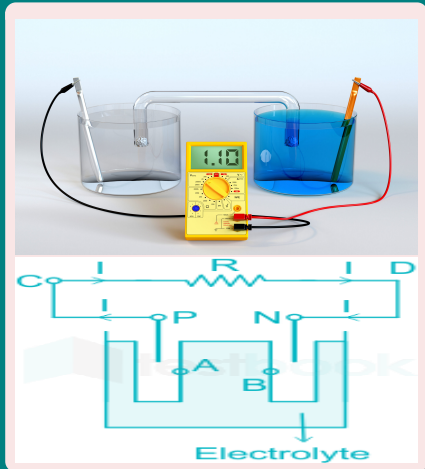

EMF

- When there is **no current (open circuit)**, the potential difference between the positive and negative electrode is called the **electromotive force (emf)** of the cell (ϵ).
- Note that **emf** is, actually, a **potential difference** and **not a force**.


CELLS, EMF, INTERNAL RESISTANCE

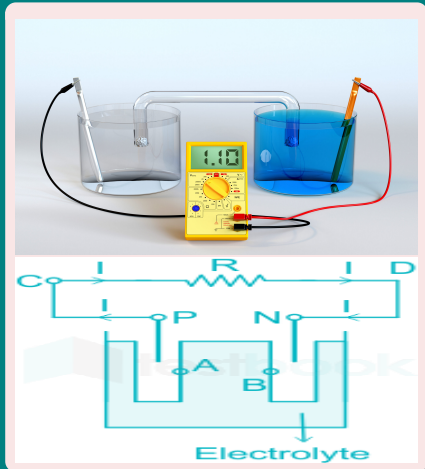

EMF

- When there is **no current (open circuit)**, the potential difference between the positive and negative electrode is called the **electromotive force (emf)** of the cell (ϵ).
- Note that **emf** is, actually, a **potential difference** and **not a force**.
- **Current flows** through the **electrolyte** from **N to P**, whereas through **R**, it flows from **P to N**.


CELLS, EMF, INTERNAL RESISTANCE

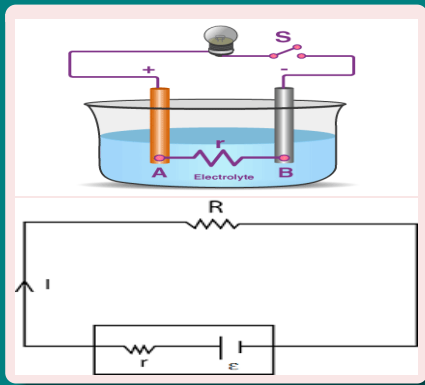

Internal Resistance Terminal Voltage

- The **electrolyte** through which a current flows has a **finite resistance r** , called the **internal resistance**.


CELLS, EMF, INTERNAL RESISTANCE

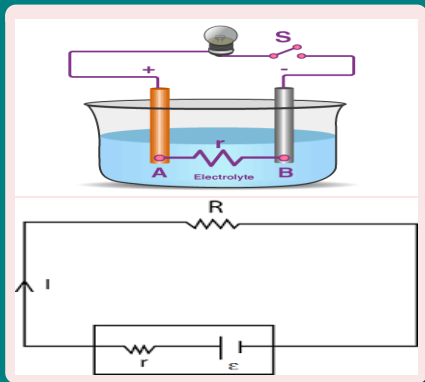

Internal Resistance Terminal Voltage

- The **electrolyte** through which a current flows has a **finite resistance r** , called the **internal resistance**.
- If **V** is the **potential difference** across **external resistor R** , also known as **terminal voltage**. then using Ohm's Law

CELLS, EMF, INTERNAL RESISTANCE

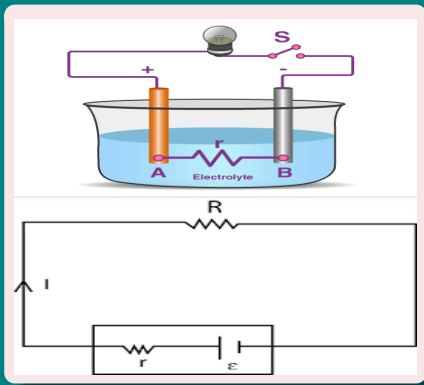


Internal Resistance Terminal Voltage

- The **electrolyte** through which a current flows has a **finite resistance r** , called the **internal resistance**.
- If **V** is the **potential difference** across **external resistor R** , also known as **terminal voltage**. then using Ohm's Law

$$\epsilon = I(r + R) \dots(1)$$

CELLS, EMF, INTERNAL RESISTANCE

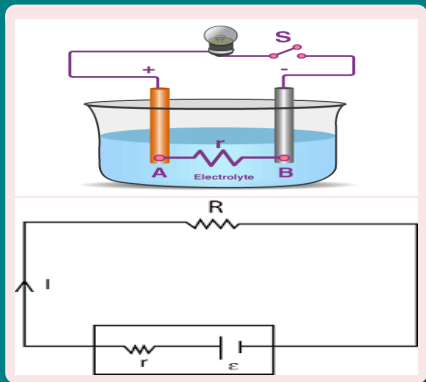


Internal Resistance Terminal Voltage

- The **electrolyte** through which a current flows has a **finite resistance r** , called the **internal resistance**.
- If **V** is the **potential difference** across **external resistor R** , also known as **terminal voltage**. then using Ohm's Law

$$\epsilon = I(r + R) \dots\dots(1)$$

$$\epsilon = Ir + IR$$

CELLS, EMF, INTERNAL RESISTANCE

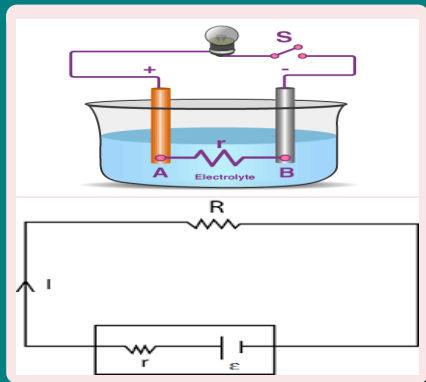

Internal Resistance Terminal Voltage


- The **electrolyte** through which a current flows has a **finite resistance r** , called the **internal resistance**.
- If **V** is the **potential difference** across **external resistor R** , also known as **terminal voltage**. then using Ohm's Law

$$\epsilon = I(r + R) \dots\dots(1)$$

$$\epsilon = Ir + IR$$

$$\boxed{\epsilon - Ir = V} \quad \because (V = IR)$$


CELLS, EMF, INTERNAL RESISTANCE

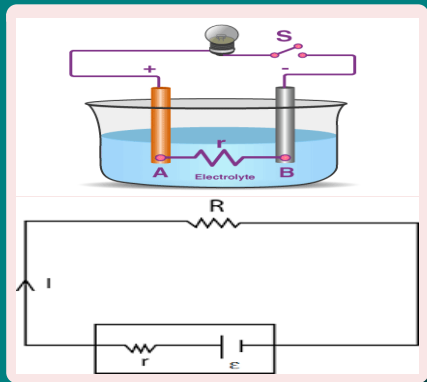

Internal Resistance and Terminal Voltage

- If no current ($I = 0$) is drawn from the cell (i.e., in an **open circuit**), the **potential difference V** across its terminal is **equal to its emf** ($\epsilon = V$)


CELLS, EMF, INTERNAL RESISTANCE

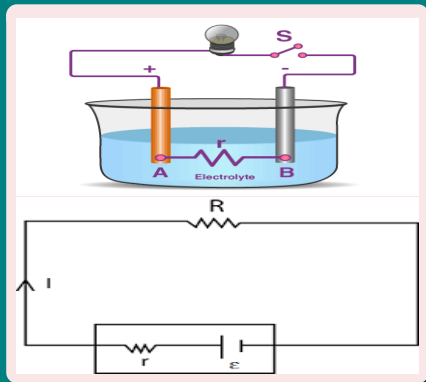

Internal Resistance and Terminal Voltage

- If no current ($I = 0$) is drawn from the cell (i.e., in an **open circuit**), the **potential difference V** across its terminal is **equal to its emf** ($\epsilon = V$)
- if $I \neq 0$ V is less than ϵ


CELLS, EMF, INTERNAL RESISTANCE

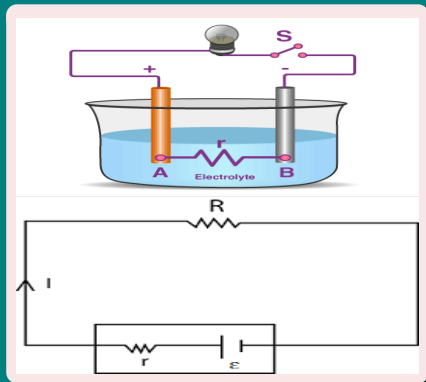

Internal Resistance and Terminal Voltage

- If no current ($I = 0$) is drawn from the cell (i.e., in an **open circuit**), the **potential difference V** across its terminal is **equal to its emf** ($\epsilon = V$)
- if $I \neq 0$ V is less than ϵ
- From eq(1) We have $I = \frac{\epsilon}{R + r}$

CELLS, EMF, INTERNAL RESISTANCE

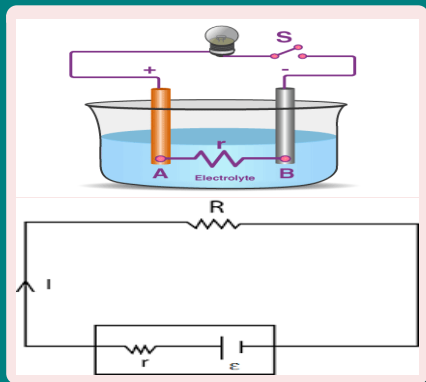

Internal Resistance and Terminal Voltage

- If no current ($I = 0$) is drawn from the cell (i.e., in an **open circuit**), the **potential difference V** across its terminal is **equal to its emf** ($\epsilon = V$)
- if $I \neq 0$ V is less than ϵ
- From eq(1) We have $I = \frac{\epsilon}{R + r}$
- The **maximum current** that can be **drawn from a cell** is for $R = 0$ and it is $I_{max} = \frac{\epsilon}{r}$.

Numericals

Question 3.1

The storage battery of a car has an **emf** of 12 V . If the **internal resistance** of the battery is $0.4\ \Omega$, what is the **maximum current** that can be drawn from the battery?

Numericals

Question 3.2

A battery of **emf 10 V** and **internal resistance** $3\ \Omega$ is connected to a resistor. If the **current** in the circuit is $0.5\ \text{A}$, what is the **resistance of the resistor**? What is the **terminal voltage** of the battery when the circuit is closed?


Numericals

Example 1

A voltmeter of resistance $998\ \Omega$ is connected across a cell of emf 2 V and internal resistance $2\ \Omega$. Find the potential difference across the voltmeter, that across the terminals of the cell and percentage error in the reading of the voltmeter [CBSE OD 19]

Numericals

Example 2

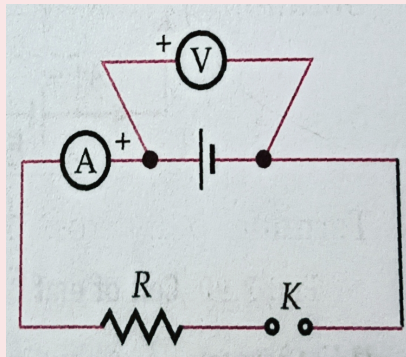

In the circuit shown in fig., the voltmeter reads 1.5 V, when key is open. When the key is closed, the voltmeter reads 1.35 V and ammeter reads 1.5 A. Find the emf and the internal resistance of the cell.

Numericals

Example 3

A battery of emf 12 V and internal resistance $4\ \Omega$ is connected to an external resistance R . If the current in the resistance is 0.5 A, calculate the value of (a) R , and (b) the terminal voltage of the battery. [CBSE F 20]

Numericals

Example 4

A battery of e.m.f ξ and internal resistance ' r ', gives a current of 0.5 A with an external resistor of $12\ \Omega$ and a current of 0.25 A with an external resistor of $25\ \Omega$. Calculate (i) internal resistance of the cell and (ii) emf of the cell [CBSE D 02]


Numericals

Example 5

A battery of emf 3 volt and internal resistance r is connected in series with a resistor of $55\ \Omega$ through an ammeter of resistance $1\ \Omega$. The ammeter reads 50 mA. Draw the circuit diagram and calculate the value of r . [CBSE D 95]

Numericals

Example 6

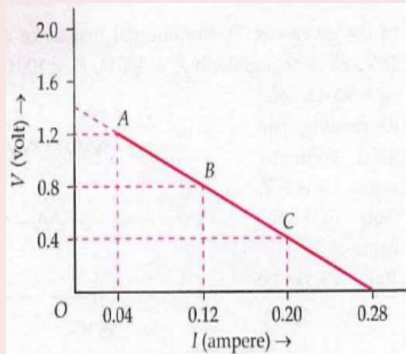

Potential differences across terminals of a cell were measured (in volt) against different currents (in ampere) flowing through the cell. A graph was drawn which was a straight line ABC, as shown in Fig. Determine from the graph

- (i) e.m.f. of the cell.
- (ii) maximum current obtained from the cell, and
- (iii) internal resistance of the cell [CBSE D 11C]

Numericals

Example 7


A cell of emf ξ and internal resistance r is connected across a variable load resistor R . It is found that when $R = 4\ \Omega$, the current is 1 A and when R is increased to $9\ \Omega$, the current reduces to 0.5 A . Find the values of the emf ξ and internal resistance r .

Numericals

Example 8


A cell of emf 4 V and internal resistance $1\ \Omega$ connected to a d.c. source of 10 V through a resistor of $5\ \Omega$. Calculate the terminal voltage across the cell during charging.

CELLS IN SERIES AND IN PARALLEL

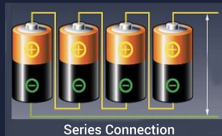


- A cell is source of electric current.
- A single cell cannot give a strong current. Therefore, to get strong current two or more cells are to be combined.
- The combination of cells is called a "battery".
- Cells can be combined in three ways:
 - 1 In series
 - 2 In parallel and,
 - 3 In mixed grouping.

CELLS IN SERIES

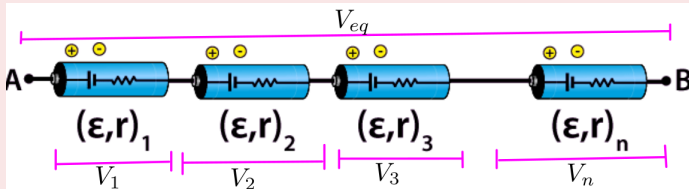

- Consider **n number of cells** are **connected in series**.
- Let $\epsilon_1, \epsilon_2, \dots, \epsilon_n$ are the **emf** of these cells and $r_1, r_2, \dots, r_n$ their **internal resistance** respectively.
- Let $(V_1 = \epsilon_1 - Ir_1), (V_2 = \epsilon_2 - Ir_2), \dots, (V_n = \epsilon_n - Ir_n)$ be the **potential difference** across each cells respectively.

CELLS IN SERIES

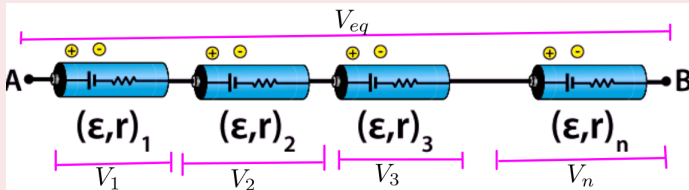

- Hence, the potential difference V_{eq} between the terminals A and B of the combination is

$$V_{eq} = V_1 + V_2 + \cdots + V_n$$
$$V_{eq} =$$